

# Single Cycle Architecture

---

Part 2

# I get enough time to answer clicker questions

---

- A) NO -never
- B) YES -always
- C) Yes and NO but I could use more time



# Office hours : Today 1-2

## Thursday by appointment(this week)

---

In class I find the Pace of the lecture...

- A) Too fast
- B) Too slow
- C) Bit too fast
- D) Bit too slow
- E) Just Right 😊

# Midterm June 18 Thursday

---

- Will do some in class review on Wed (june 17)
- Covering everything ending at Monday Lecture


# What Statement about memory in the Datapath is NOT true 😊


---

- A) the instruction and data memory are a type of cache
- B) Data memory can be read from and written to
- C) The Registers contain memory in flip flops
- D) The Register file allows reading and writing to the registers
- E) The Instruction memory in the datapath allows reading of instructions and writing new instructions


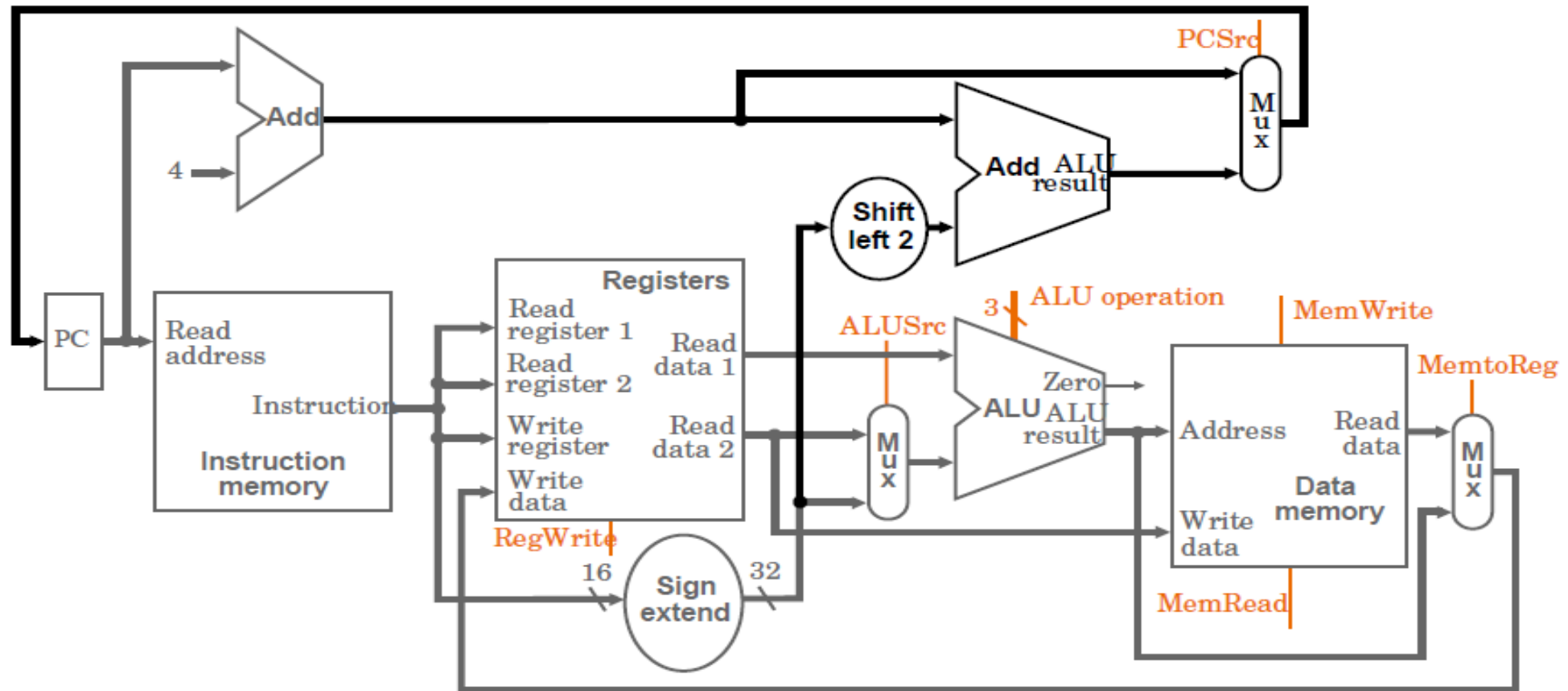
## Assembled Datapath Without Control Unit:




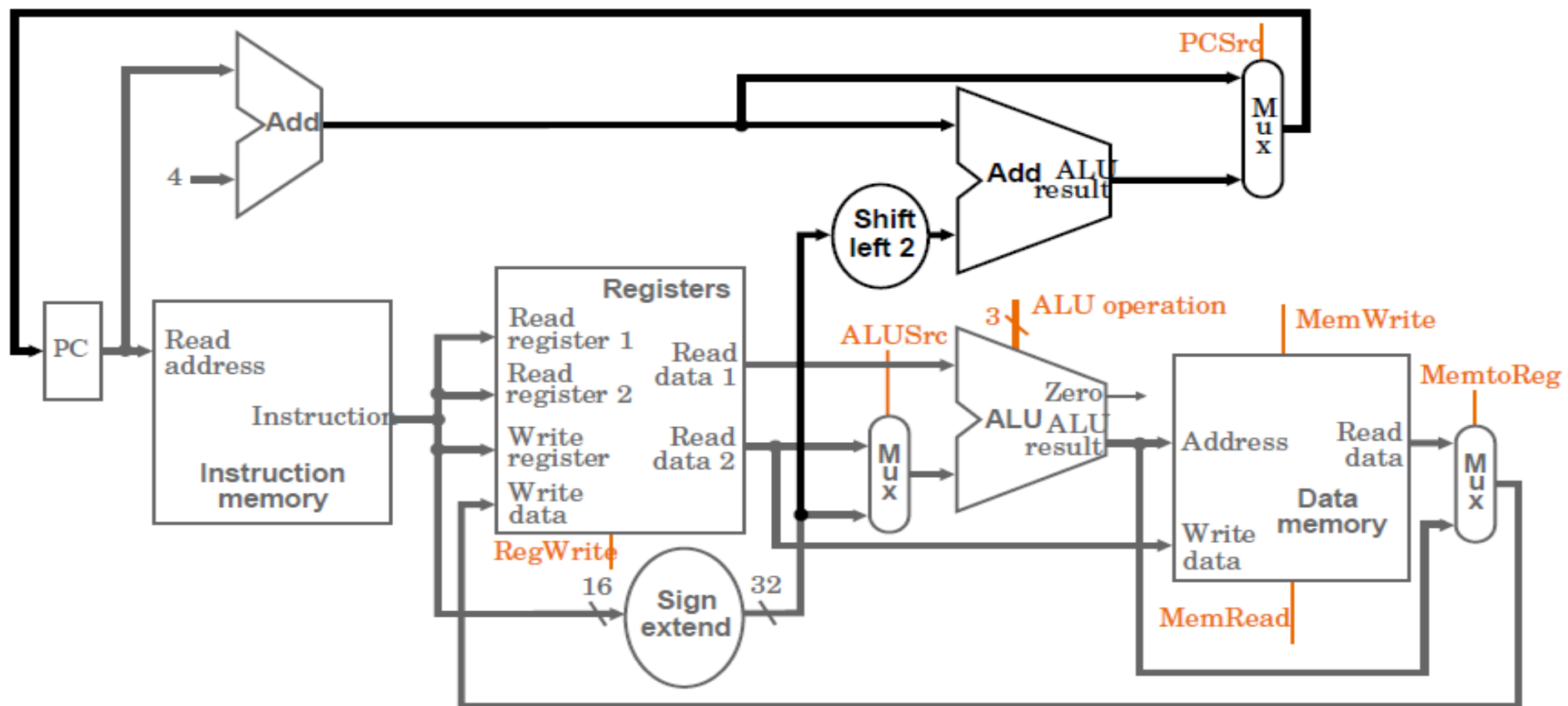

**add \$t1, \$t2, \$t3**





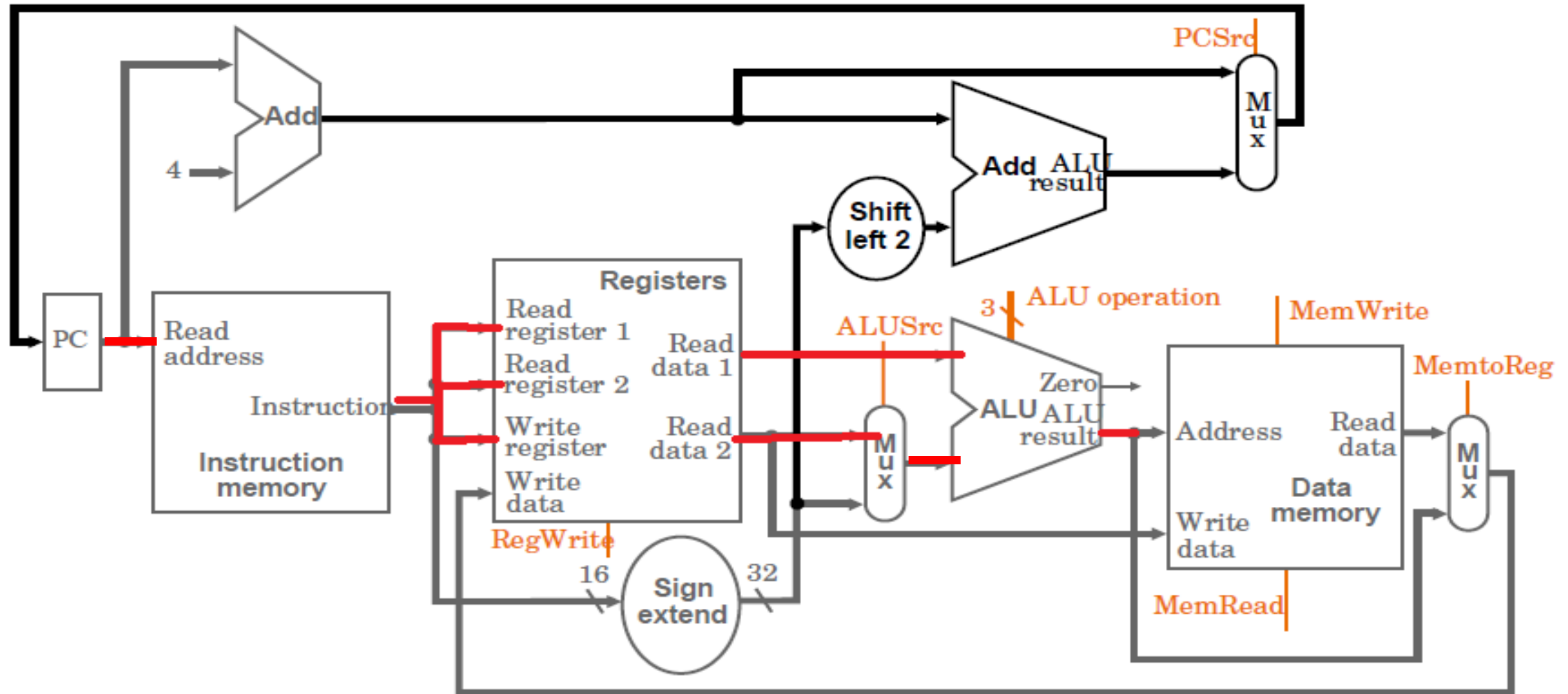


**add \$t1, \$t2, \$t3**

Next: Take Data of the two source registers

\*Send this through the ALU, Perform an operation  
as given in the instruction (add).

\*Produce a Result – out of the ALU




 

**add \$t1, \$t2, \$t3**    Next: This result needs to be Written to the Destination register.  
                                  \*provide the result as Write Data to register file  
                                  \*Writing to the Register file occurs at END of the clock cycle.

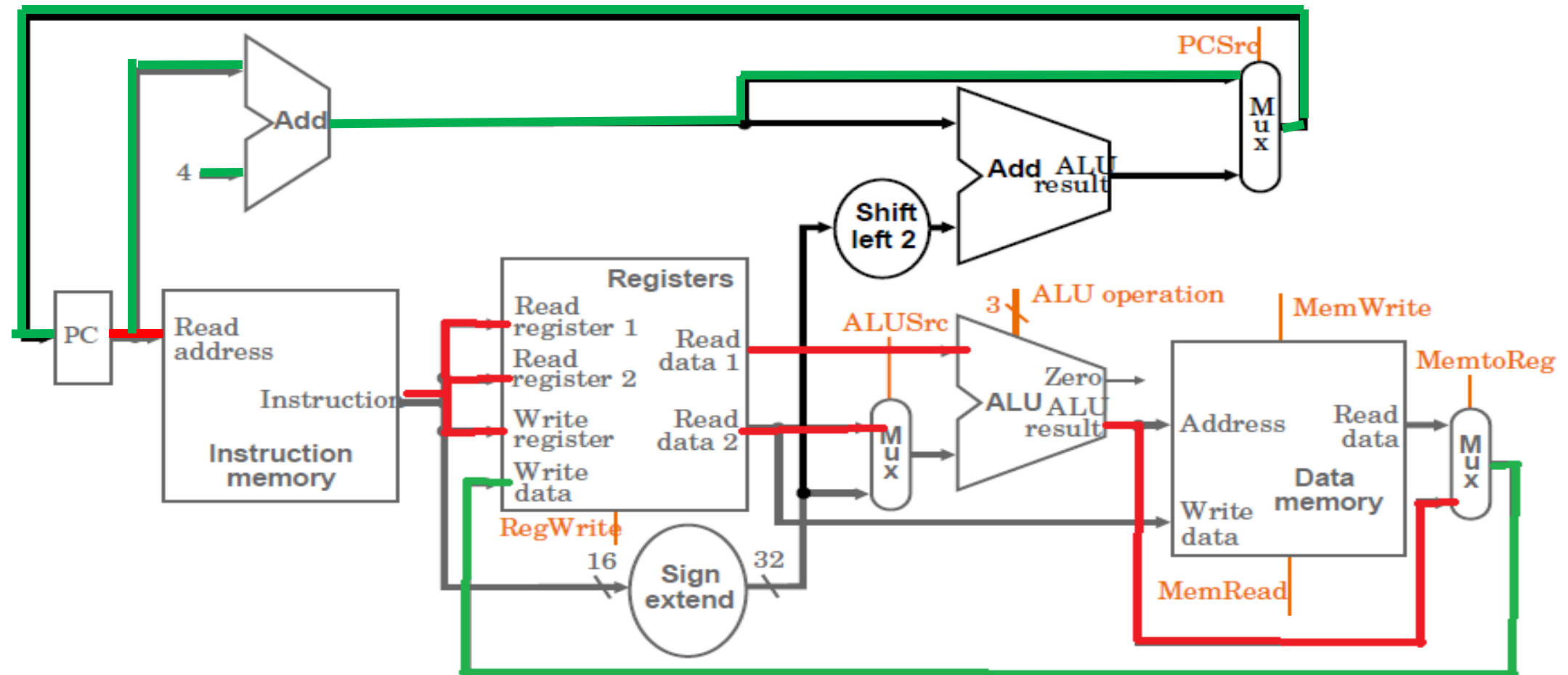All writes will occur at the end of the clock cycle: Including PC update





**add \$t1, \$t2, \$t3**    **Important: Control Line Bits (Select lines to Multiplexors, and other control lines) are essential in this process**


**Control Lines must guarantee that Add instruction will get executed in the datapath**



\_\_\_\_\_




lw \$t1, 100(\$t2)

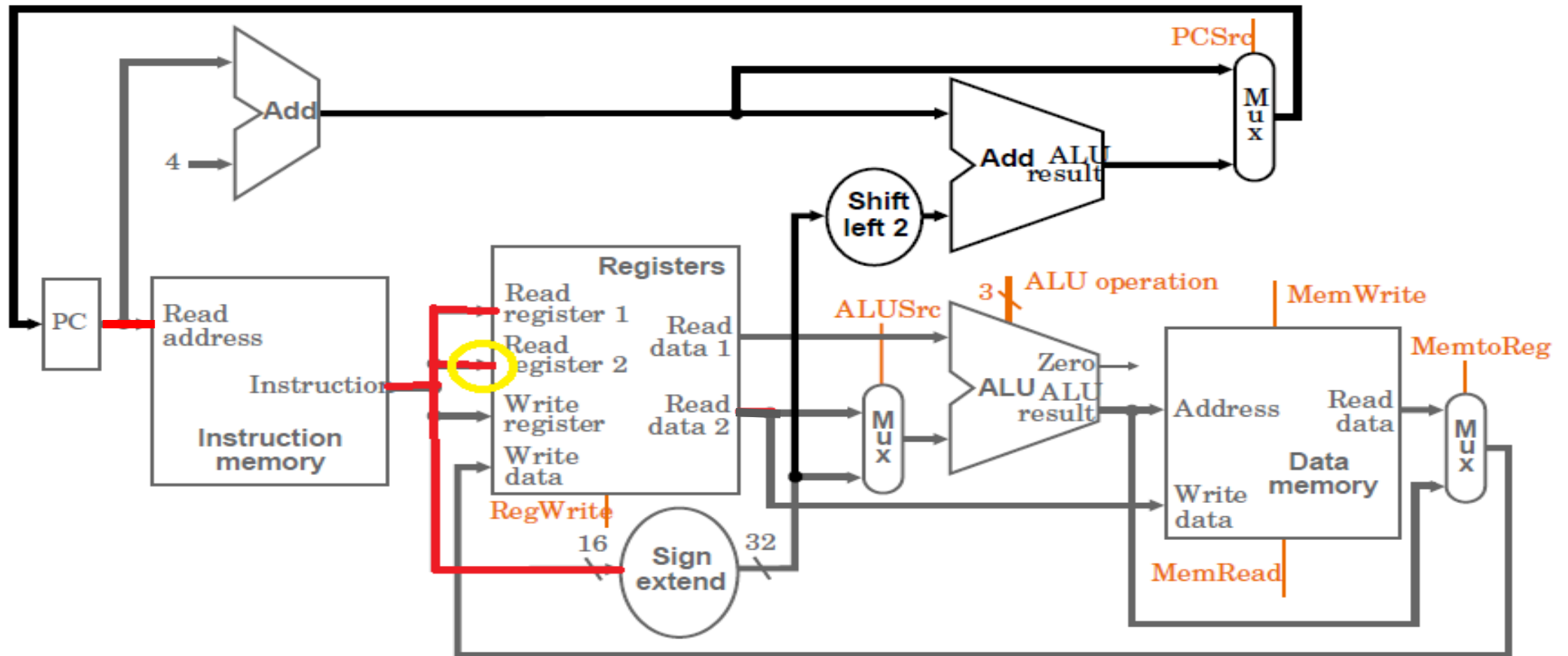


Now the `rt` register is the destination \_Not a source

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`






lw \$t1, 100(\$t2)

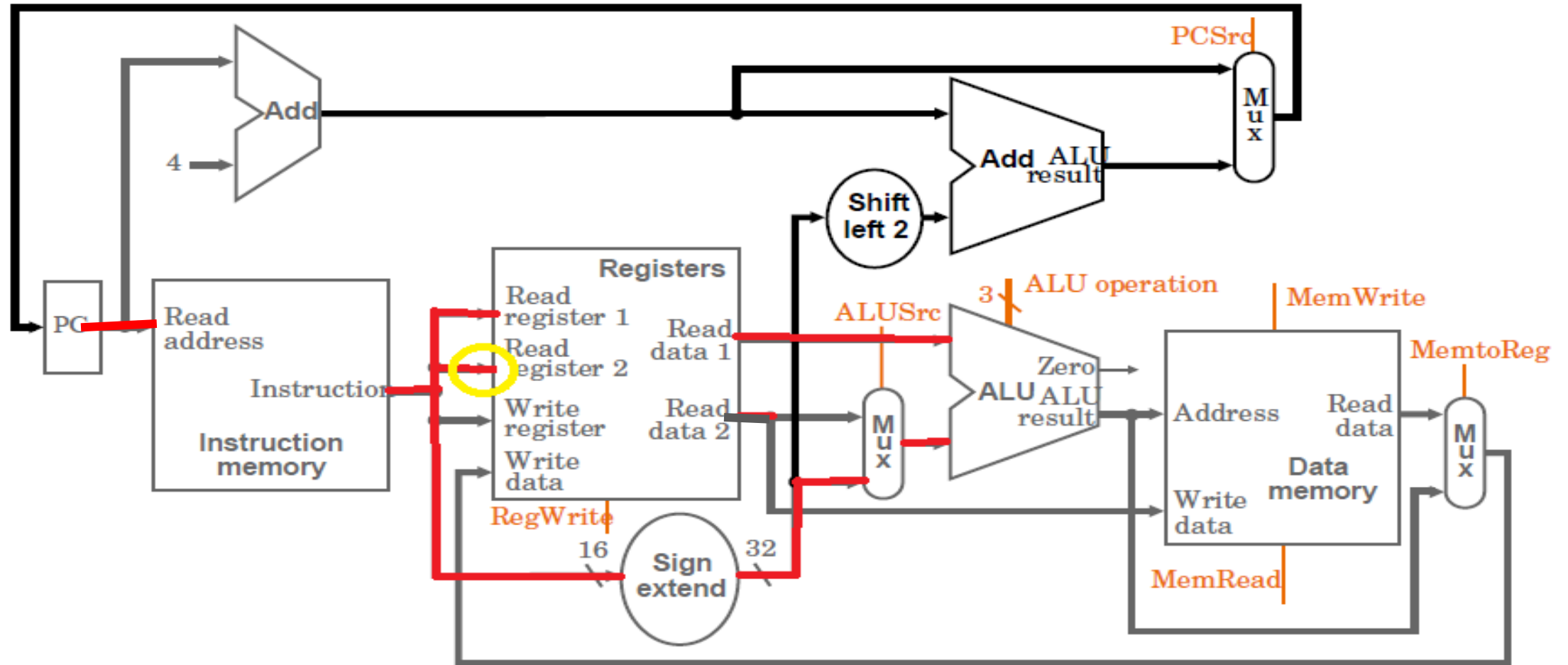


ALU: Will perform  $rs + \text{sign extended offset}$   
\*Sign Extend?

 Load/store: `lw $t1, 100($t2)  $\Rightarrow$  lw rt, 100(rs)`




lw \$t1, 100(\$t2)

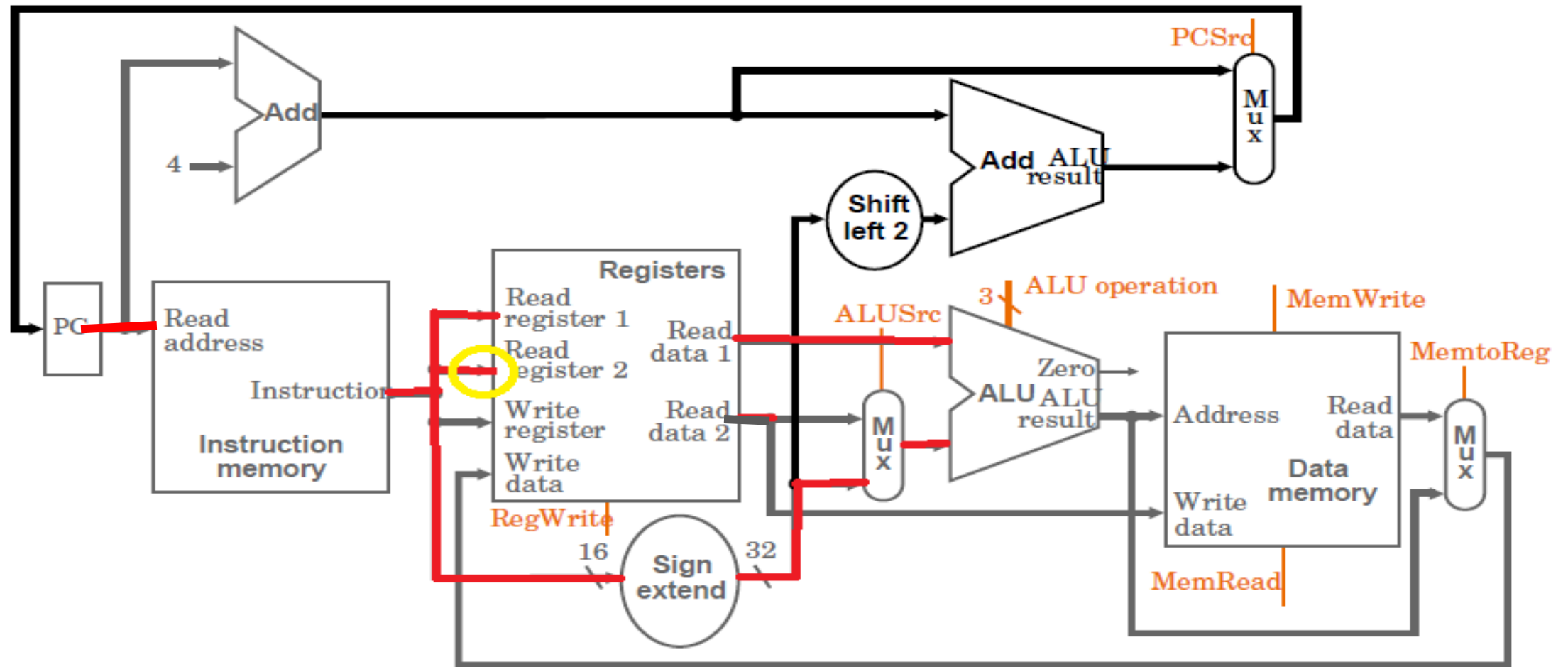


ALU: Will perform  $rs + \text{sign extended offset}$

\*Sign Extend → ALU needs two inputs that are 32 bits each

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`




lw \$t1, 100(\$t2)

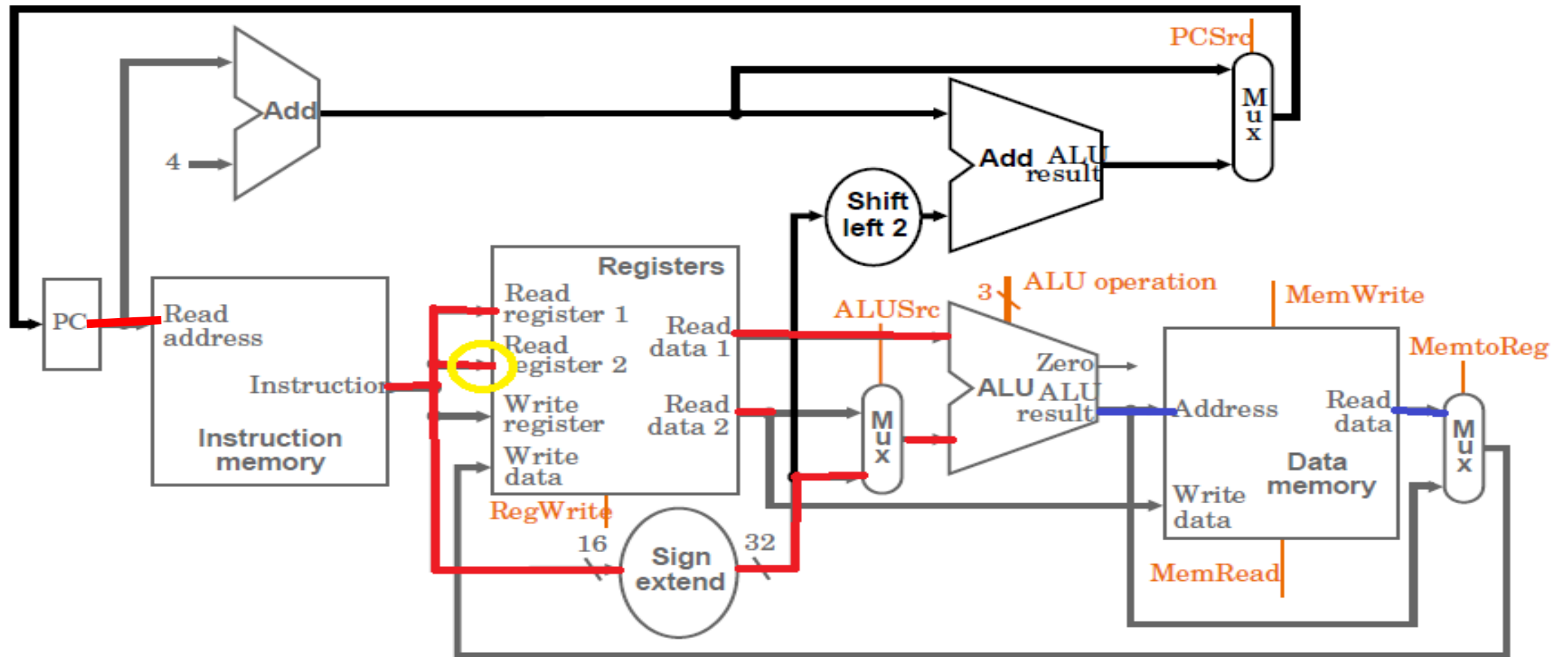


Result of ALU is an Address: Use this address to Access Data Memory

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`





lw \$t1, 100(\$t2)

 


Once we access data memory  $\rightarrow$  we now have 32 bits of data

 
**\* this data needs to be written to destination register (rt)**

- \* therefore send data back to register file

Load/store: lw \$t1, 100(\$t2)  $\Rightarrow$  lw rt, 100(rs)




lw \$t1, 100(\$t2)

 


We need **rt** to be the Write Register

Need more hardware here : to connect **rt** as also an option for a write register

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



Add in a Multiplexor

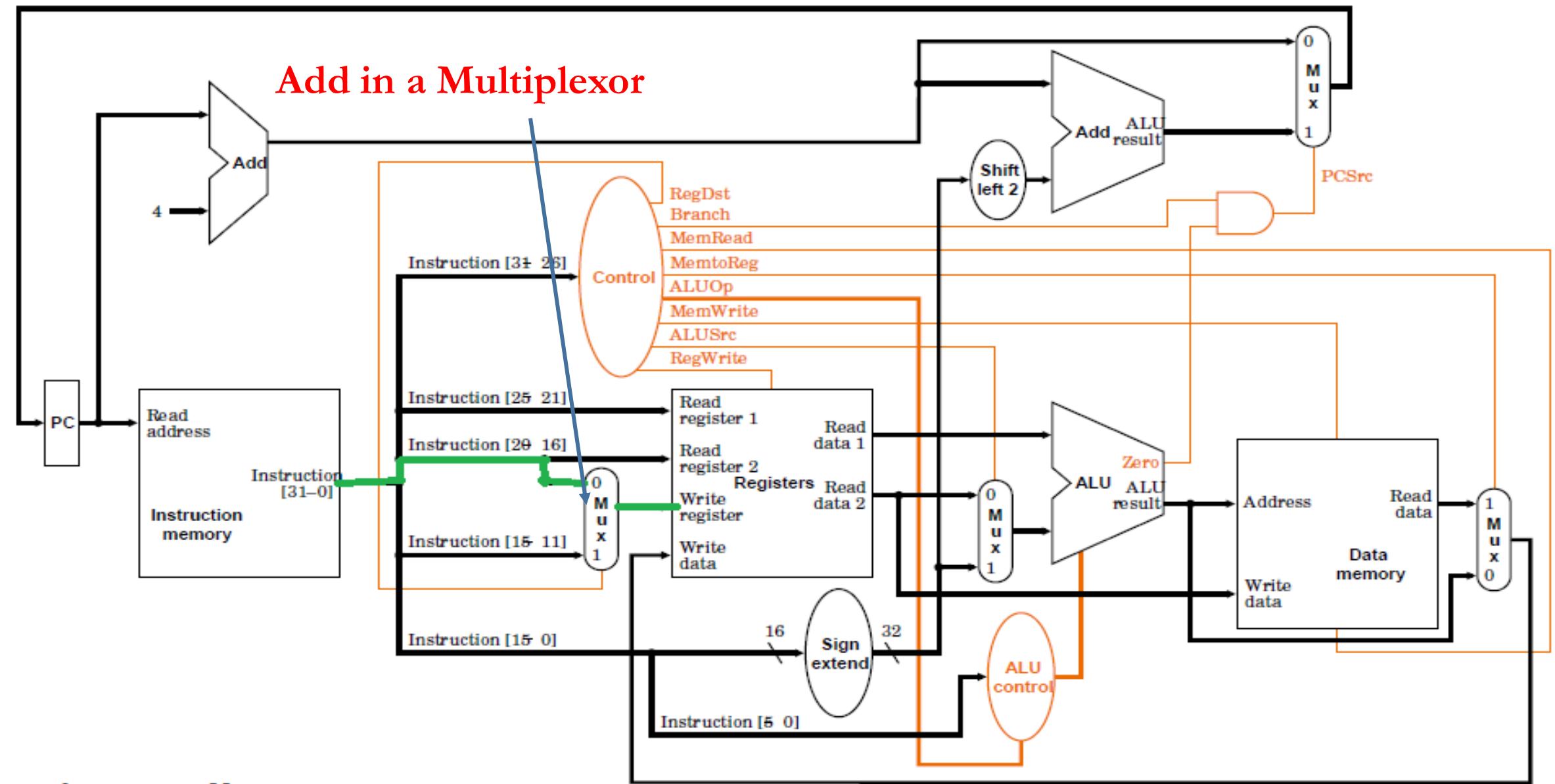

lw rs rt offset

Load/store: lw \$t1, 100(\$t2)  $\Rightarrow$  lw rt, 100(rs)

