


# Single Cycle Architecture

---

Part 3

 
# How the Instruction Bits are Broken up:

R-format: `add $t1, $t2, $t3`  $\Rightarrow$  `add rd, rs, rt`



sll, sub

 Load/store: `lw $t1, 100($t2)`  $\Rightarrow$  `lw rt, 100(rs)`




beq, subi, addi

Jump: `j 3000`



special

beq \$t1, \$t2, 28

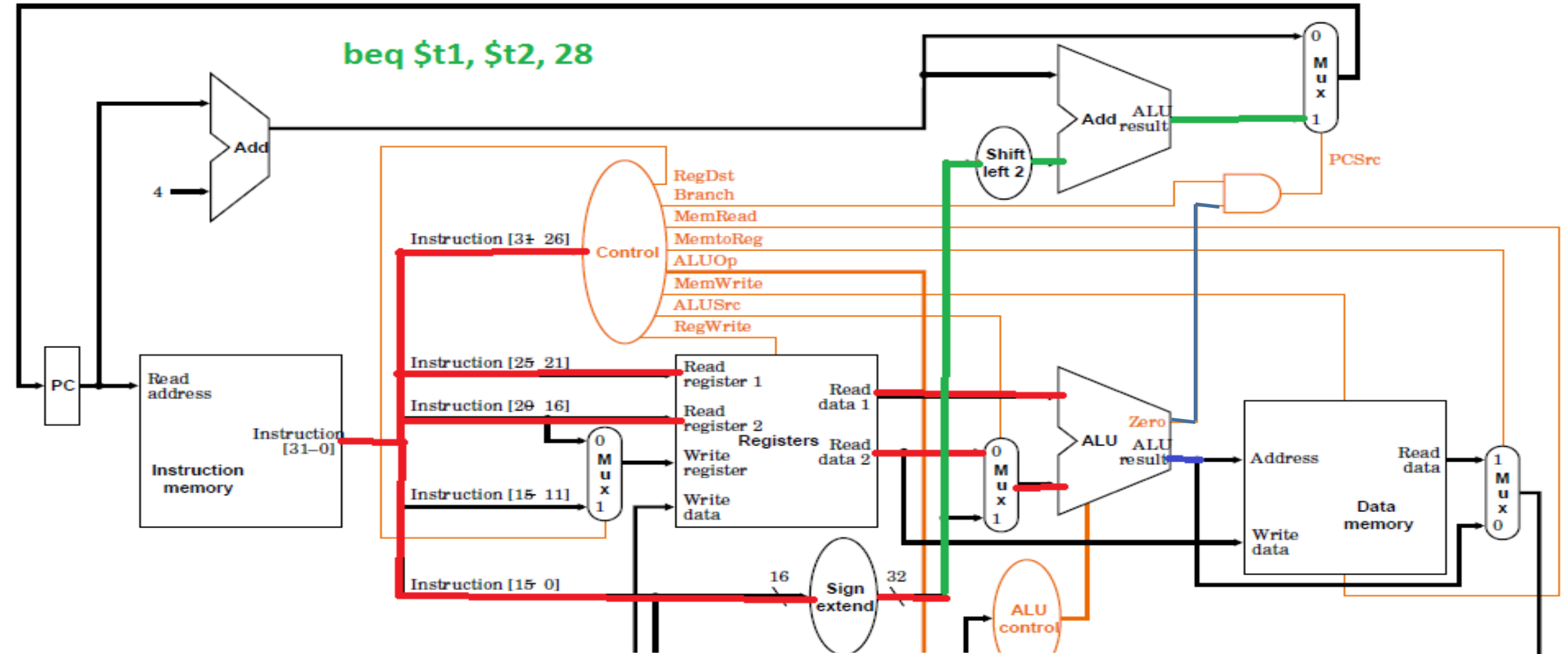


Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Tells you exactly what the control lines  
Need to be for each instruction




Which instruction is this?

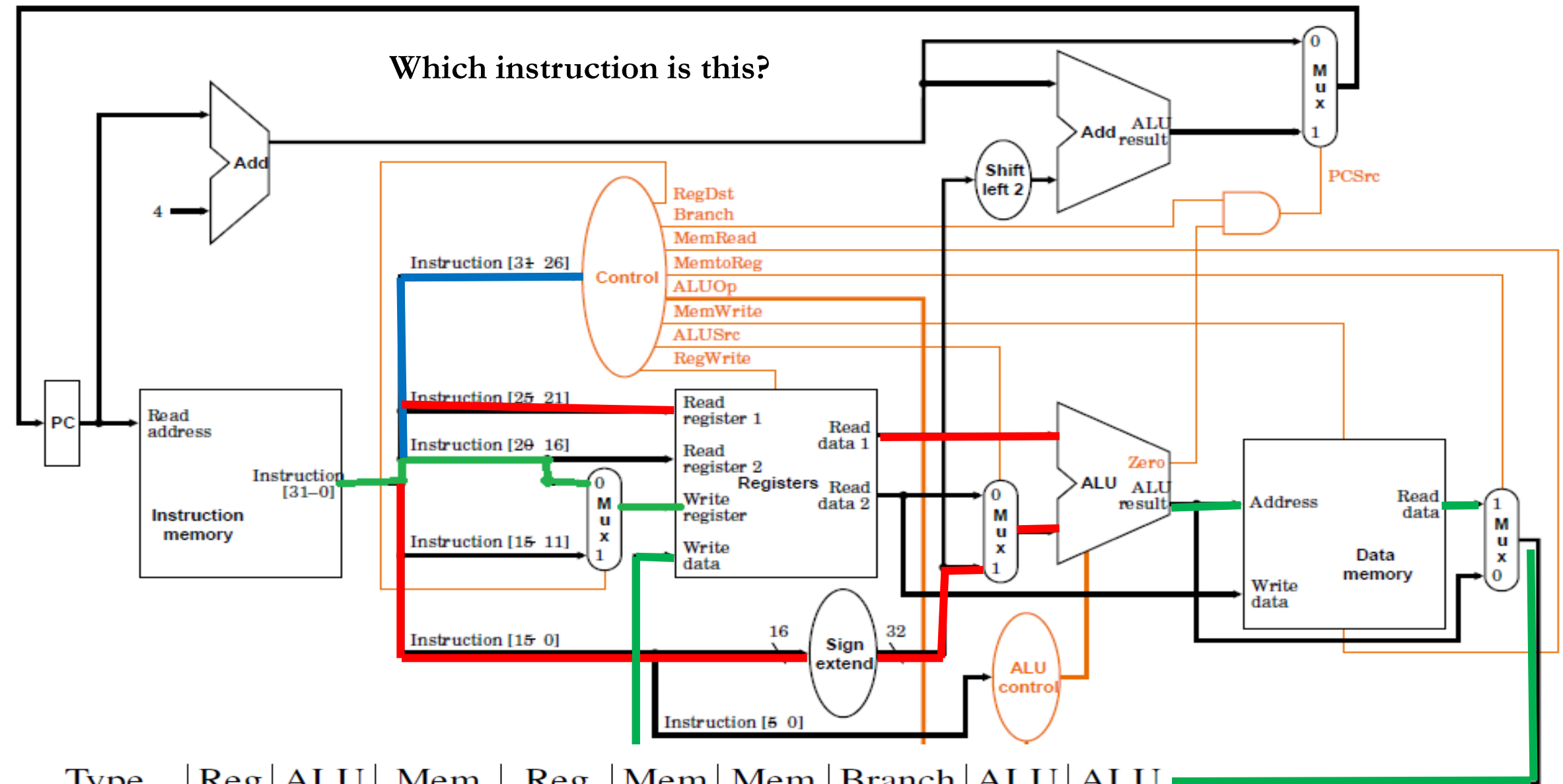

Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0

Which instruction is this?

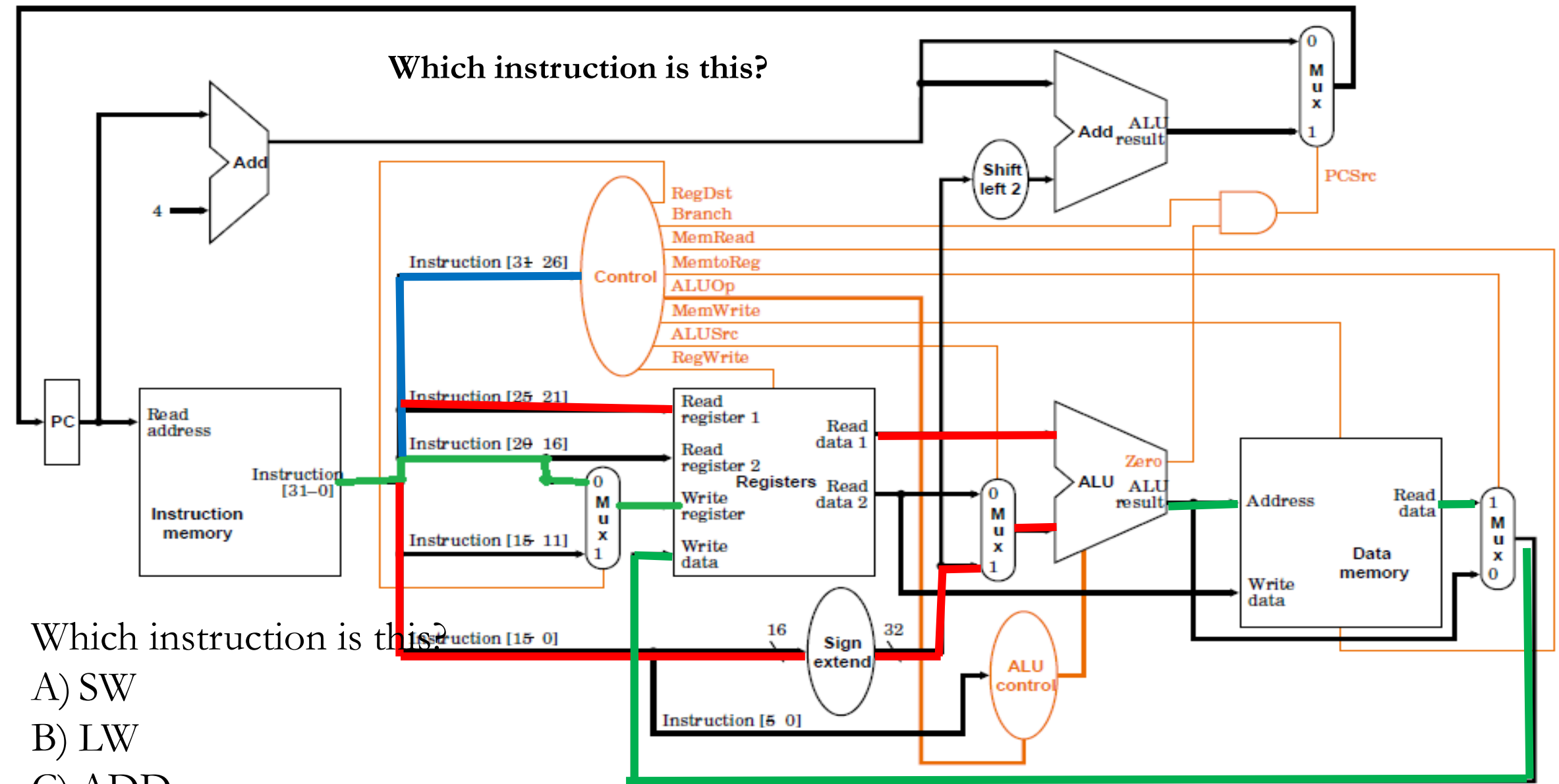


Which instruction is this?

- A) SW
- B) LW
- C) ADD
- D) SUB
- E) ANY

# Control Units : Course Notes


---

sw \$t1, 100(\$t2)

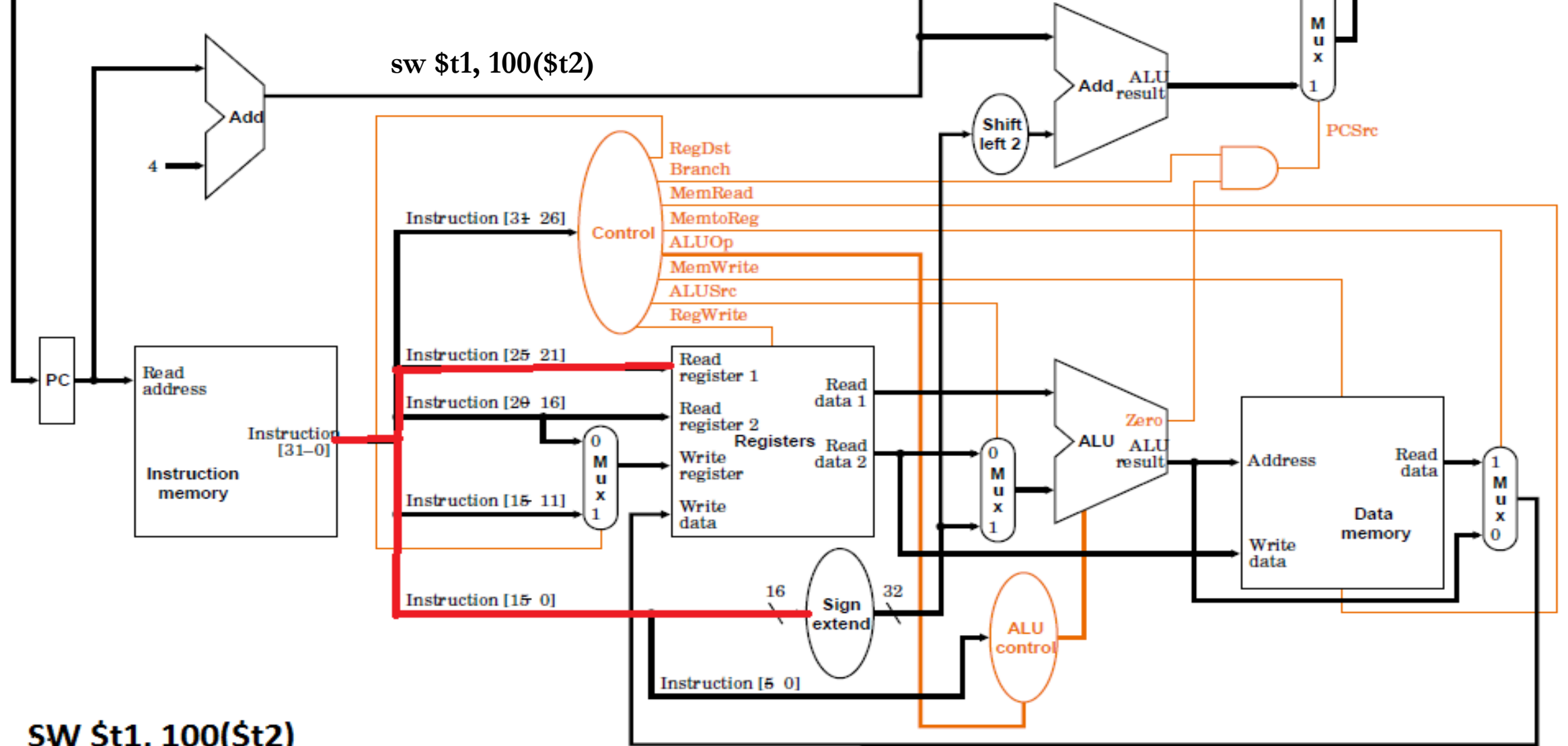


SW \$t1, 100(\$t2)

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`






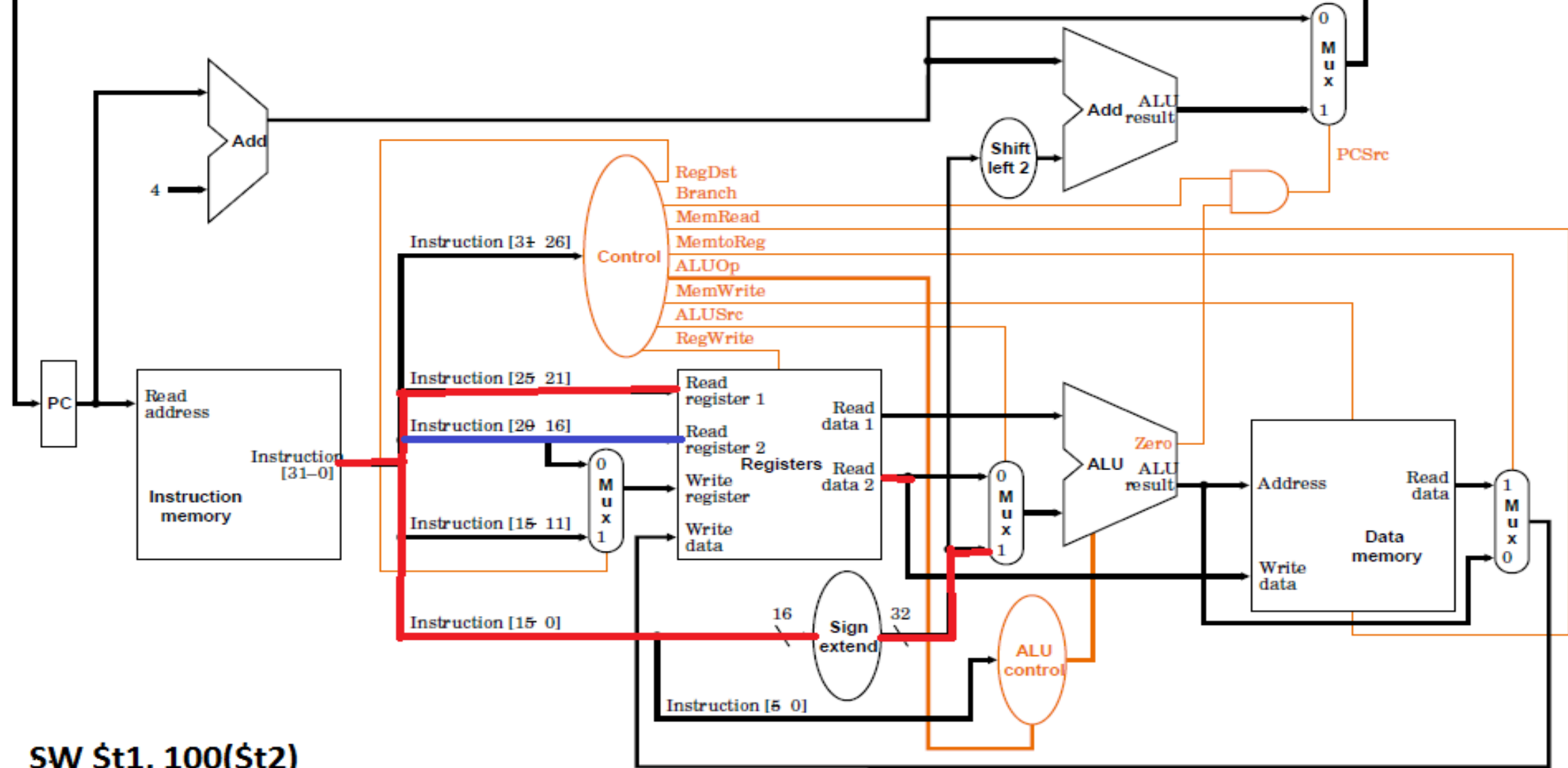


 **SW \$t1, 100(\$t2)**

Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`







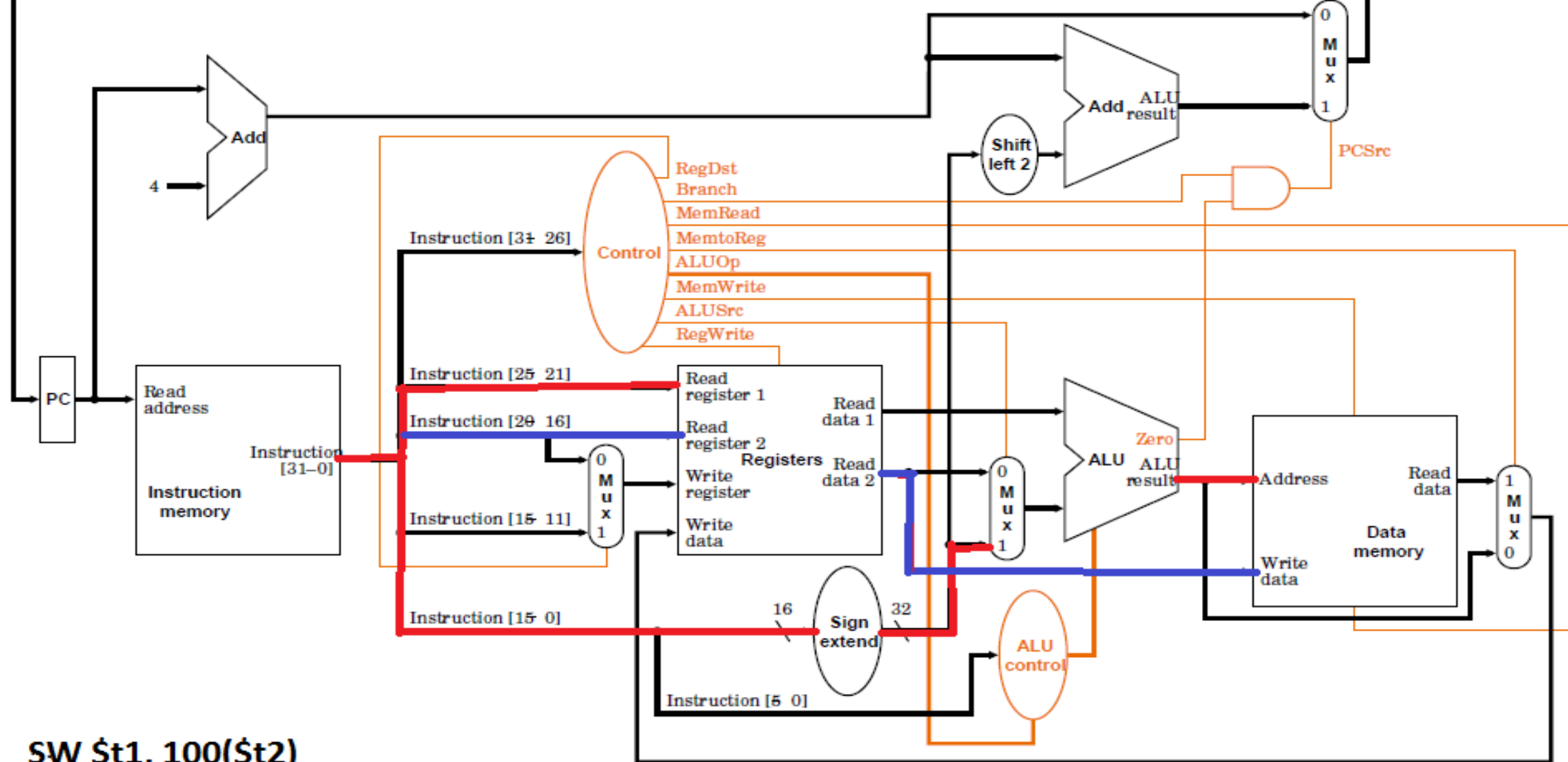

 **SW \$t1, 100(\$t2)**


Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



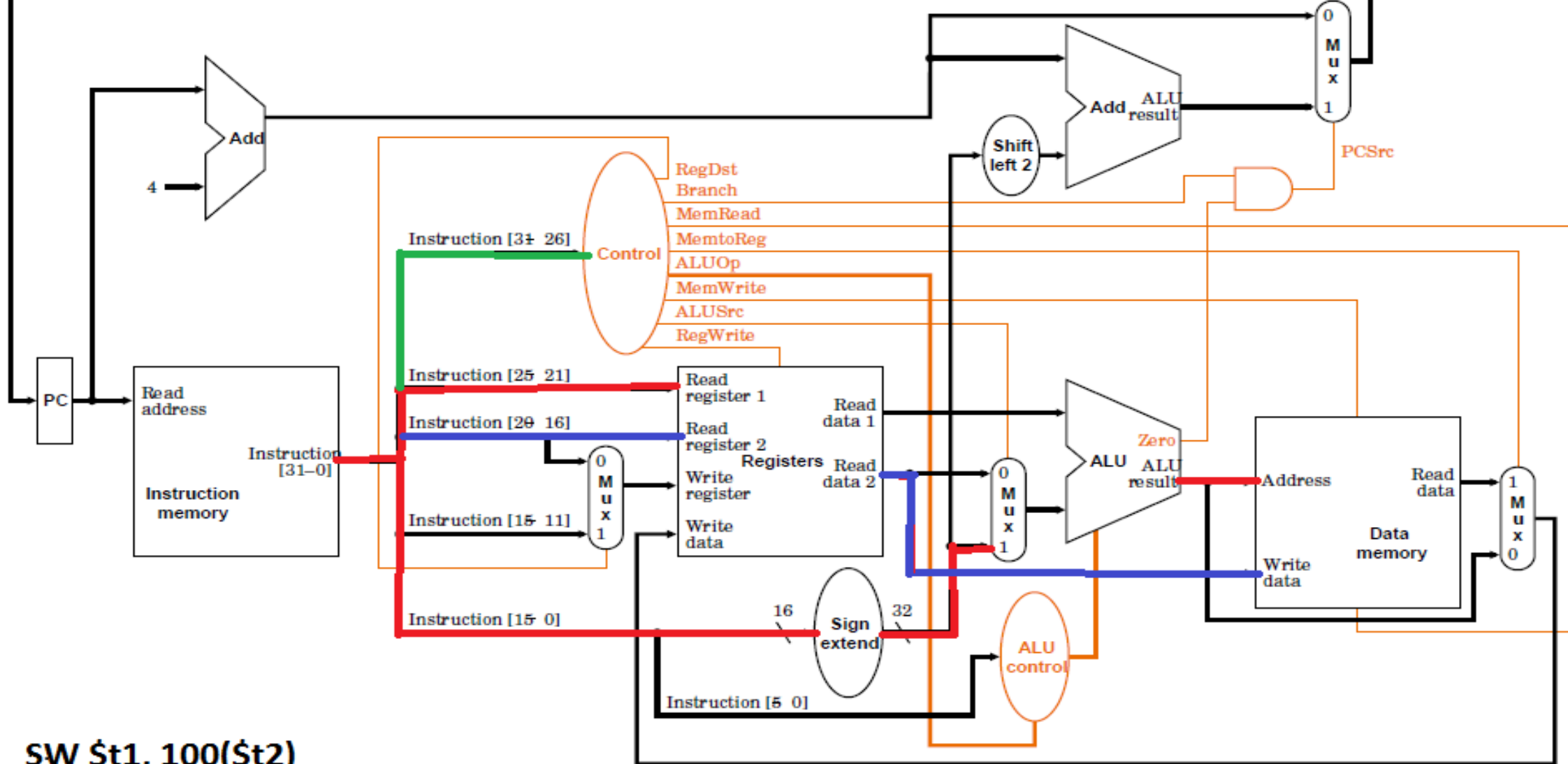


 **SW \$t1, 100(\$t2)**


Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



sw \$t1, 100(\$t2)

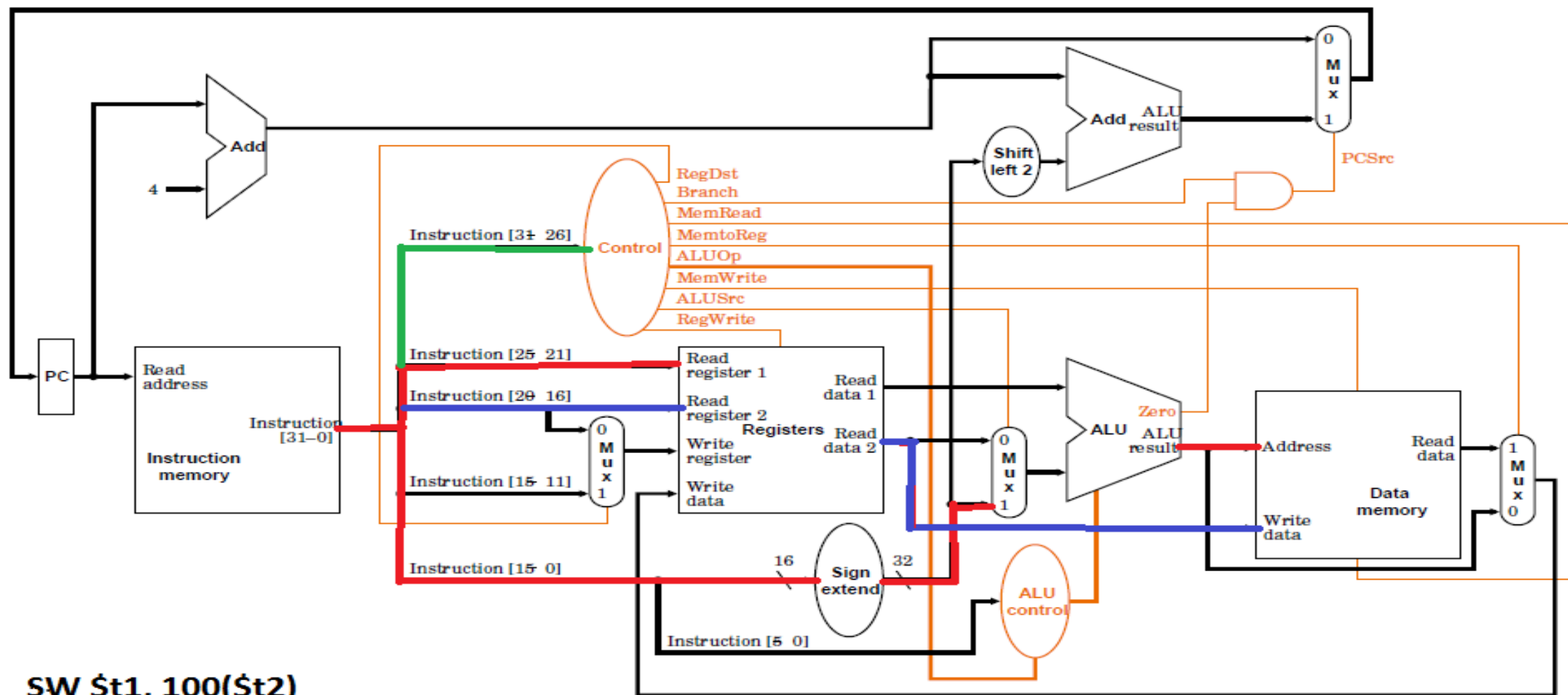

SW \$t1, 100(\$t2)

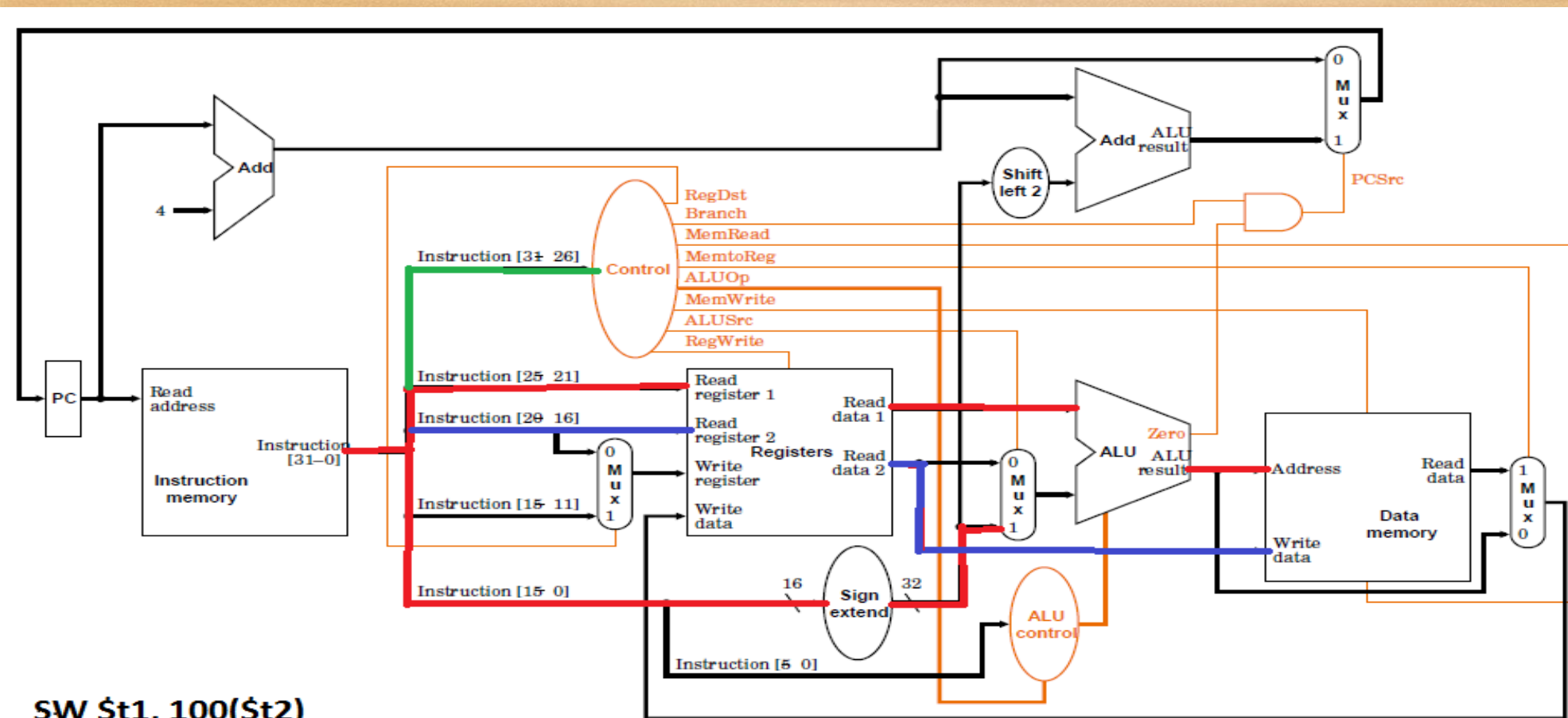


SW \$t1, 100(\$t2)

WHICH ONE OF THE FOLLOWING MUST BE TRUE TO COMPLETE SW instruction

- A) MemWrite = OFF (Low) , MemtoReg = 1
- B) ALUSrc = 1 RegDst = 1
- C) ALUSrc = 1 , MemWrite = 1
- D) MemtoReg = 1 , MemWrite = 1
- E) MemtoReg = X, ALUSrc = 0




## Full Datapath + Control Units

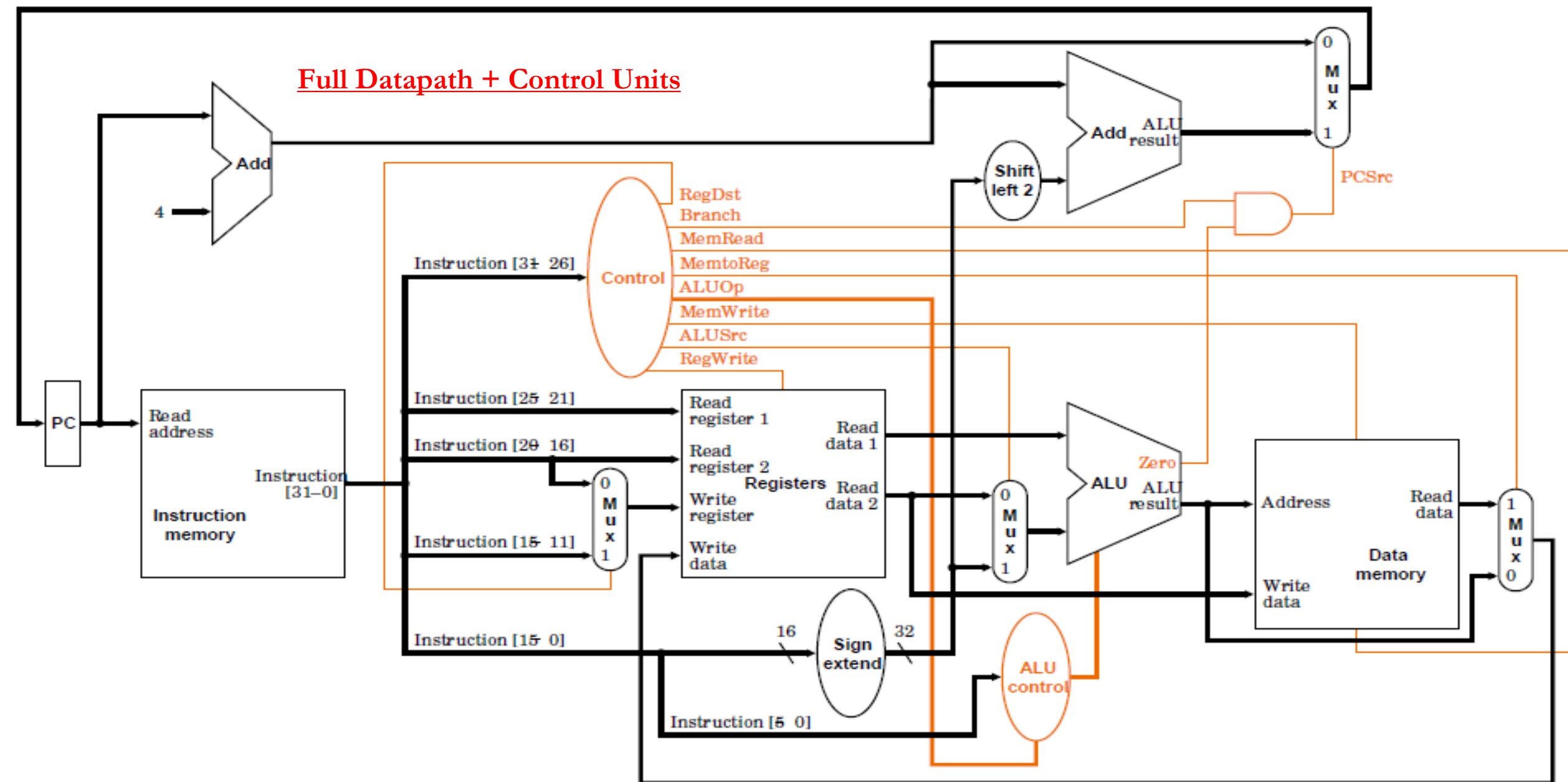

Mapping of operation to ALU control input:


Opcode	Operation	ALUOp	Funct	ALU action	ALU ctrl input
35	lw	00	XXXXXX	add	0010
43	sw	00	XXXXXX	add	0010
4	beq	01	XXXXXX	subtract	0110
0	add	10	100000	add	0010
0	sub	10	100010	subtract	0110
0	and	10	100100	AND	0000
0	or	10	100101	OR	0001
0	slt	10	101010	slt	0111

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	3210
0	0	X	X	X	X	X	X	0010
X(0)	1	X	X	X	X	X	X	0110
1	X(0)	X	X	0	0	0	0	0010
1	X(0)	X	X	0	0	1	0	0110
1	X(0)	X	X	0	1	0	0	0000
1	X(0)	X	X	0	1	0	1	0001
1	X(0)	X	X	1	0	1	0	0111

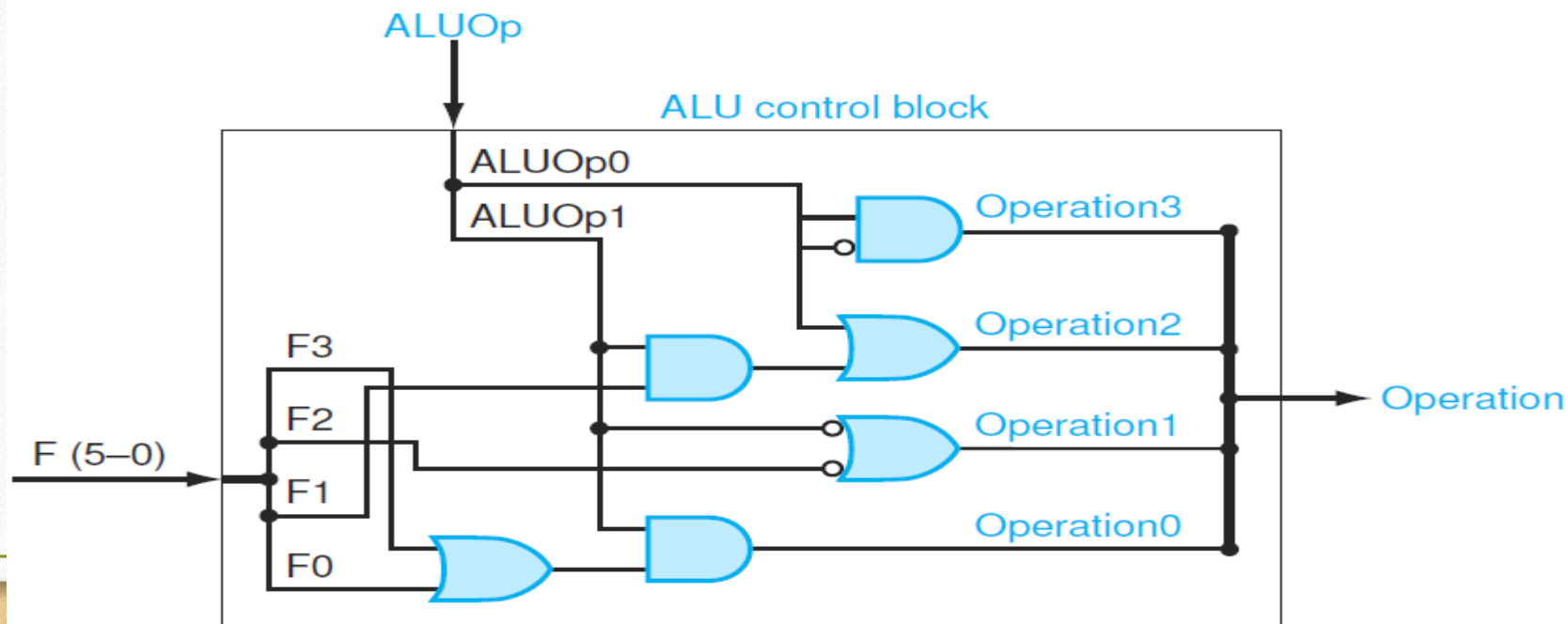

Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1


Type	Dec Opcode	Binary Opcode
R-format	0	000 000
lw	35	100 011
sw	43	101 011
beq	4	000 100

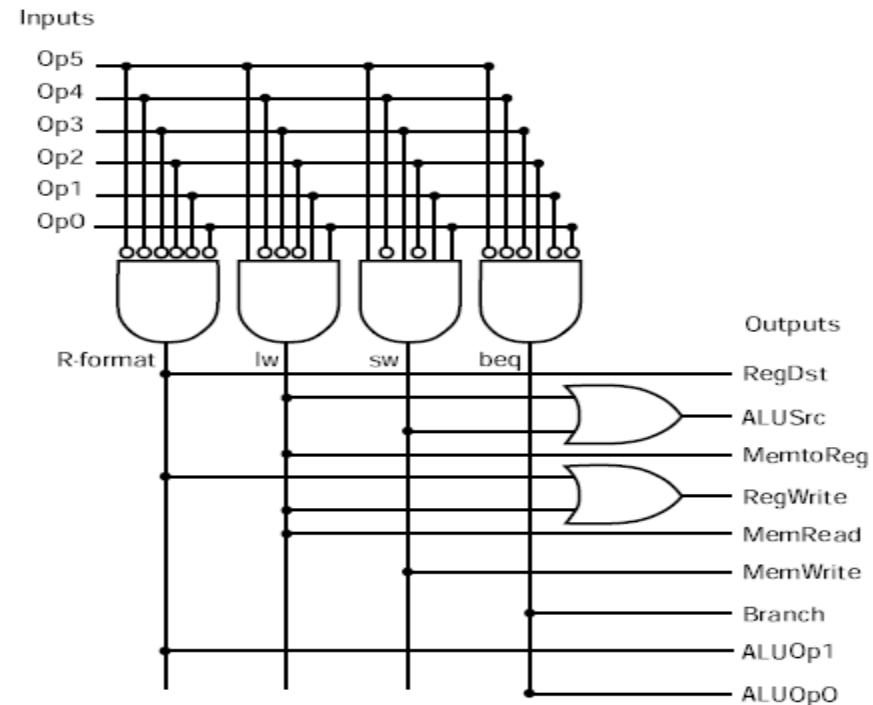

## slt \$d, \$a, \$b R-Format


Description:

Operation:

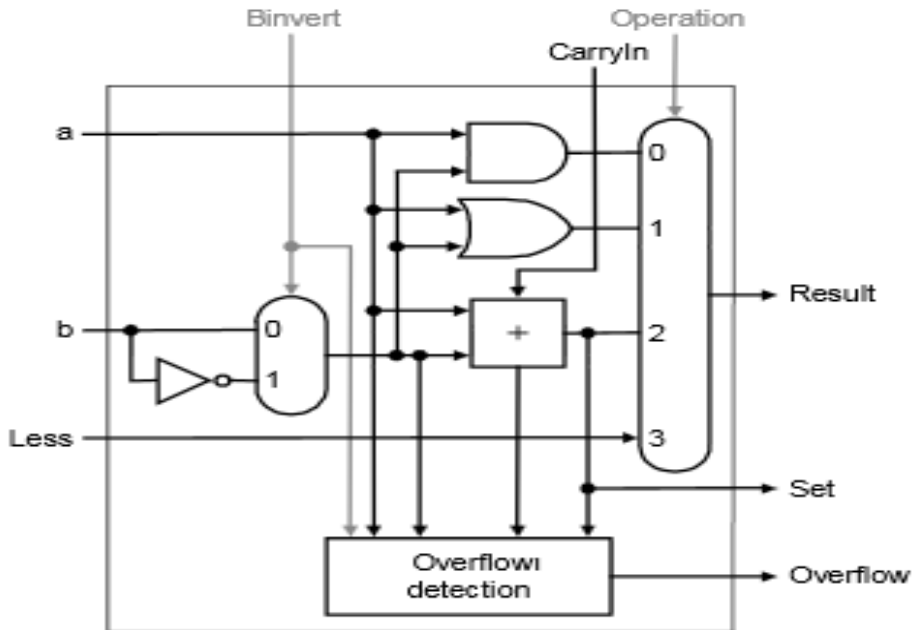



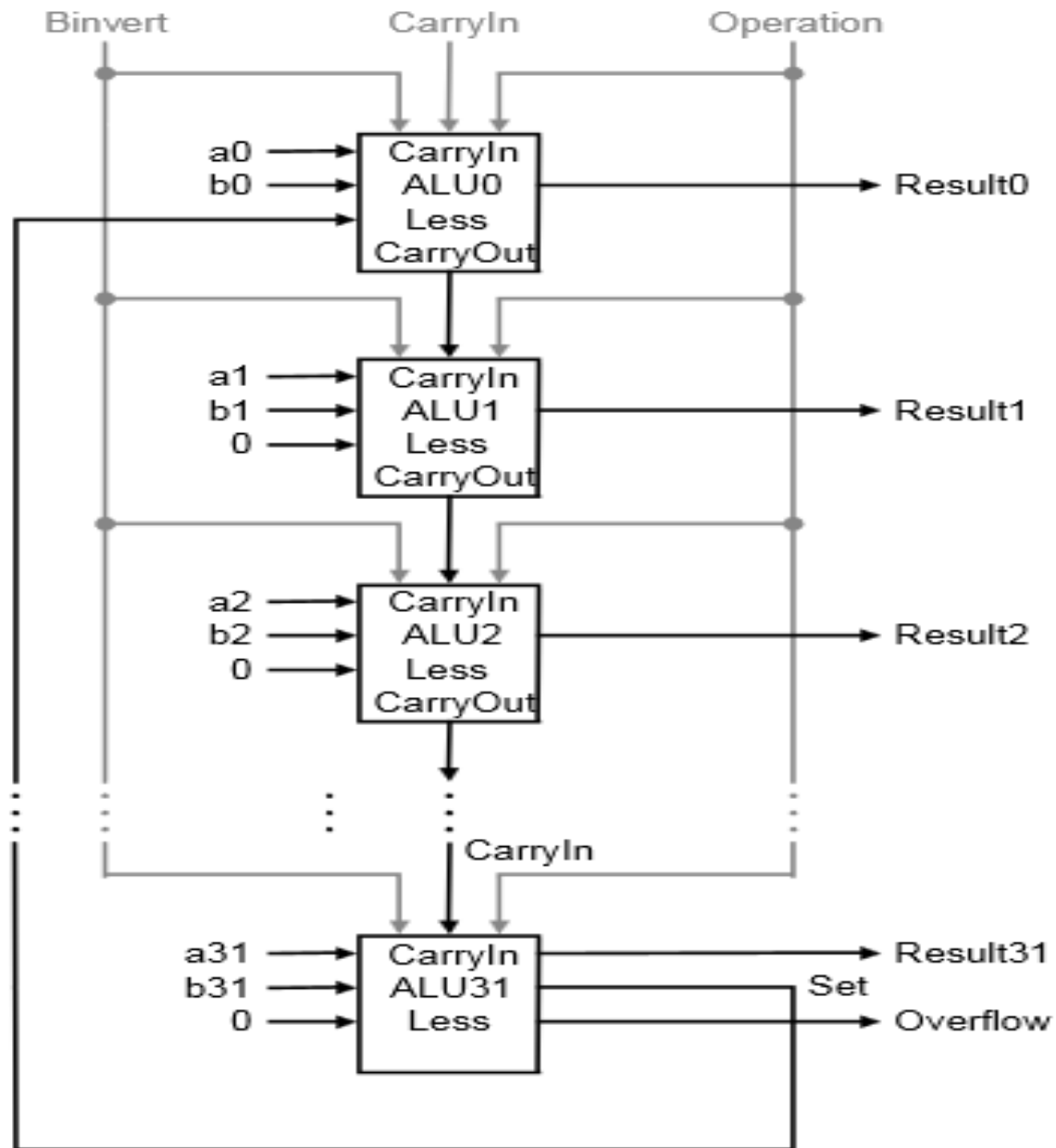- 
- Recall that a 32bit ALU is actually a series of 1-bit ALUs that are all
  - Performing the same operation.



## Hardware for SLT: Internal using ALU

Zero sent to every bit

Except first:

This is dependent on Sign of the difference  
Between a, and b.

IS  $a < b$ , if so  $a - b$ , and a is smaller

Answer will be negative

If  $a = -3$ ,  $b = -4$  answer will be positive


If  $a = -5$ ,  $b = -4$  answer will be negative also

We need to examine the very Last Bit


Is this big indicating a negative answer:

This bit is used to SET first bit of answer

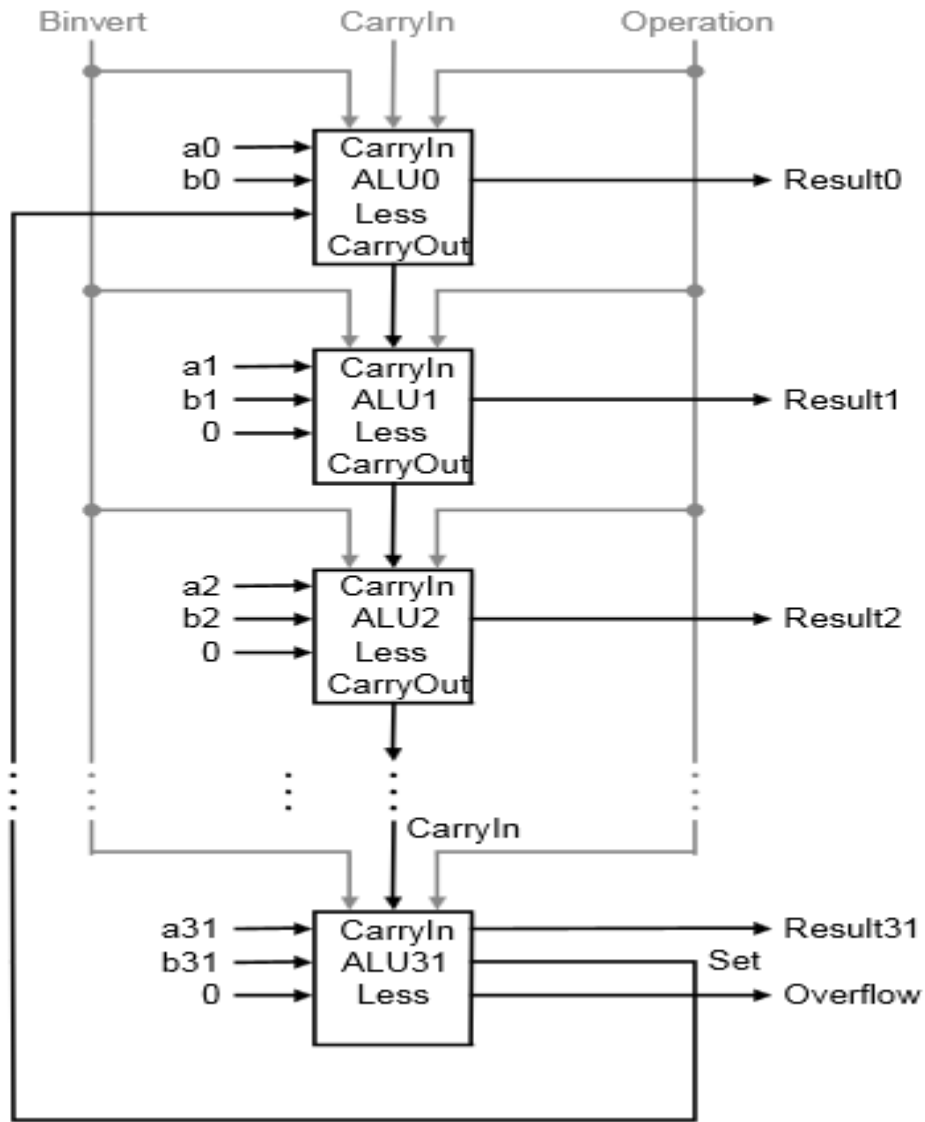
## Mapping of operation to ALU control input:



Opcode	Operation	ALUop	Funct	ALU action	ALU ctrl input
35	lw	00	XXXXXX	add	0010
43	sw	00	XXXXXX	add	0010
4	beq	01	XXXXXX	subtract	0110
0	add	10	100000	add	0010
0	sub	10	100010	subtract	0110
0	and	10	100100	AND	0000
0	or	10	100101	OR	0001
0	slt	10	101010	slt	0111

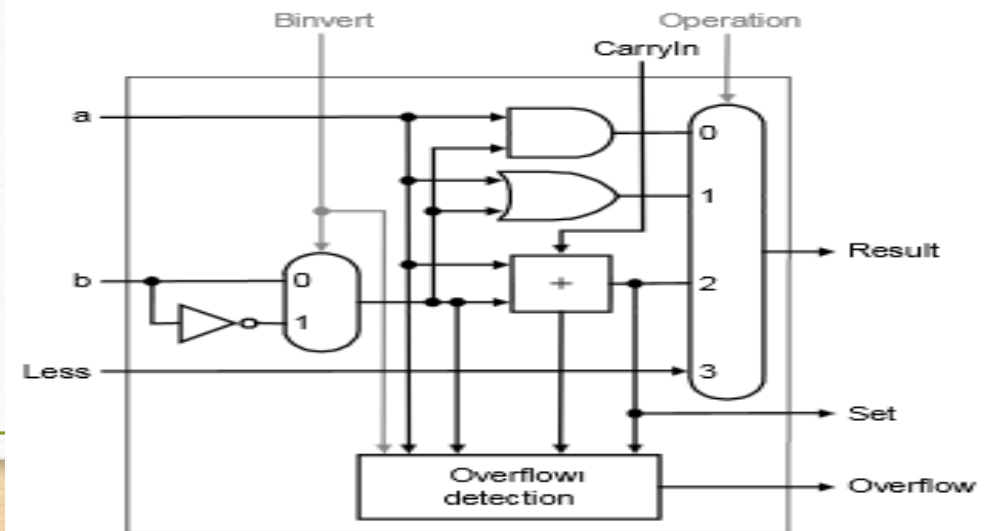

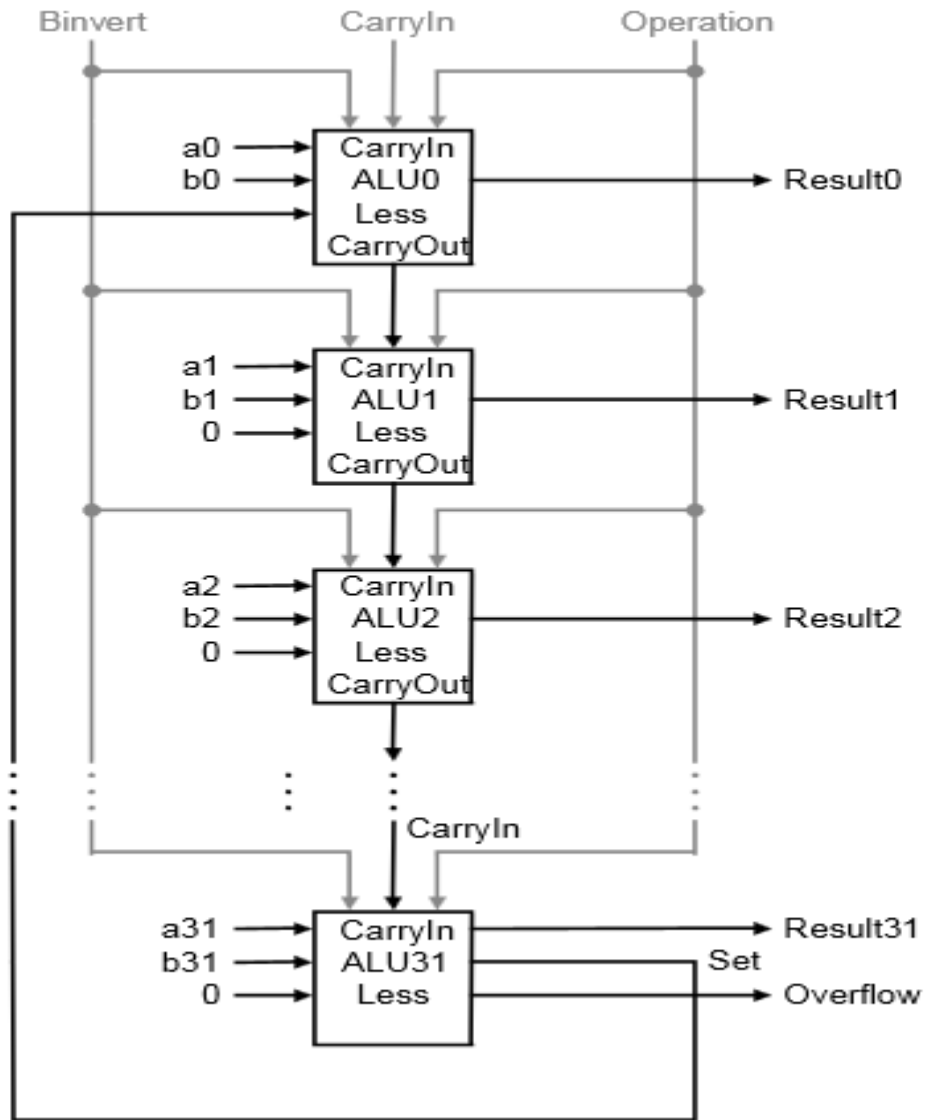
## Mapping of operation to ALU control input:




Internally  
B-invert  
Would be tied to the  
First Carry-In

Opcode	Operation	ALUop	Funct	ALU action	ALU ctrl input
35	lw	00	XXXXXX	add	0010
43	sw	00	XXXXXX	add	0010
4	beq	01	XXXXXX	subtract	0110
0	add	10	100000	add	0010
0	sub	10	100010	subtract	0110
0	and	10	100100	AND	0000
0	or	10	100101	OR	0001
0	slt	10	101010	slt	0111

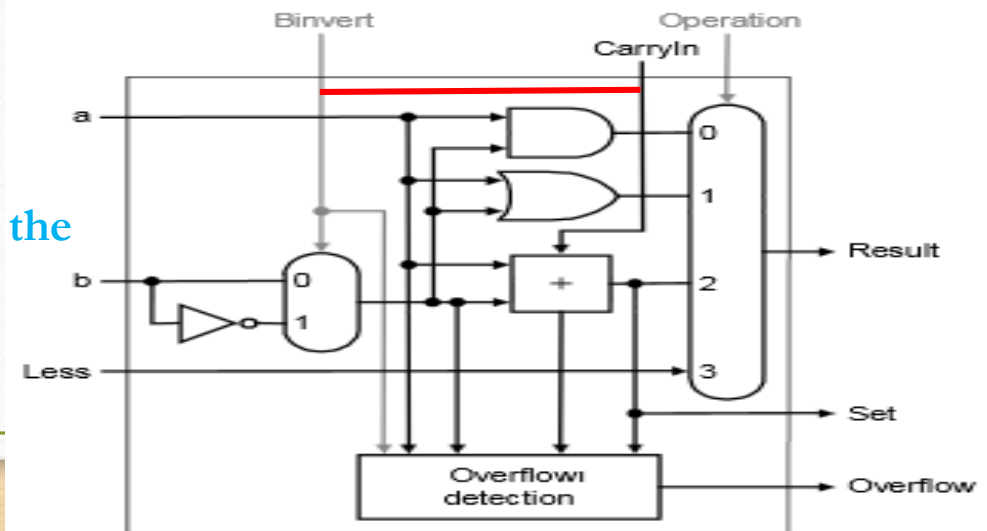



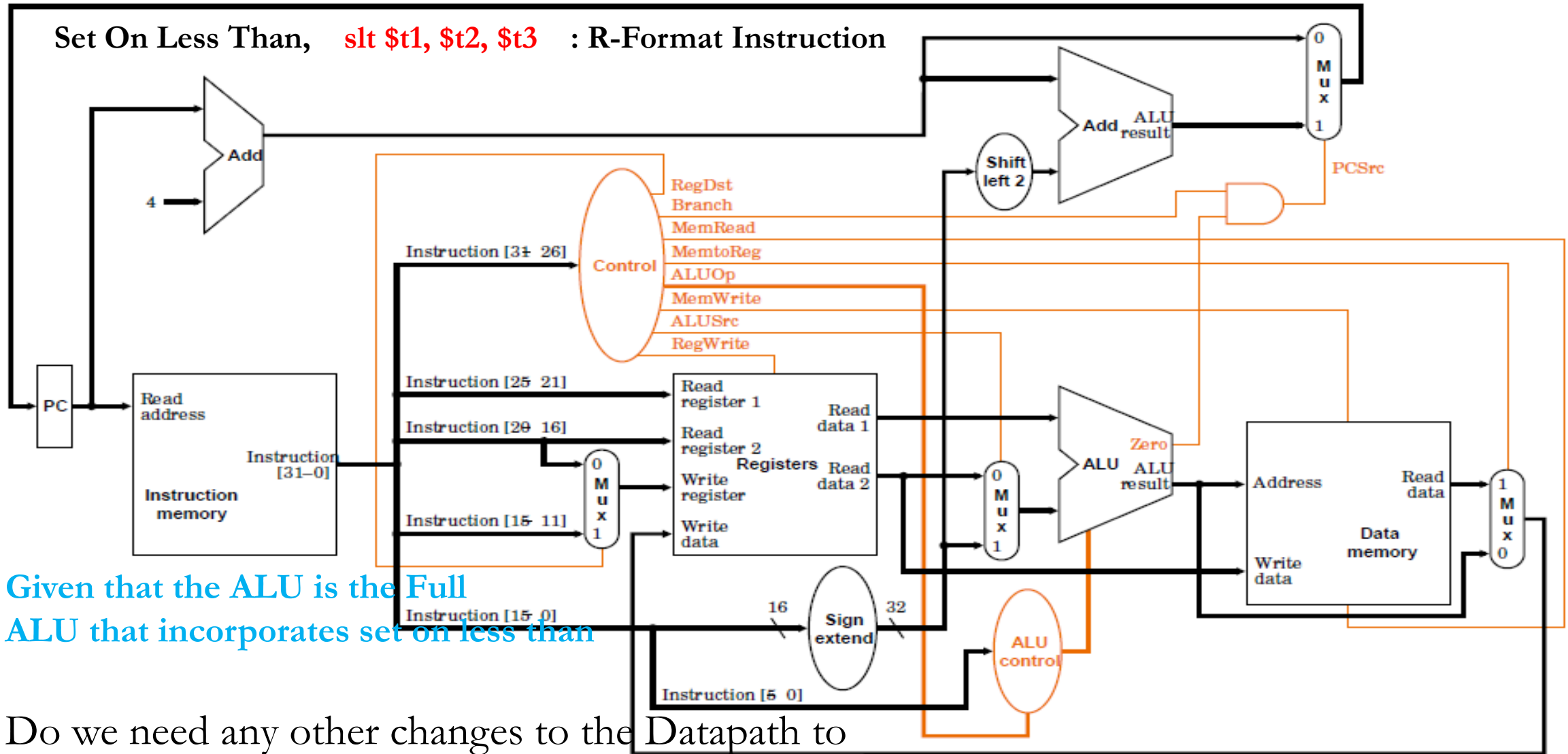
Set On Less Than, **slt \$t1, \$t2, \$t3** : R-Format Instruction



Given that the ALU is the Full ALU that incorporates set on less than

Do we need any other changes to the Datapath to Perform the slt instruction:

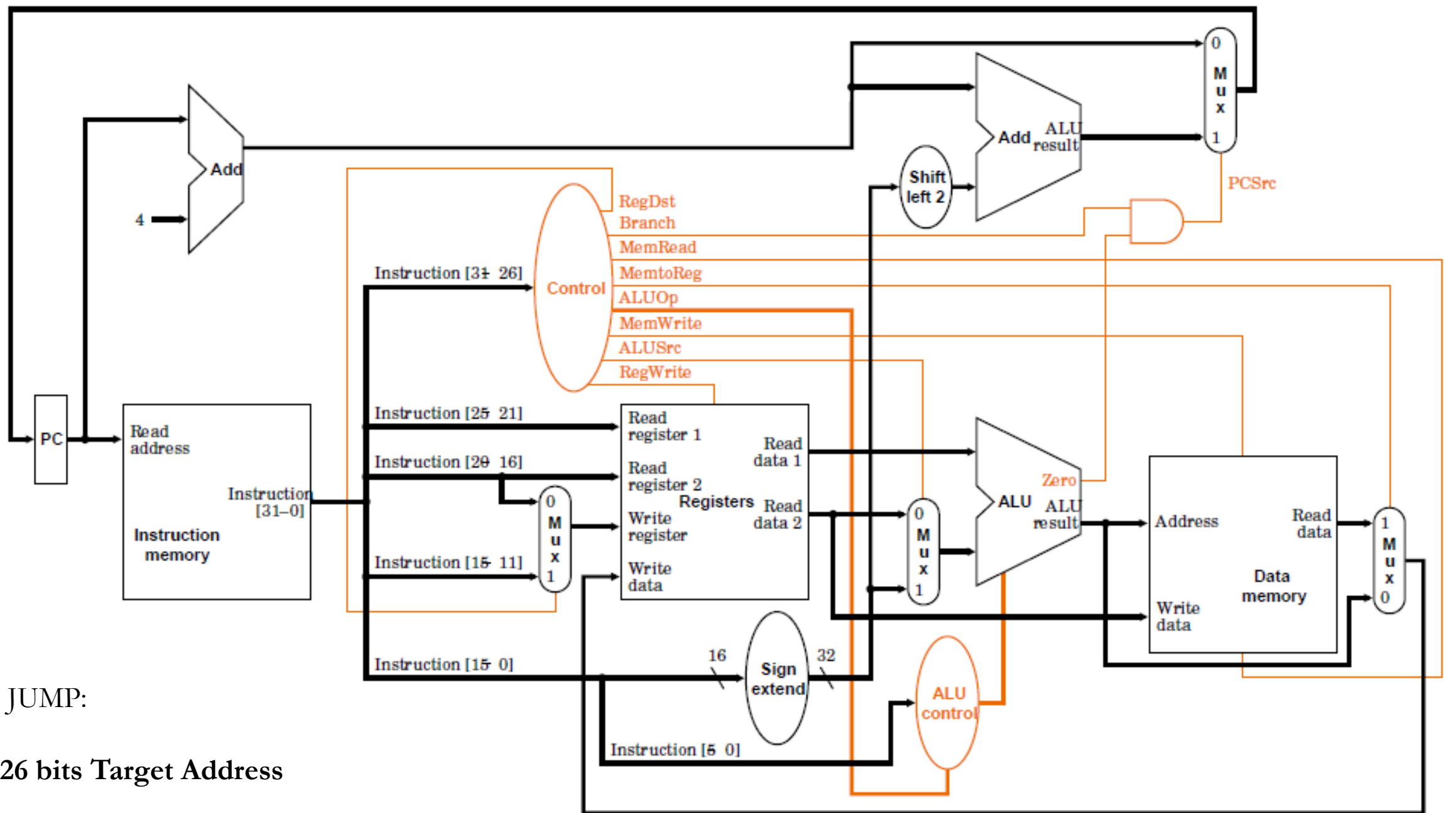- A) Yes : need to be able to WRITE to the Destination Register \$t1
- B) NO, Datapath has everything it needs
- C) Yes: need to be able to compare two registers, \$t2 and \$t3




JUMP:

26 bits Target Address

 
# How the Instruction Bits are Broken up:

R-format: `add $t1, $t2, $t3`  $\Rightarrow$  `add rd, rs, rt`



sll, sub

 Load/store: `lw $t1, 100($t2)`  $\Rightarrow$  `lw rt, 100(rs)`




beq, subi, addi

Jump: `j 3000`




special

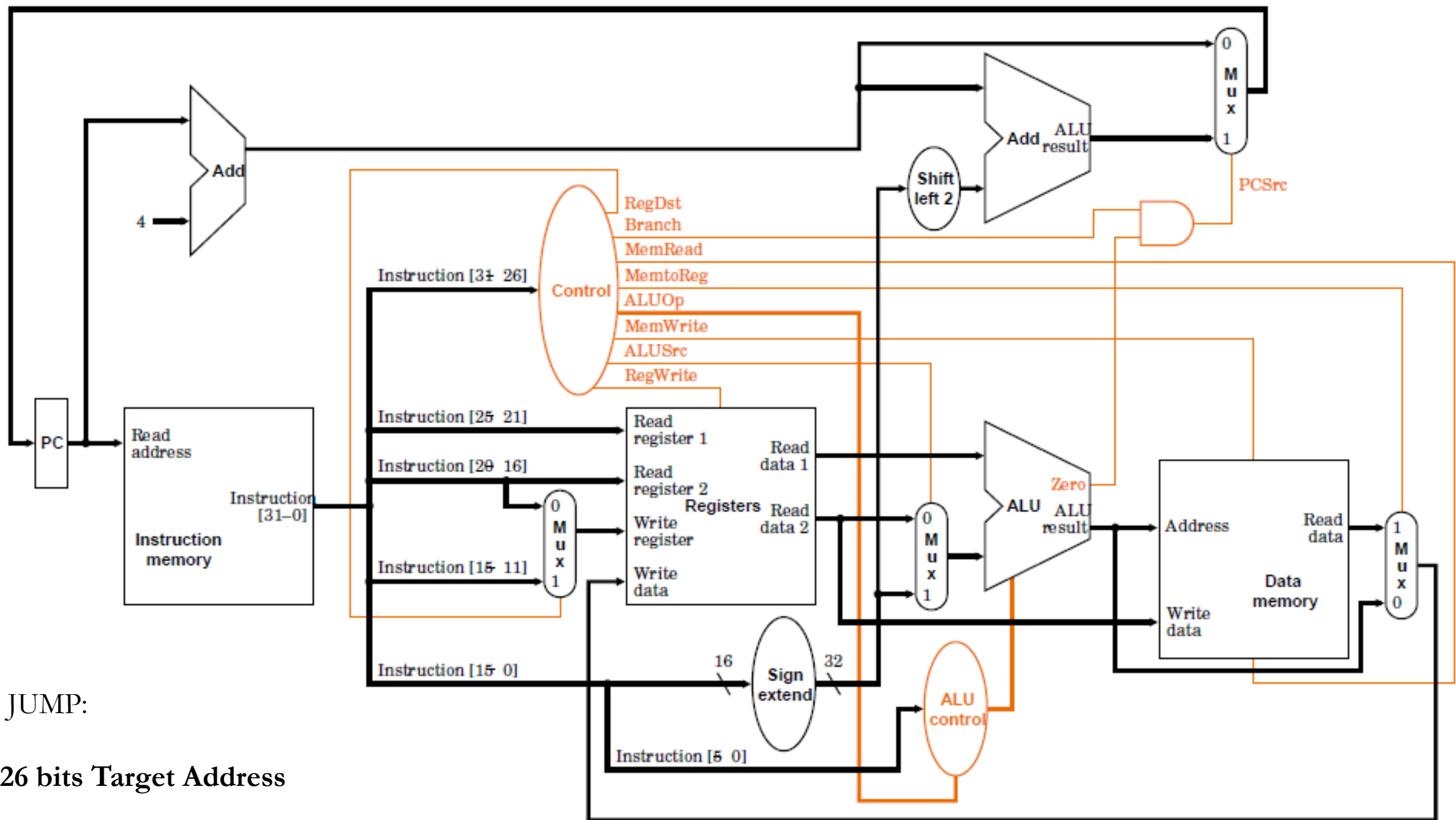


JUMP:

26 bits Target Address



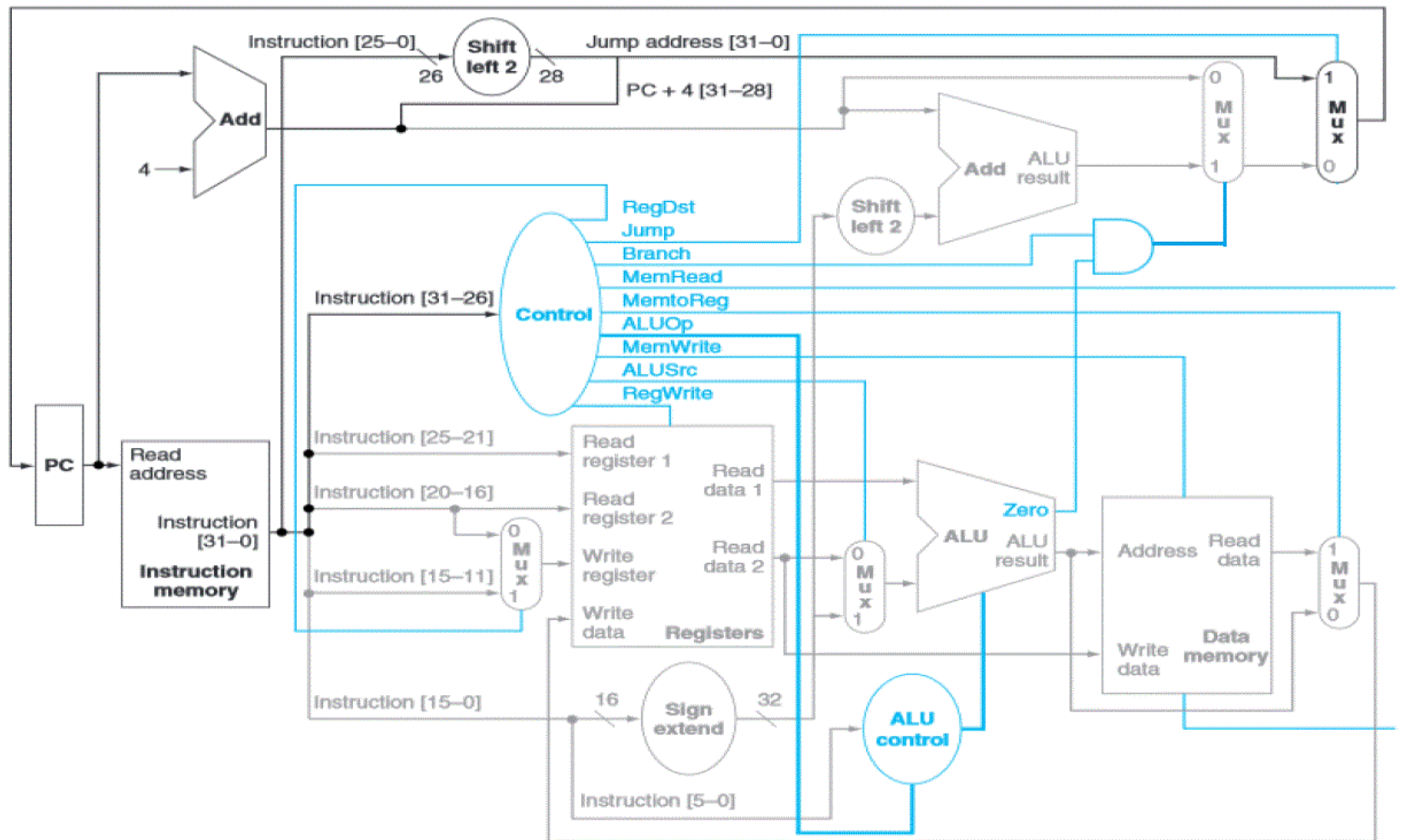



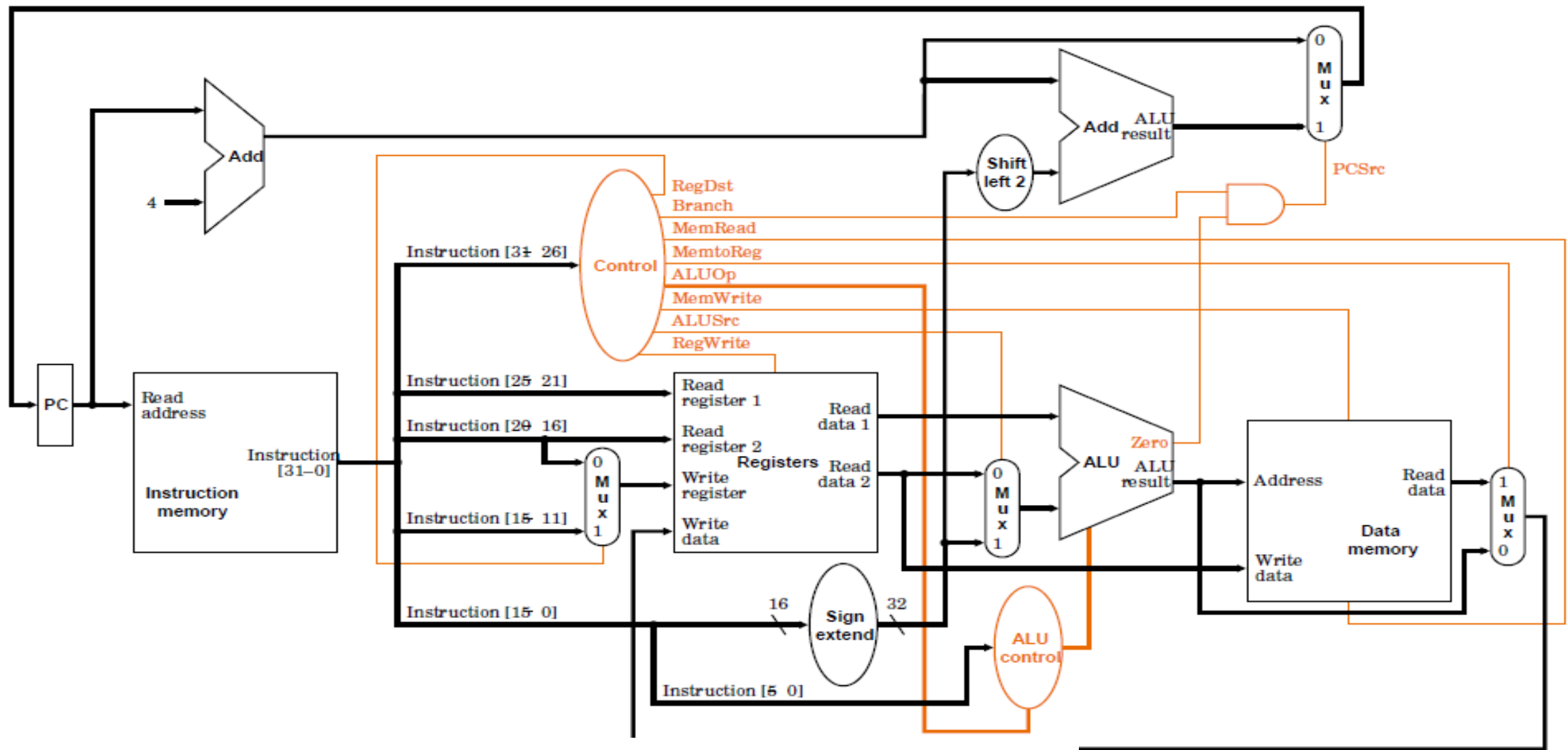

- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units


How Long Does JUMP TAKE? :

- 
- Jump: Read from Instruction memory
  - Shift Left x2 : Minimal Time
  - Write to PC: Minimal Time




- 
- Jump: Read from Instruction memory (200ps)
  - Shift Left x2 : Minimal Time (0)
  - Write to PC: Minimal Time (0)
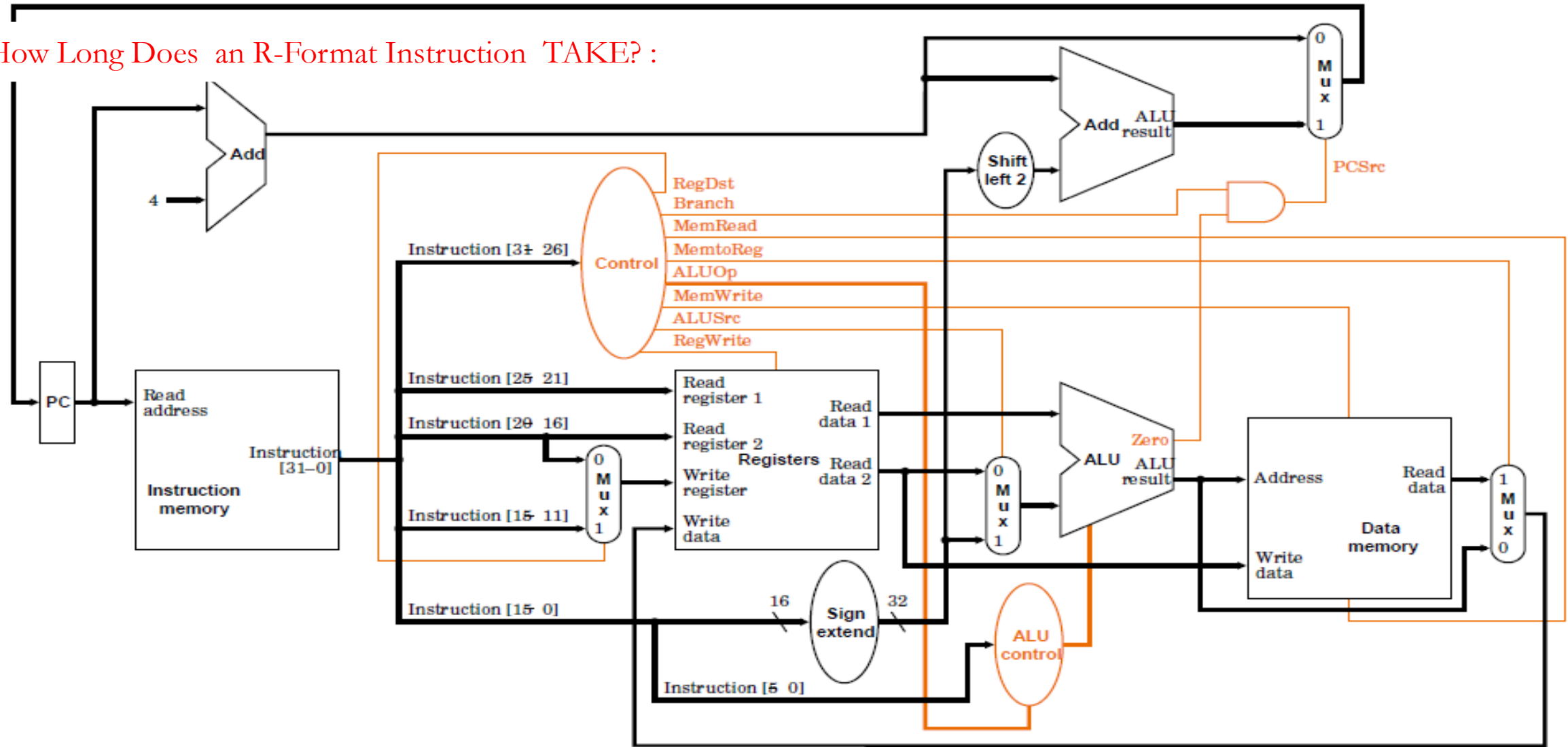
## How Long Does an R-Format Instruction TAKE? :




- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units

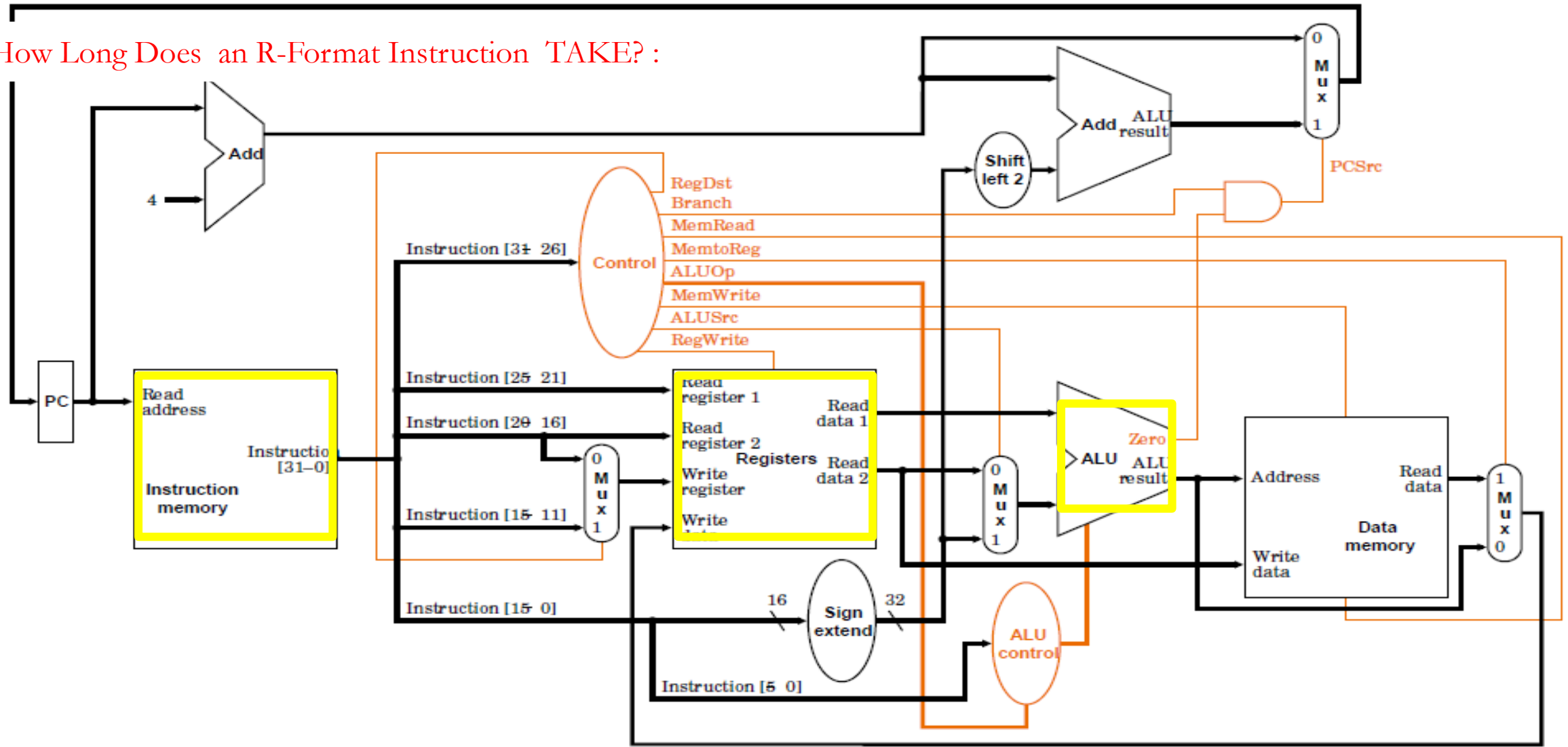How Long Does an R-Format Instruction TAKE? :



- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units

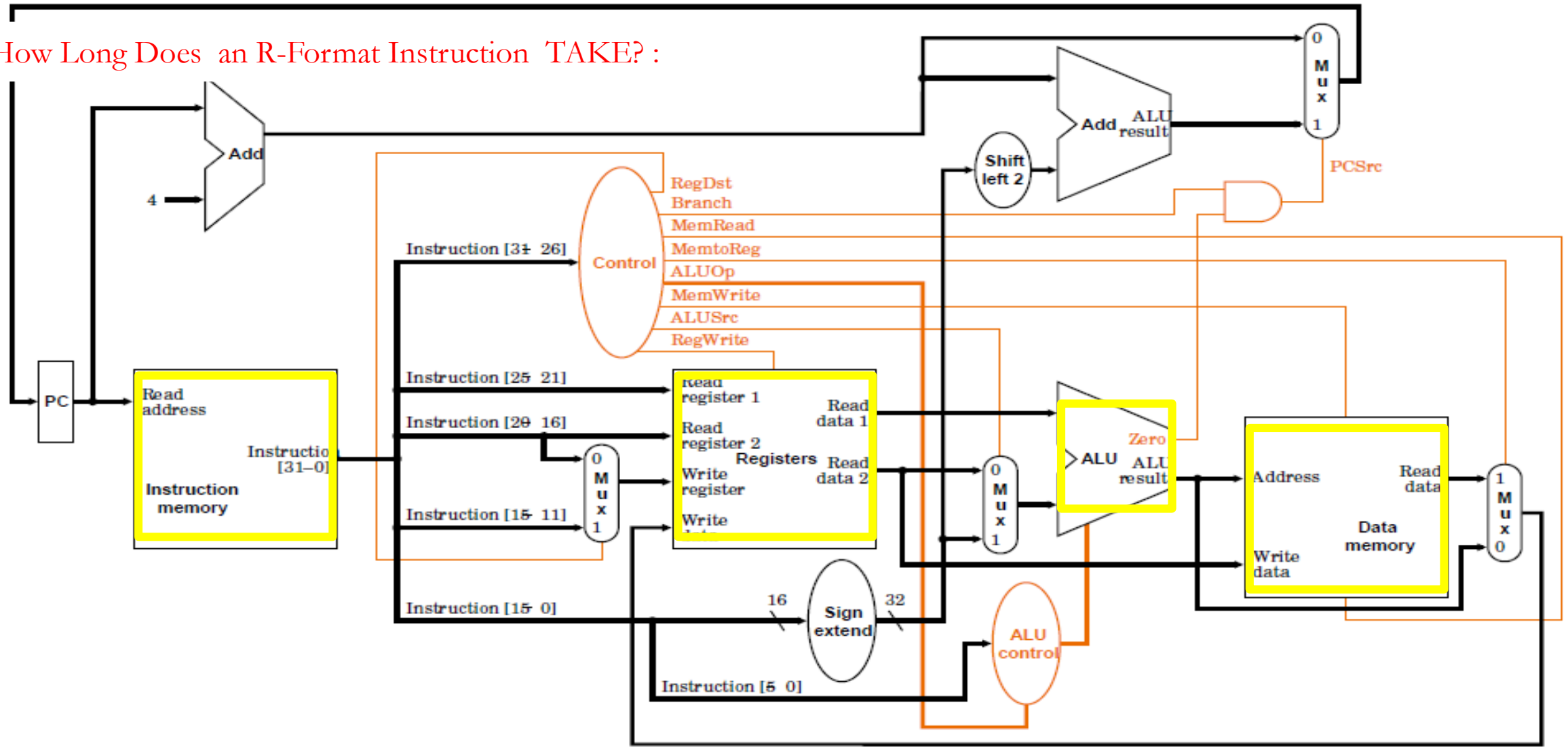
How Long Does an R-Format Instruction TAKE? :



- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units




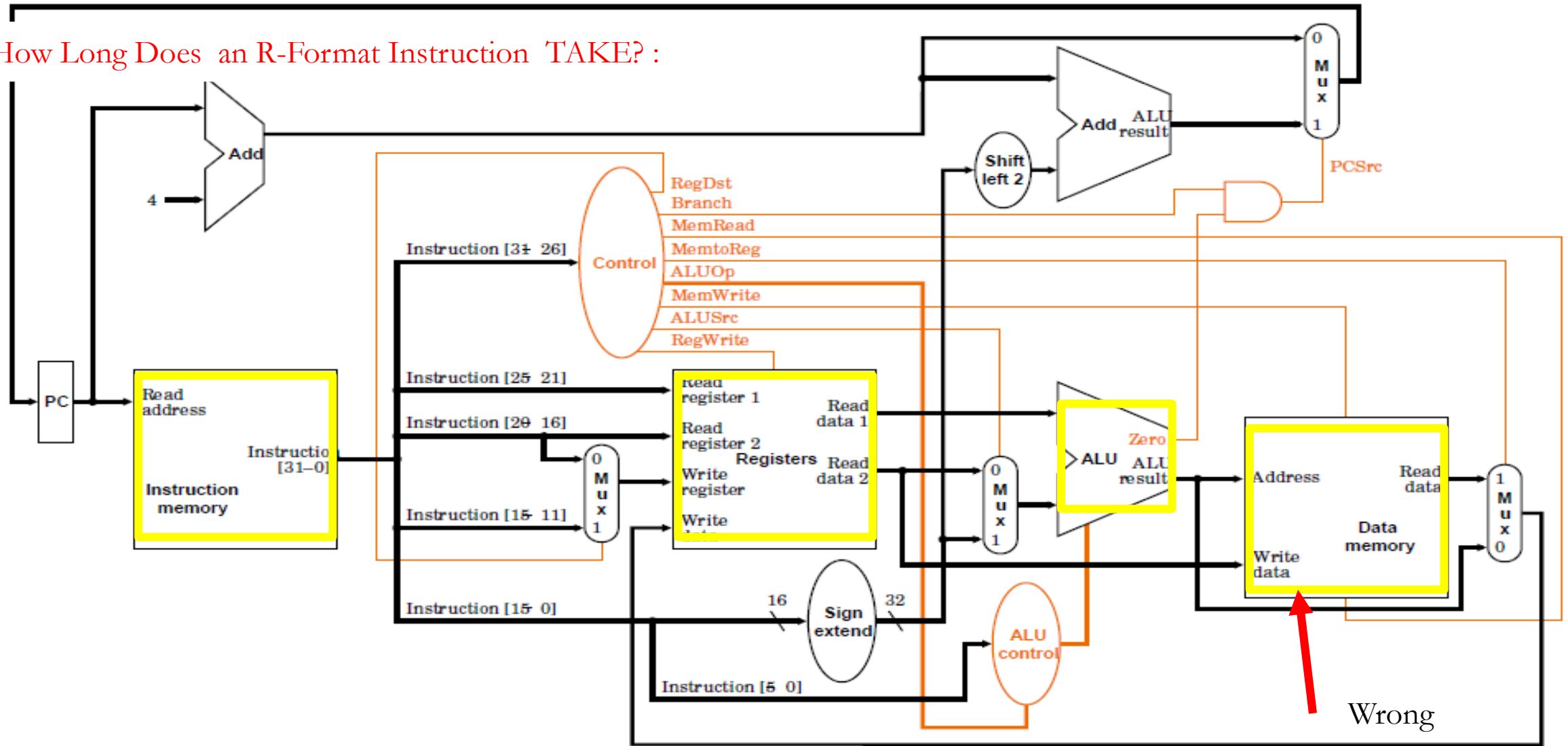How Long Does an R-Format Instruction TAKE? :



- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units

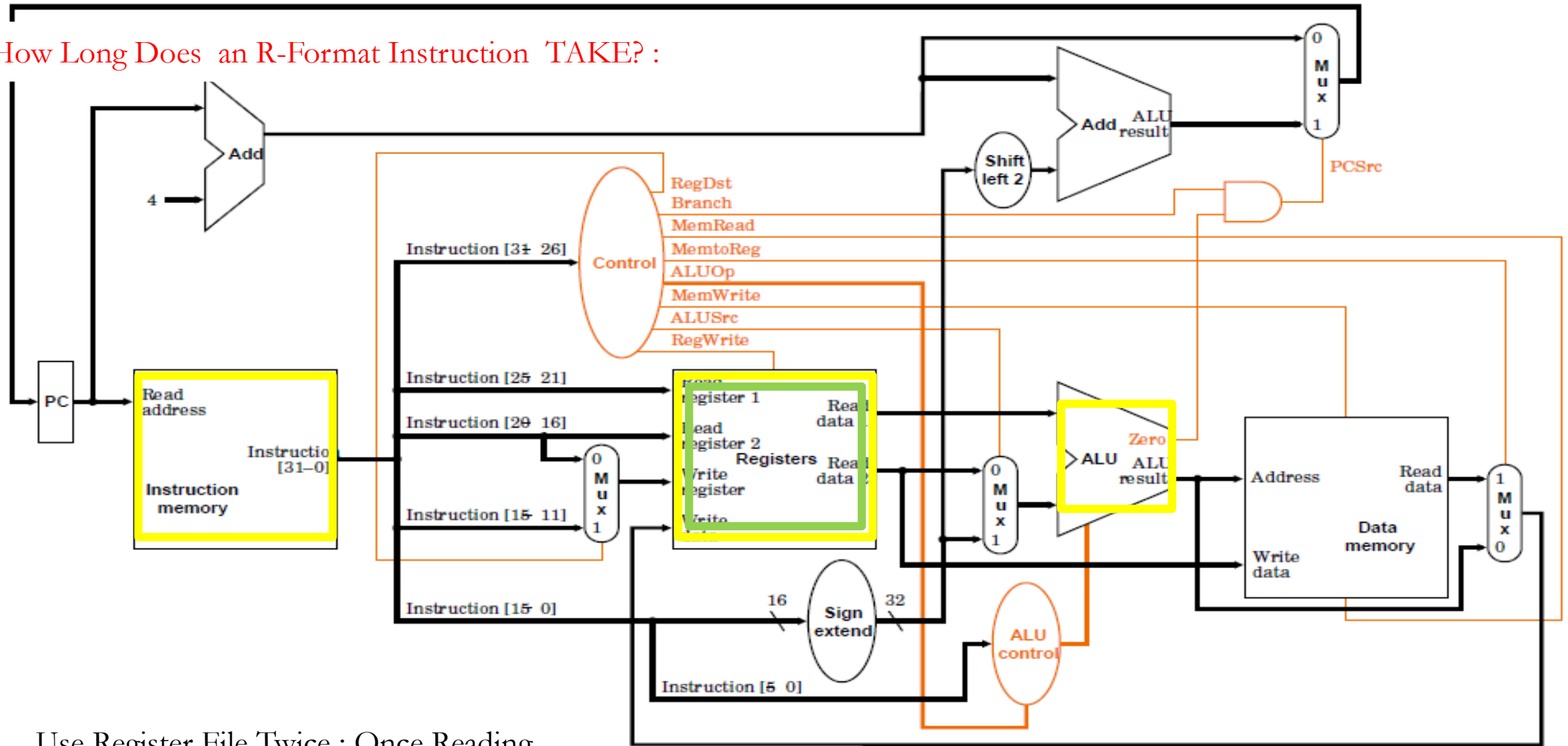
## How Long Does an R-Format Instruction TAKE? :



Use Register File Twice : Once Reading  
Once Writing

- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units

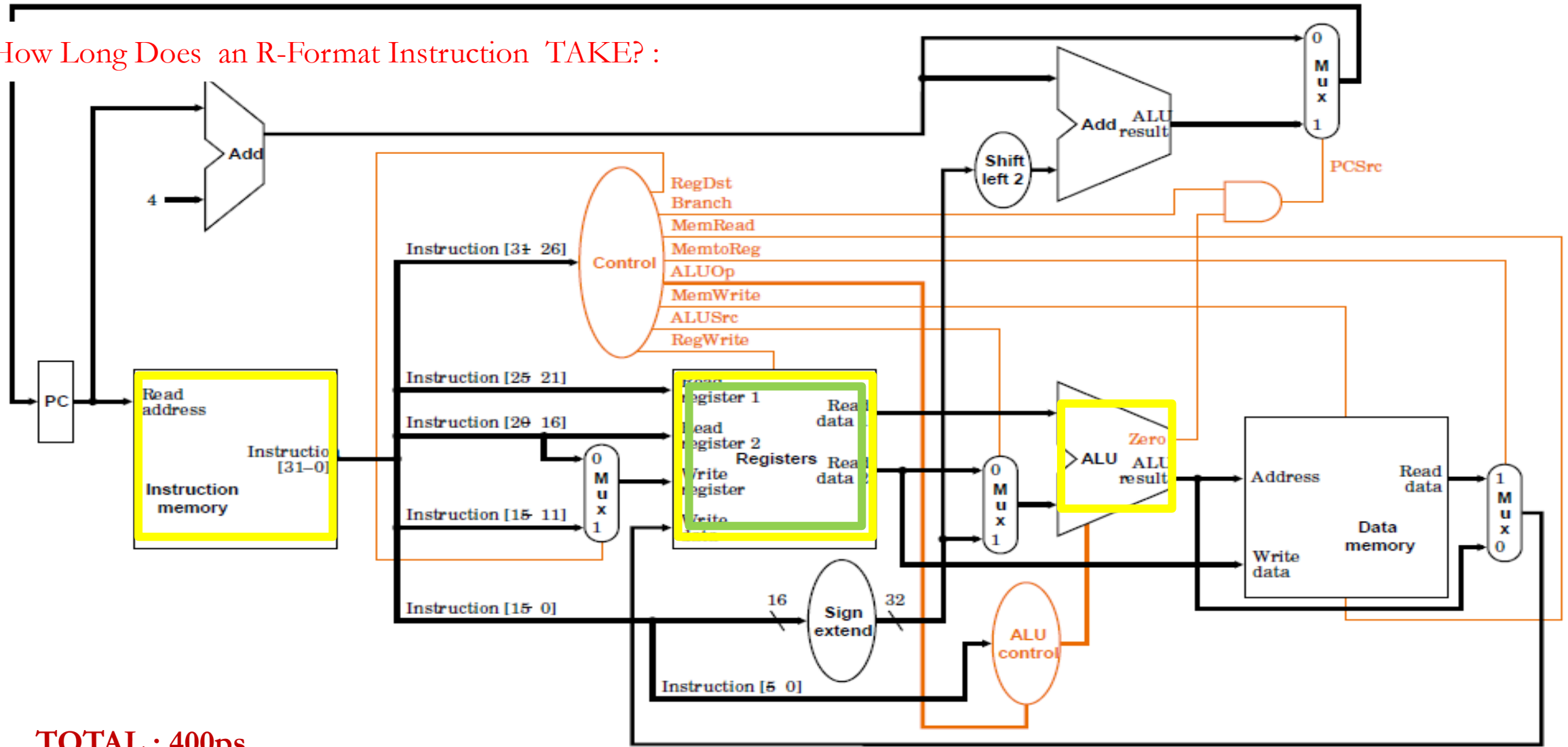How Long Does an R-Format Instruction TAKE? :



**TOTAL : 400ps**

- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units

## Performance of Single Cycle Machines

- Suppose memory units take 200 ps (picoseconds), ALUs 100 ps, register files 50 ps, no delay on other units
- Jumps take 200 ps, branches take 350 ps, R-format instructions 400 ps, stores 550 ps, loads 600 ps.
- Clock period must be increased to 600 ps or more
- Even worse when floating-point instructions are implemented
- Idea: use multicycle implementation and R format




## Modifying the datapath

- Normally design complete datapath for all instructions together.
- Various ways to modify datapath. The following is one approach for adding a new assembly instruction:
  1. Determine what datapath is needed for new command
  2. Check if any components in current datapath can be used
  3. Wire in components of new datapath into existing datapath  
Probably requires MUXes
  4. Add new control signals to Control units
  5. Adjust old control signals to account for new command

- Add jrel \$ra which performs  

$$PC \leftarrow PC + 4 + 4 * \$ra$$

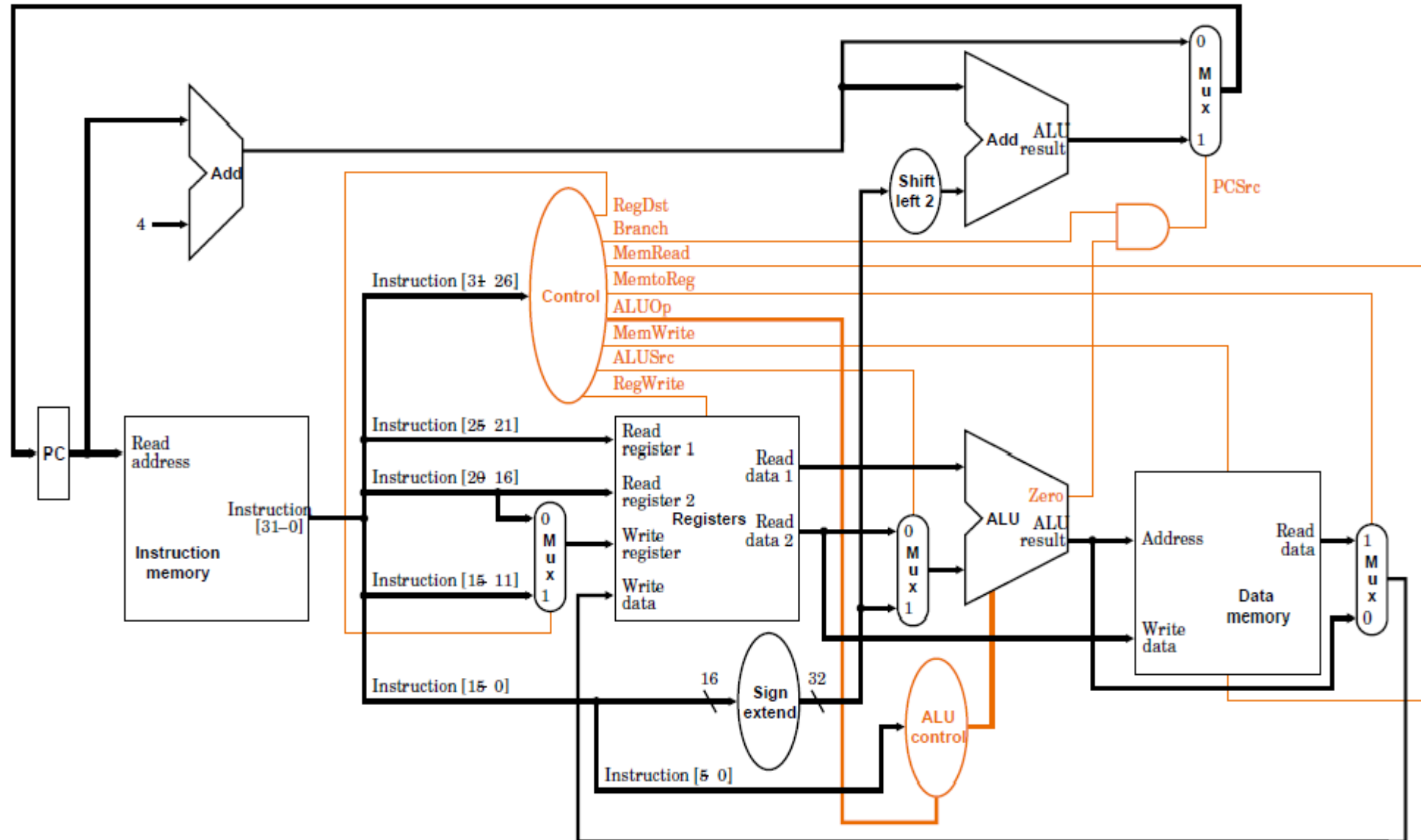

- Add jrel \$ra which performs  

$$PC \leftarrow PC + 4 + 4 * \$ra$$

Note : \$ra is the \$rs Register

