

Single Cycle Architecture

Part 2

Office hours : this week


- A) Today 1-2pm my office
- B) Wed: 1-2:30
- C) Thursday 1:30-2:30
- Check Piazza for Sean's Office Hours Also and midterm related info

What Statement about memory in the Datapath is NOT true ☺

 - A) the instruction and data memory are a type of RAM
- B) Data memory can be read from and written to
- C) The Registers contain memory in flip flops
- D) The Register file allows reading and writing to the registers
- E) The Instruction memory in the datapath allows reading of instructions and writing new instructions


How the Instruction Bits are Broken up:

R-format: `add $t1, $t2, $t3` \Rightarrow `add rd, rs, rt`



sll, sub

 Load/store: `lw $t1, 100($t2)` \Rightarrow `lw rt, 100(rs)`




beq, subi, addi

Jump: `j 3000`



special

lw \$t1, 100(\$t2)

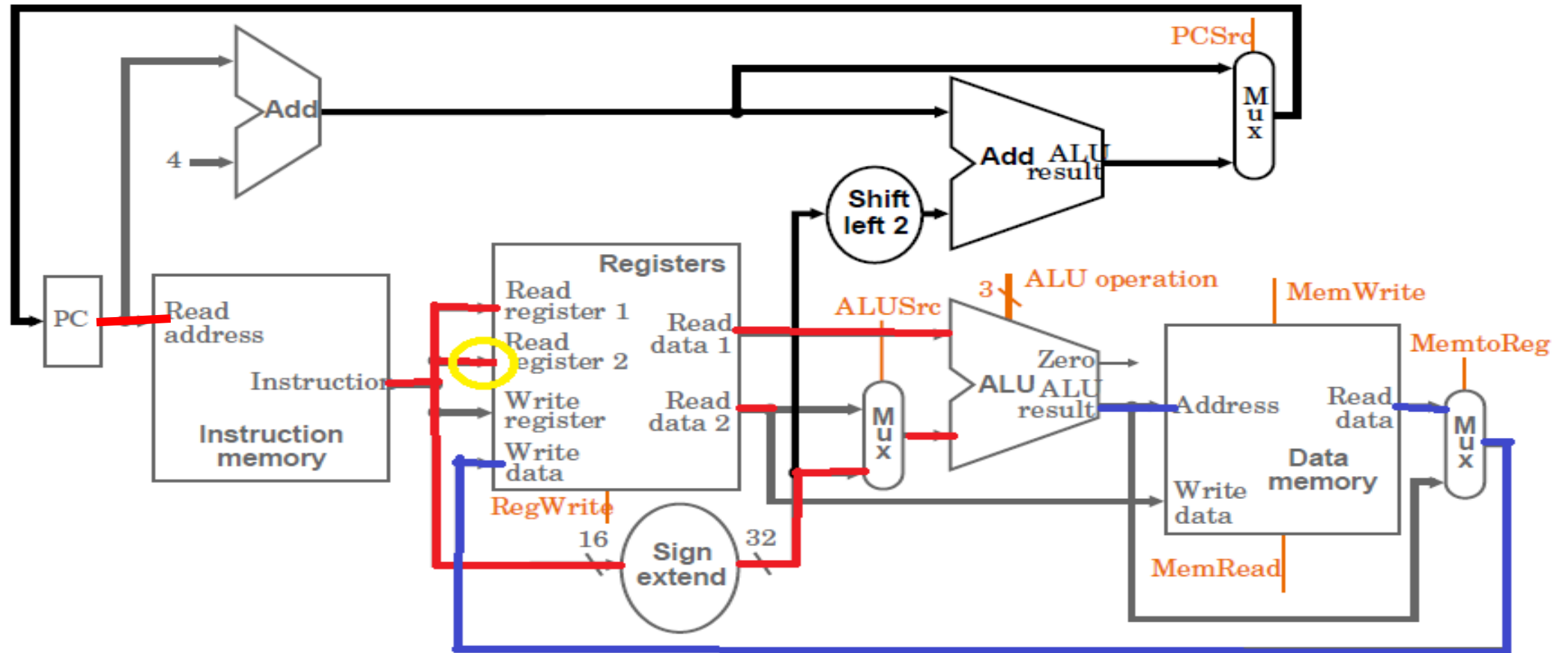


Once we access data memory → we now have 32 bits of data


* this data needs to be written to destination register (rt)

* therefore send data back to register file

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



lw \$t1, 100(\$t2)

 


We need **rt** to be the Write Register

Need more hardware here : to connect **rt** as also an option for a write register

Load/store: `lw $t1, 100($t2) \Rightarrow lw rt, 100(rs)`


31	26 25	21 20	16 15	0
35/43	rs	rt	offset	
6 bits	5 bits	5 bits	16 bits	


Add in a Multiplexor

 

lw rs rt offset

 
Load/store: lw \$t1, 100(\$t2) \Rightarrow lw rt, 100(rs)




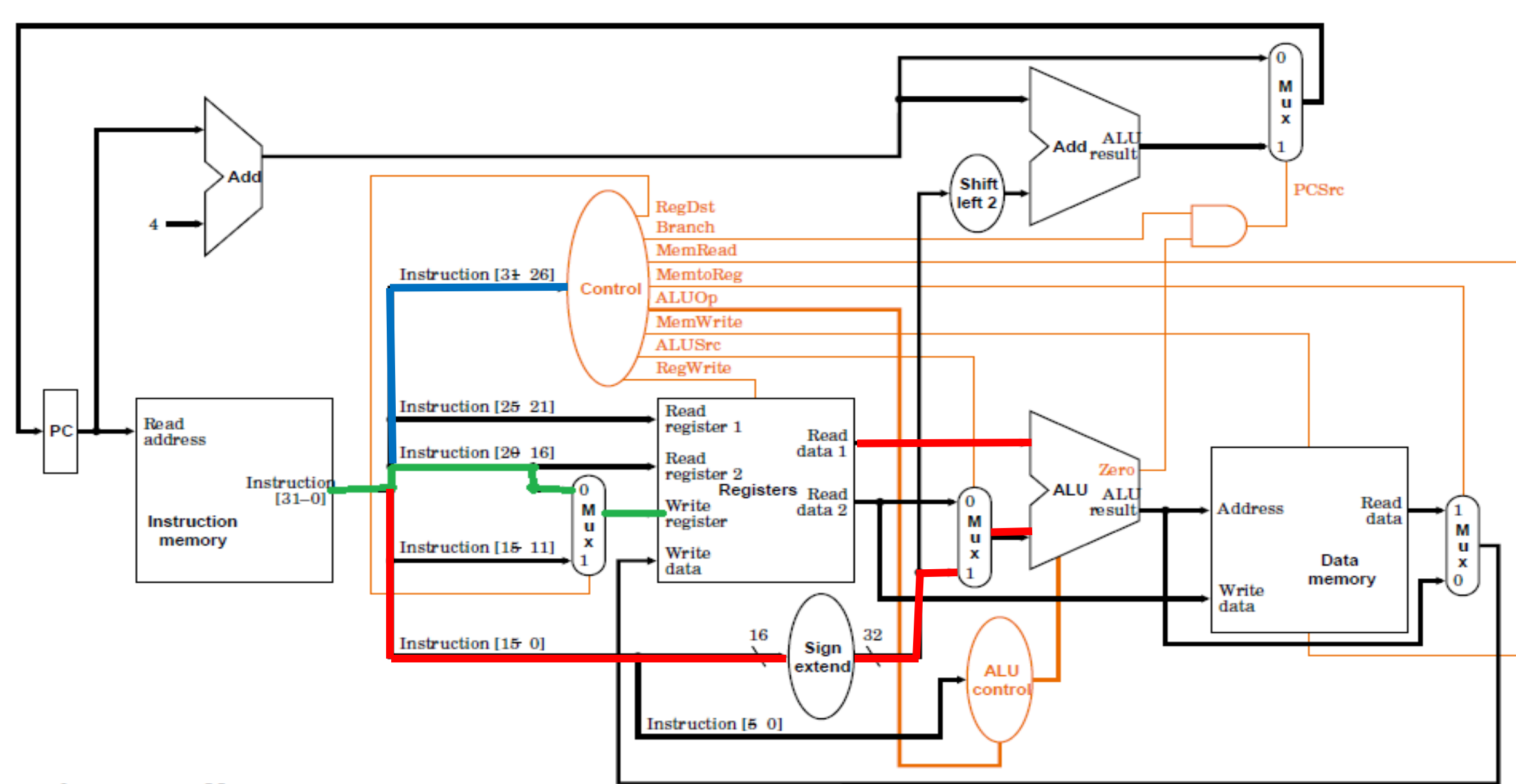

lw rs rt offset

 
Load/store: lw \$t1, 100(\$t2) \Rightarrow lw rt, 100(rs)




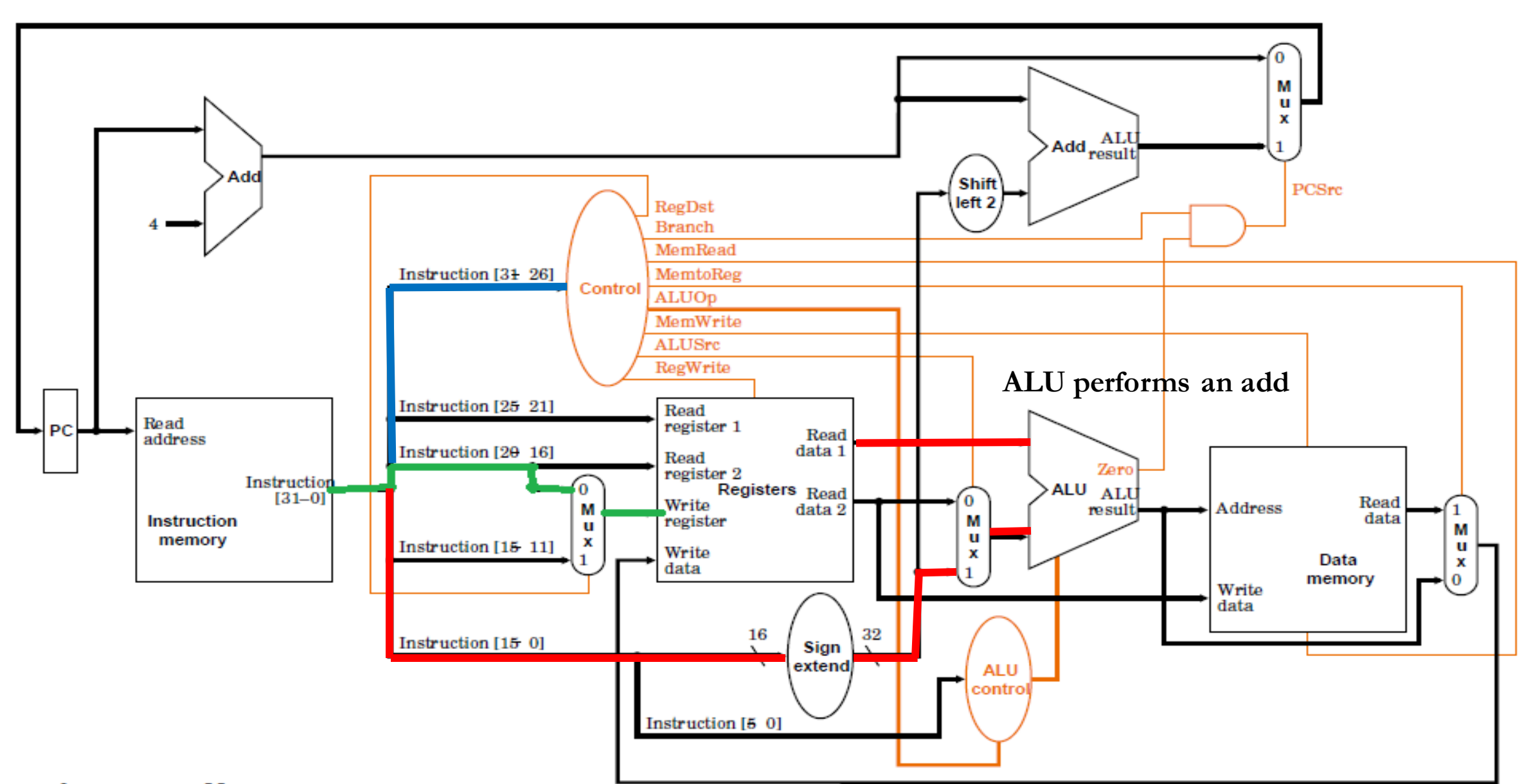

lw rs rt offset

 
Load/store: lw \$t1, 100(\$t2) \Rightarrow lw rt, 100(rs)




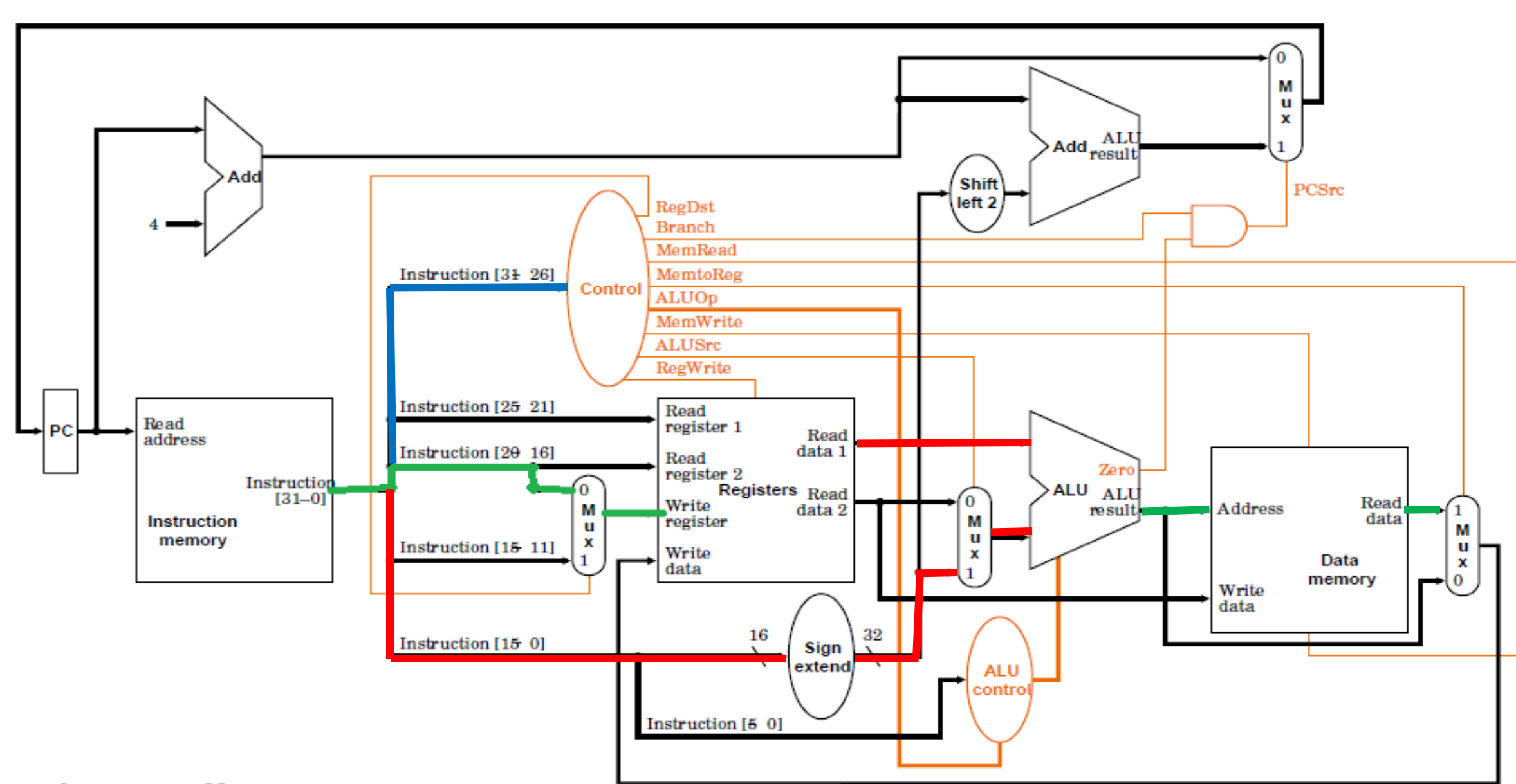

lw rs rt offset

 
Load/store: lw \$t1, 100(\$t2) \Rightarrow lw rt, 100(rs)




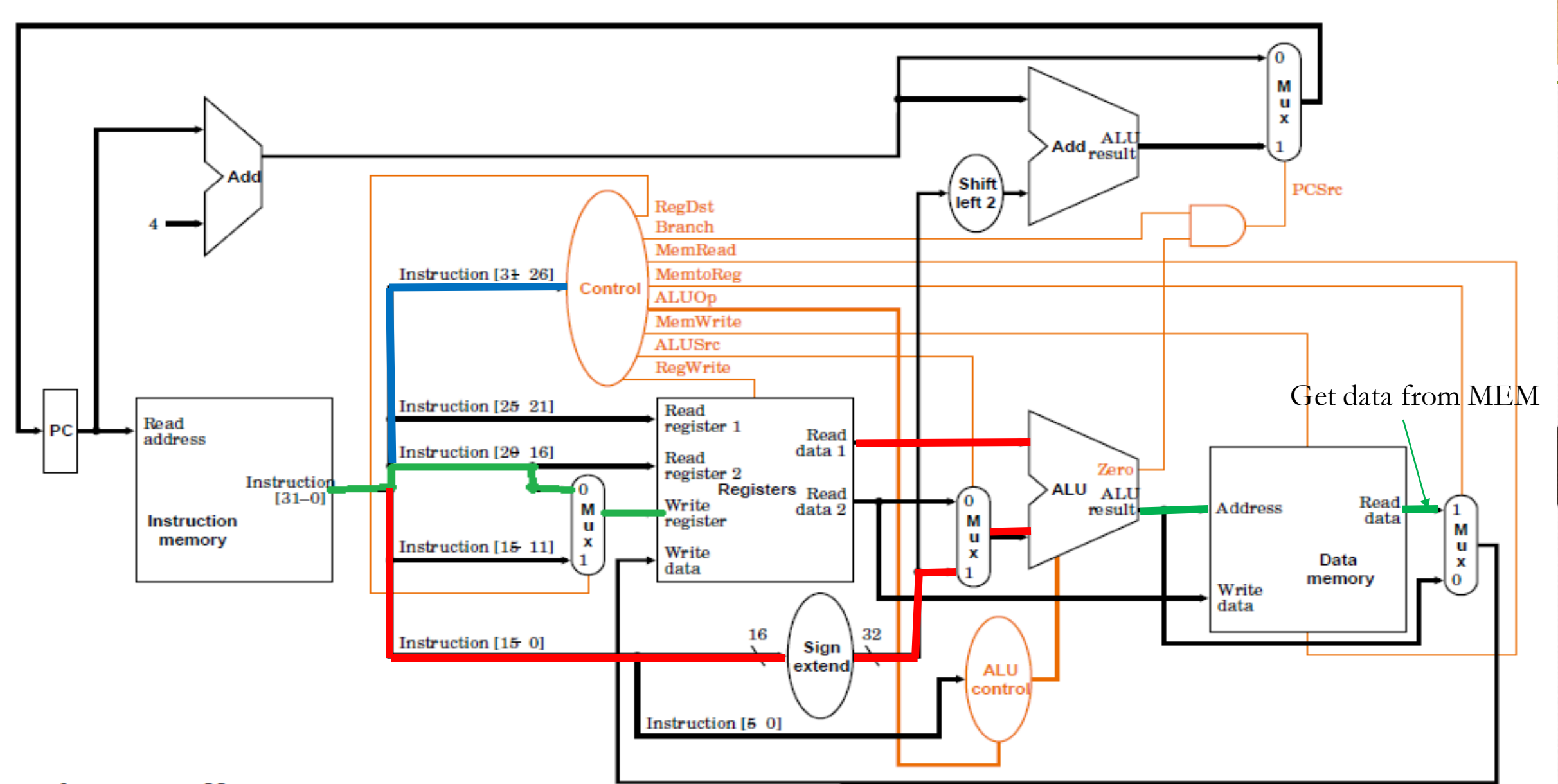

lw rs rt offset

 
Load/store: lw \$t1, 100(\$t2) \Rightarrow lw rt, 100(rs)




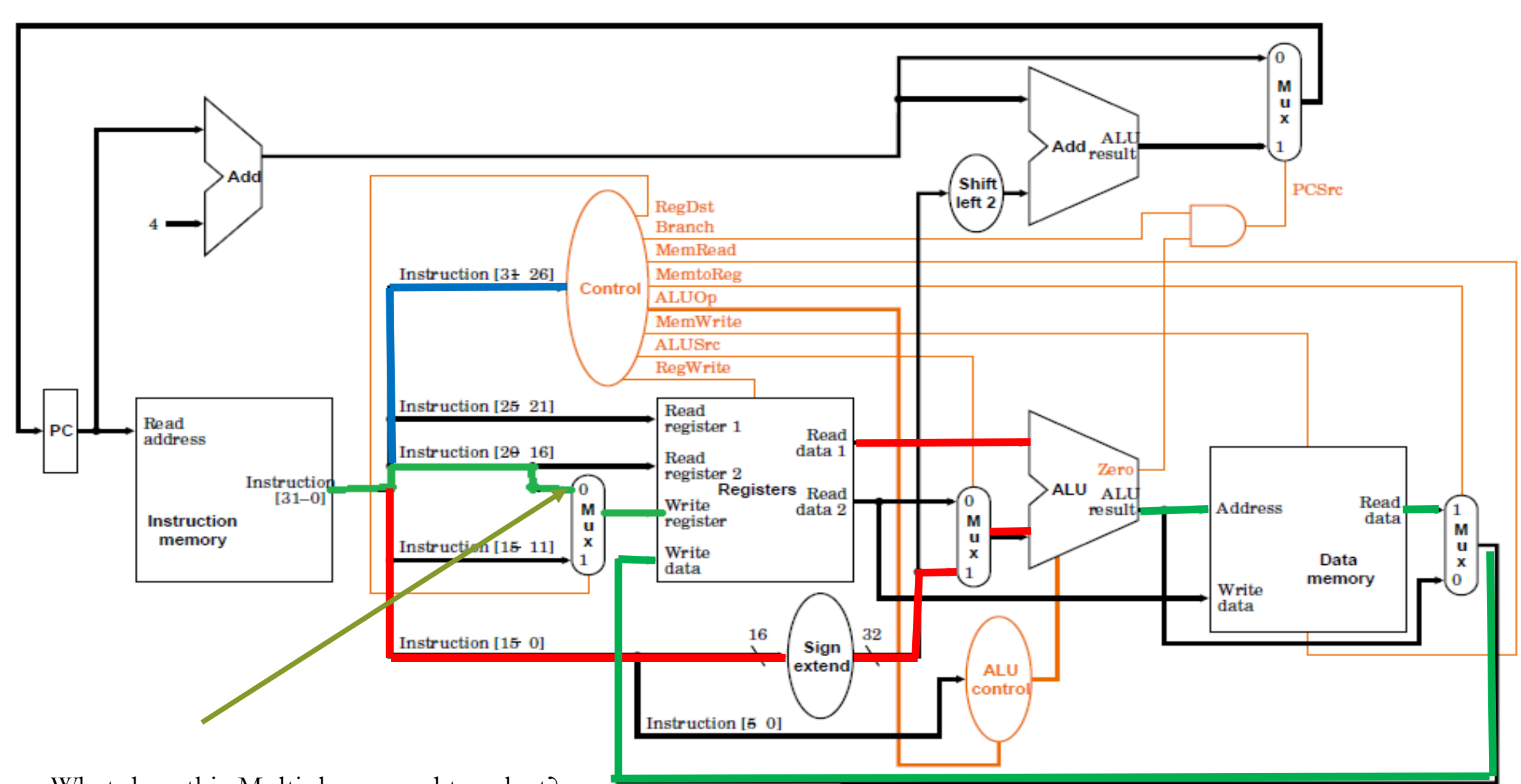

What does this Multiplexor need to select?

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



 



What does this Multiplexor need to select?

Zero

Option 1 is used for which instructions?

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



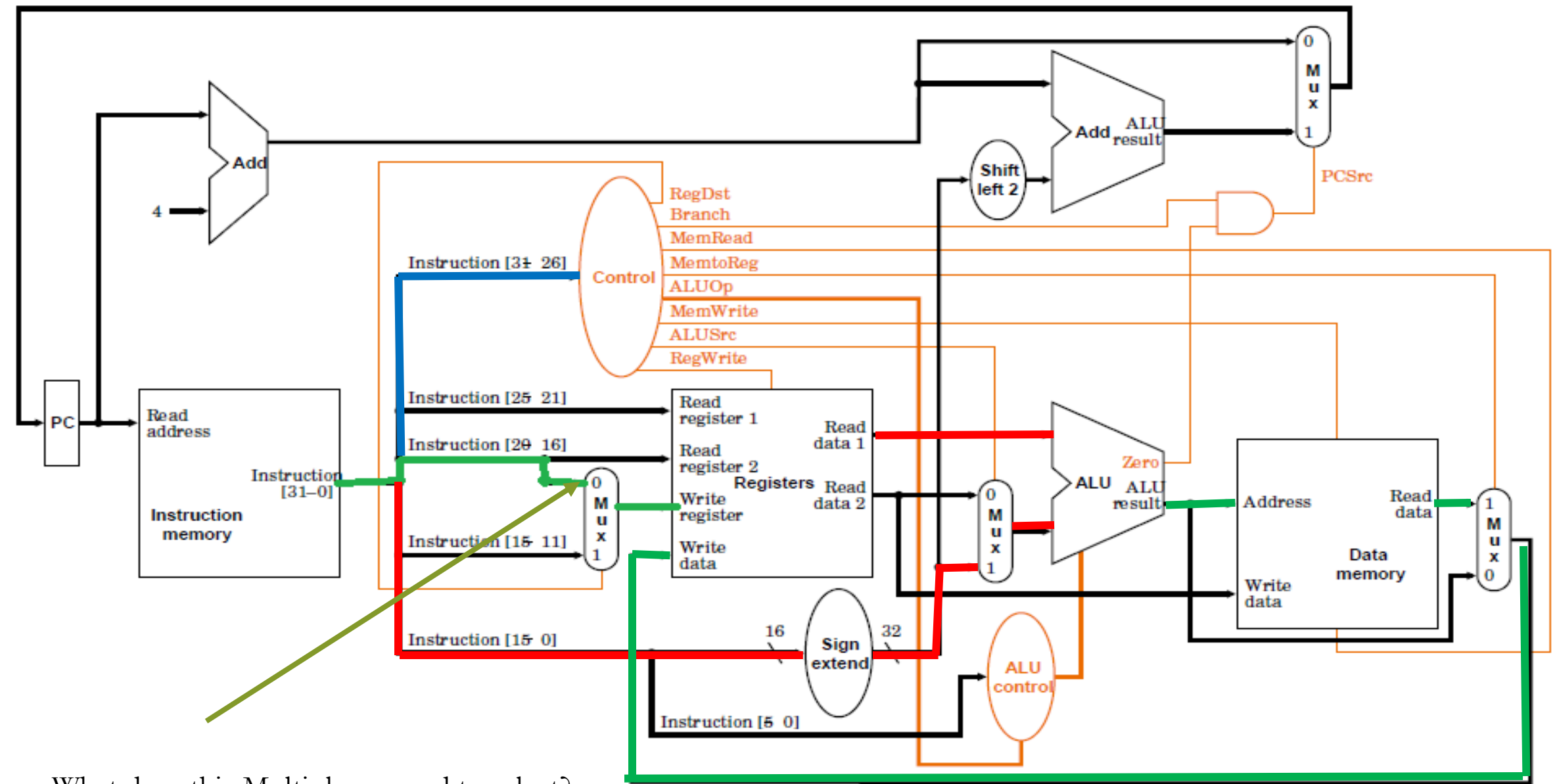


What does this Multiplexor need to select?

Zero


Option 1 is used for which instructions?


Rformat

 Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



BRANCHING

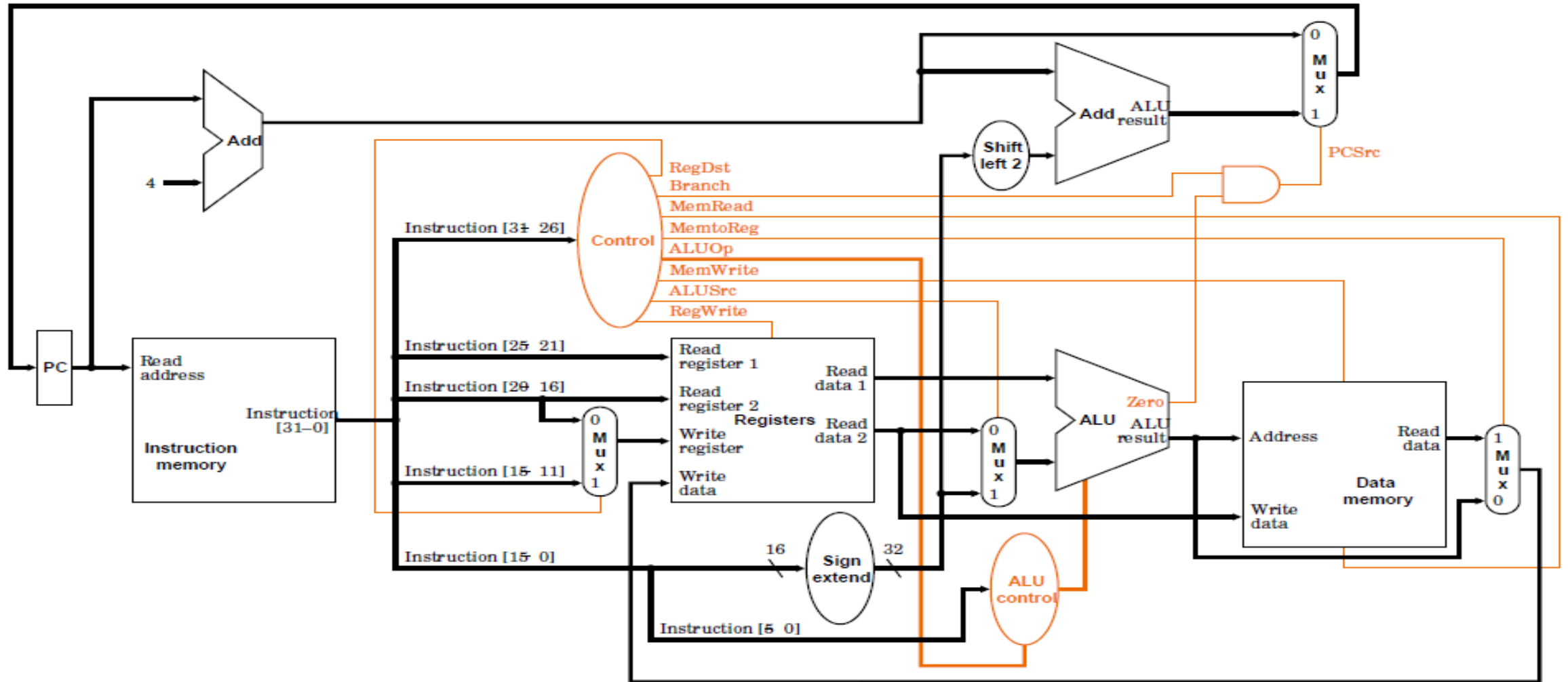


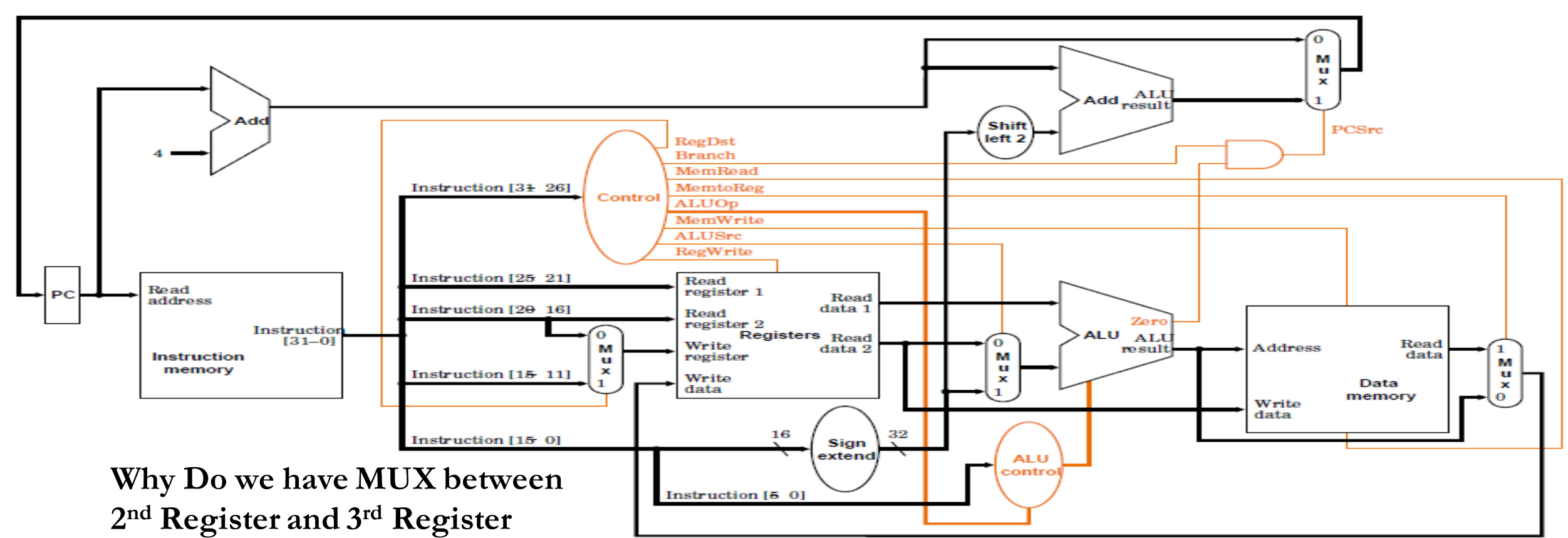


Why Do we have MUX between
2nd Register and 3rd Register
(RegDst Mux)

- A) Write Register for SW and Beq instruction
- B) Write Register for LW and SW
- C) Write Register for Data Memory
- D) Write Register between an Rformat Instruction and LW
- E) Write Register between Add instruction and Sub Instruction

BRANCHING

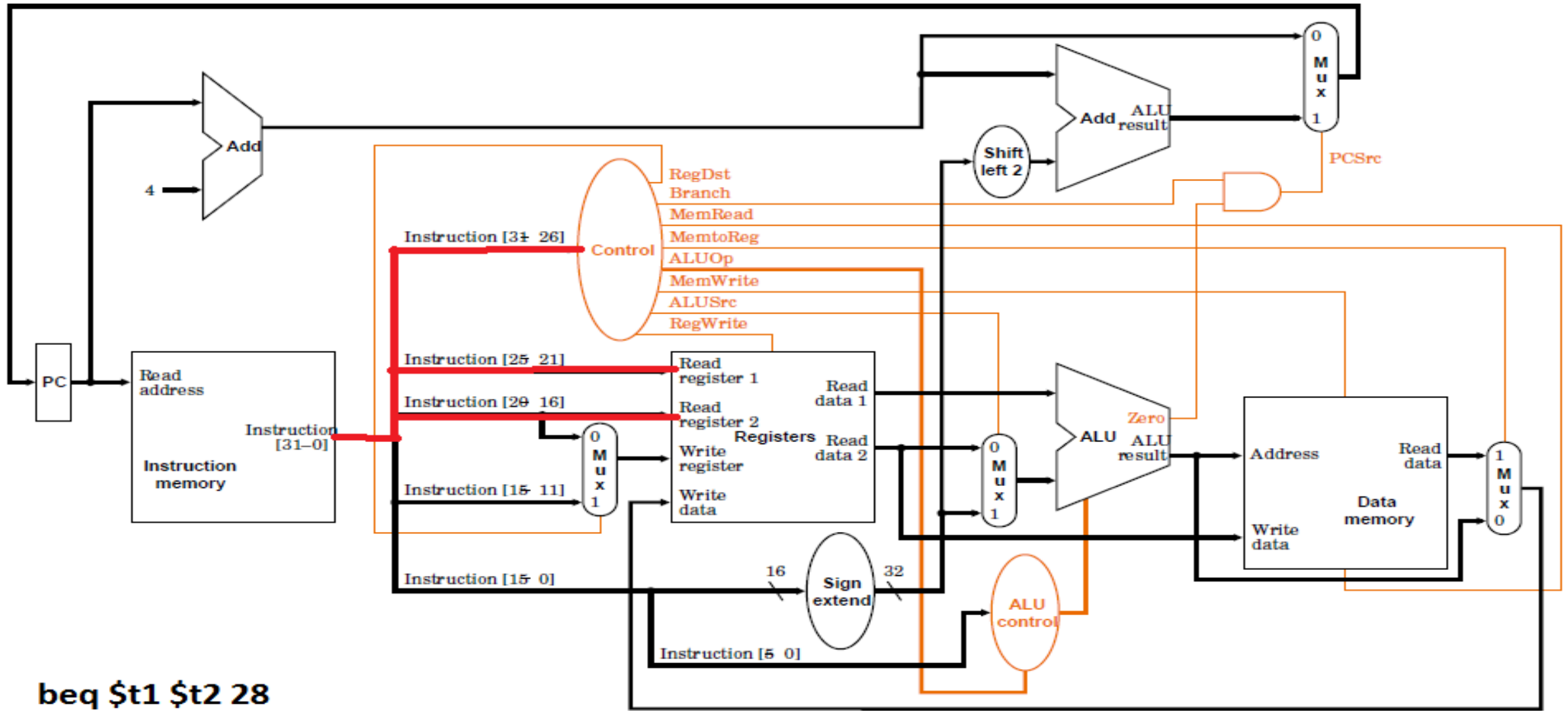


BRANCHING

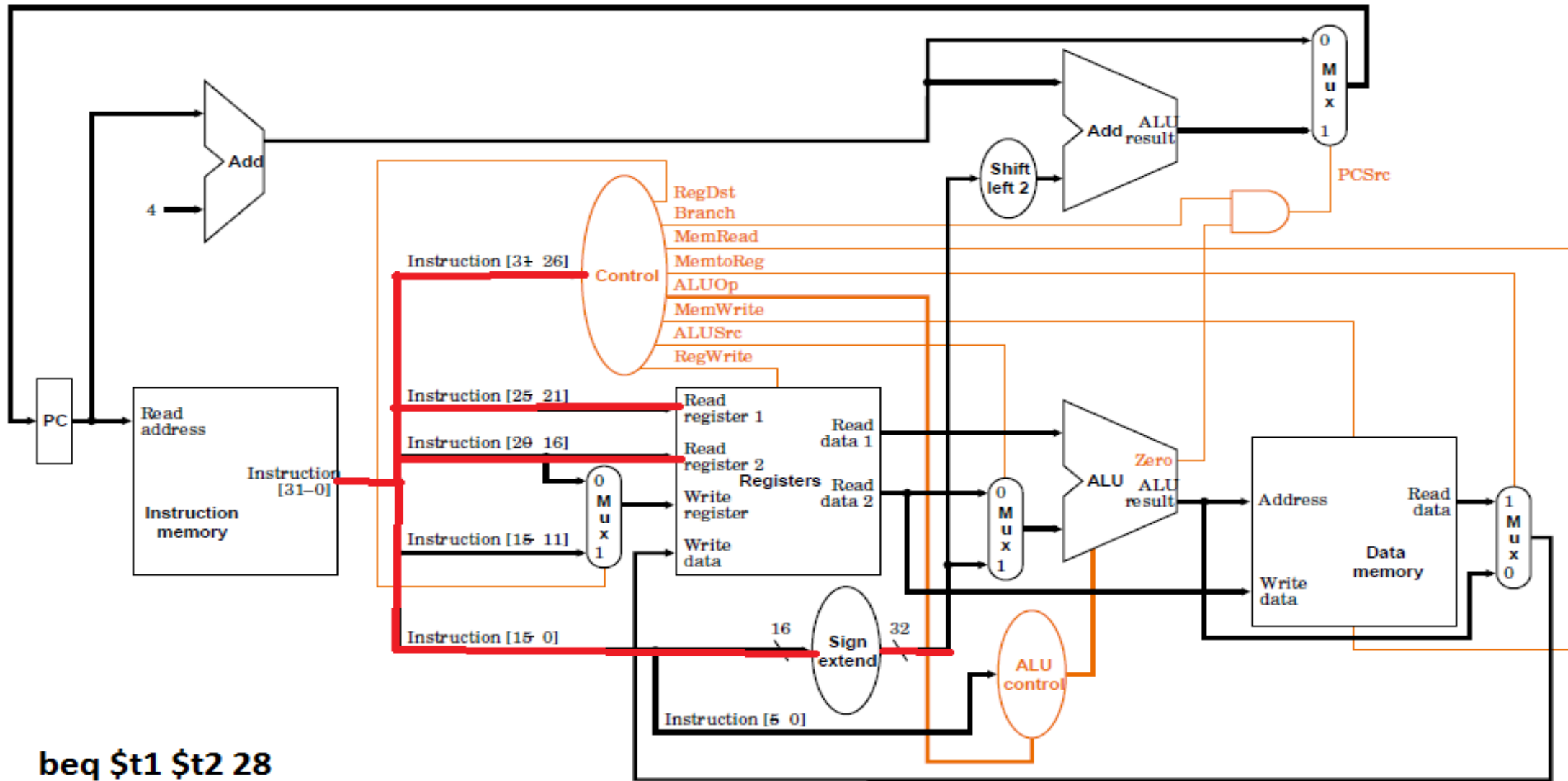

beq \$t1 \$t2 28


BRANCHING

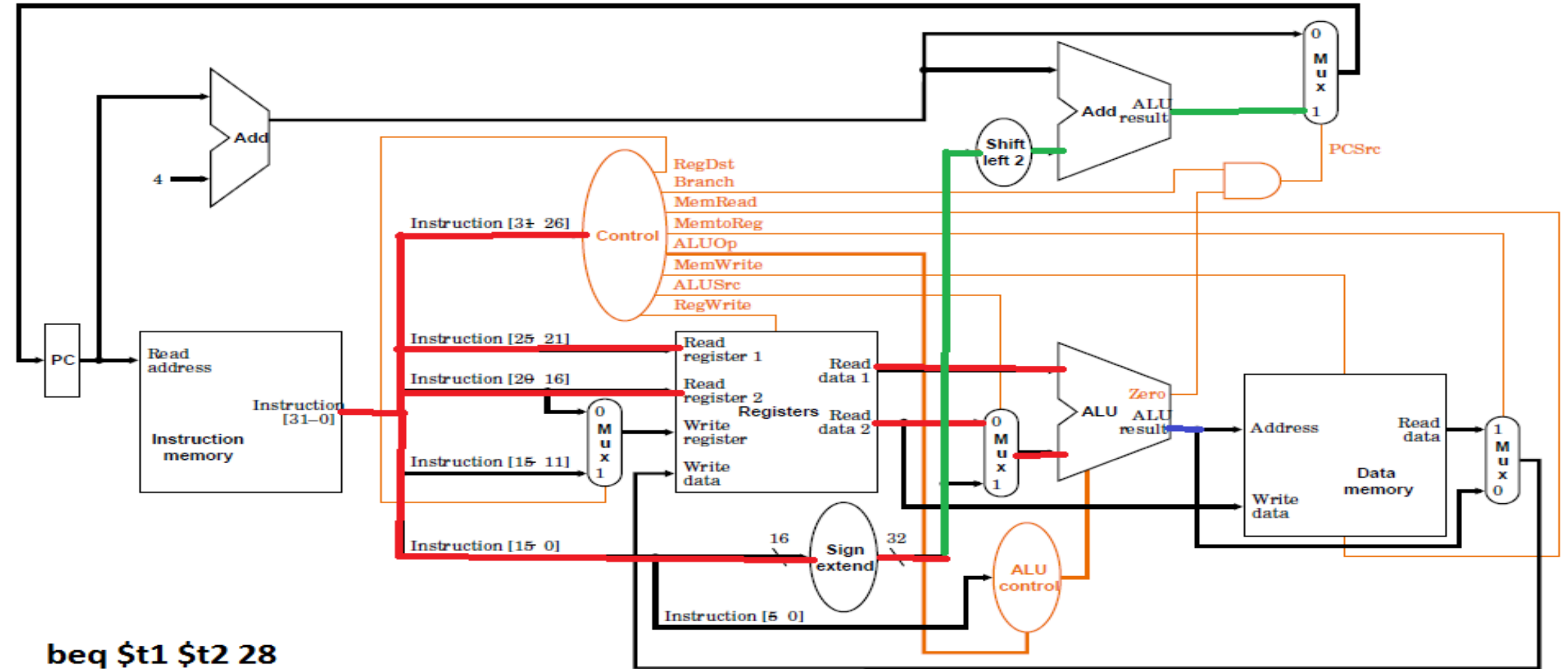

BRANCHING

Computation of Branch Target address

beq \$t1 \$t2 28

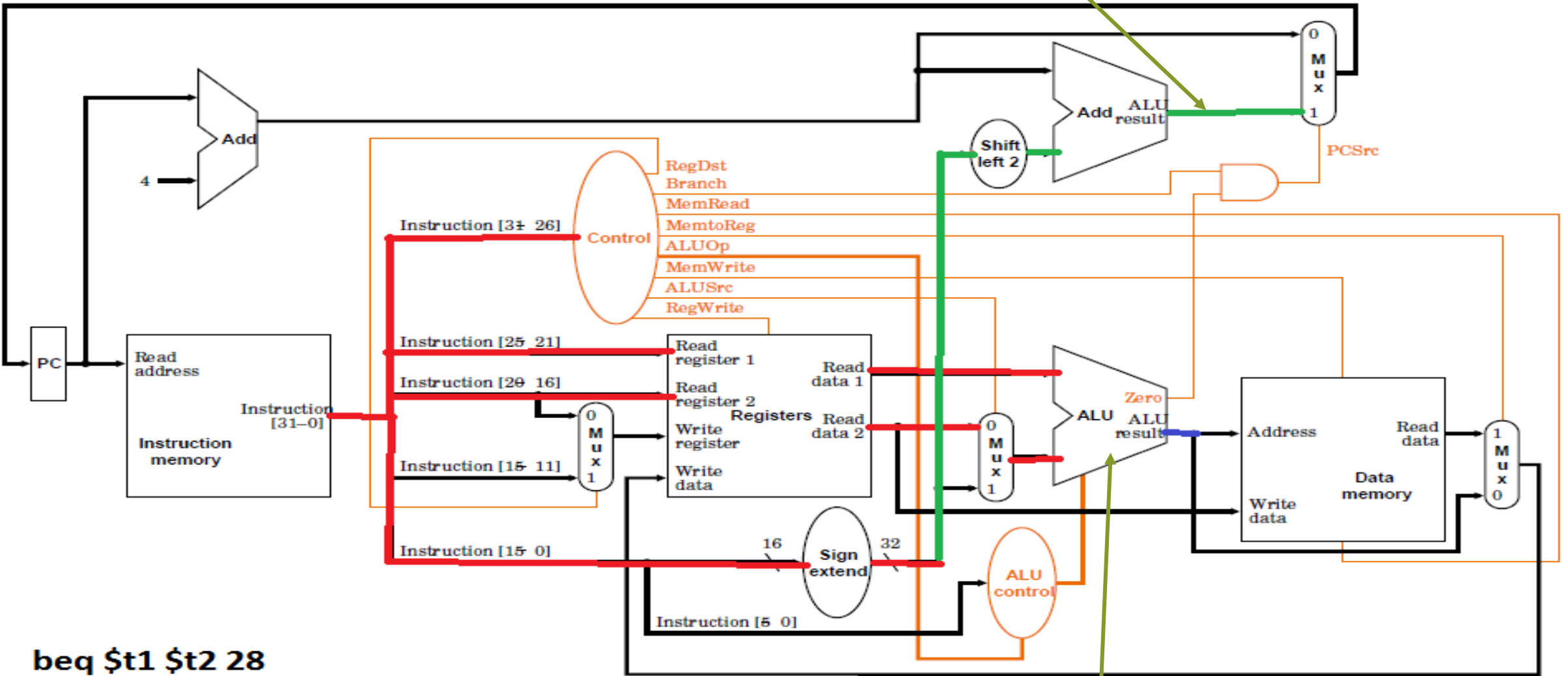


Branch instruction ALU will subtract
Two Source Registers

BRANCHING

Computation of Branch Target address

beq \$t1, \$t2, 28

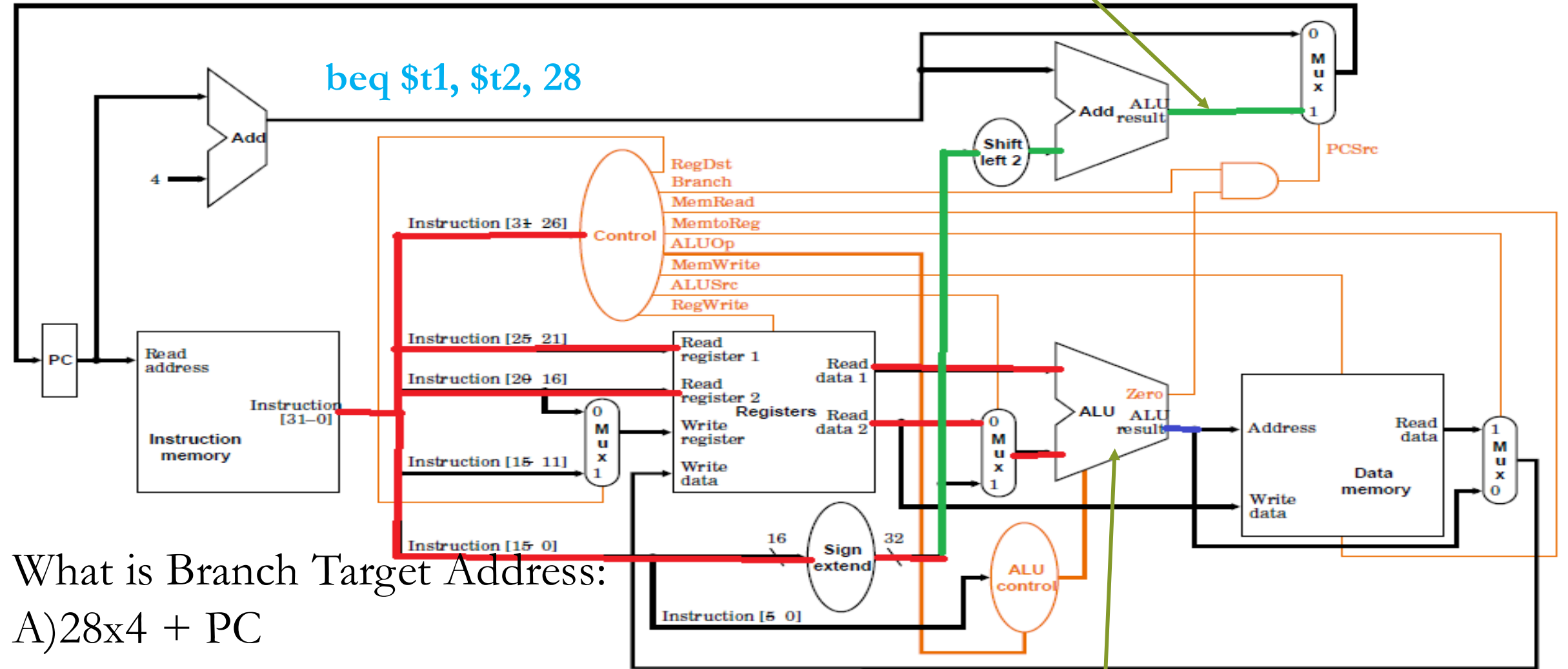

What is Branch Target Address:

A) $28 \times 4 + PC$

B) 28×4

C) $28 \times 32 + PC + 4$


D) $28 \times 4 + (PC + 4)$

Branch instruction ALU will subtract
Two Source Registers

BRANCHING

Computation of Branch Target address

beq \$t1, \$t2, 28

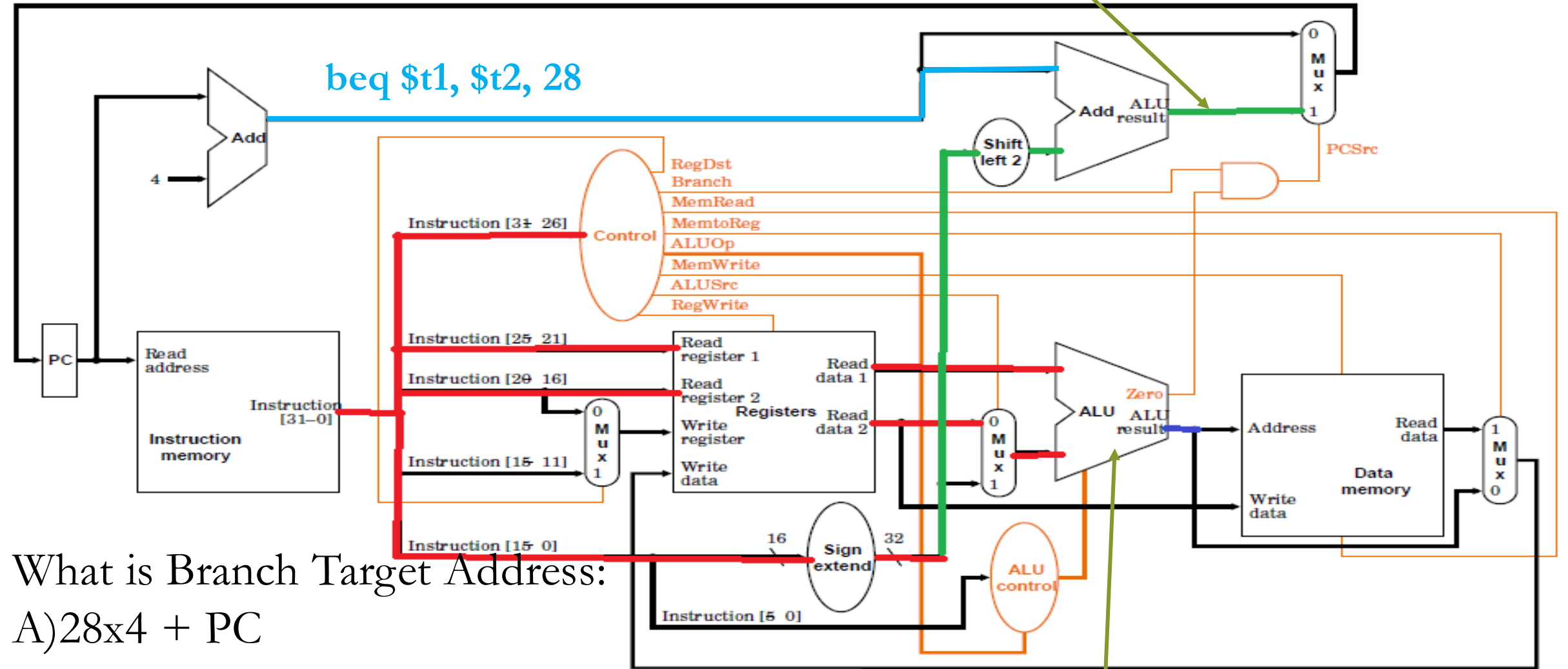


What is Branch Target Address:


- A) $28 \times 4 + \text{PC}$
- B) 28×4
- C) $28 \times 32 + \text{PC} + 4$
- D) $28 \times 4 + (\text{PC} + 4)$

Branch instruction ALU will subtract
Two Source Registers

beq \$t1, \$t2, 28

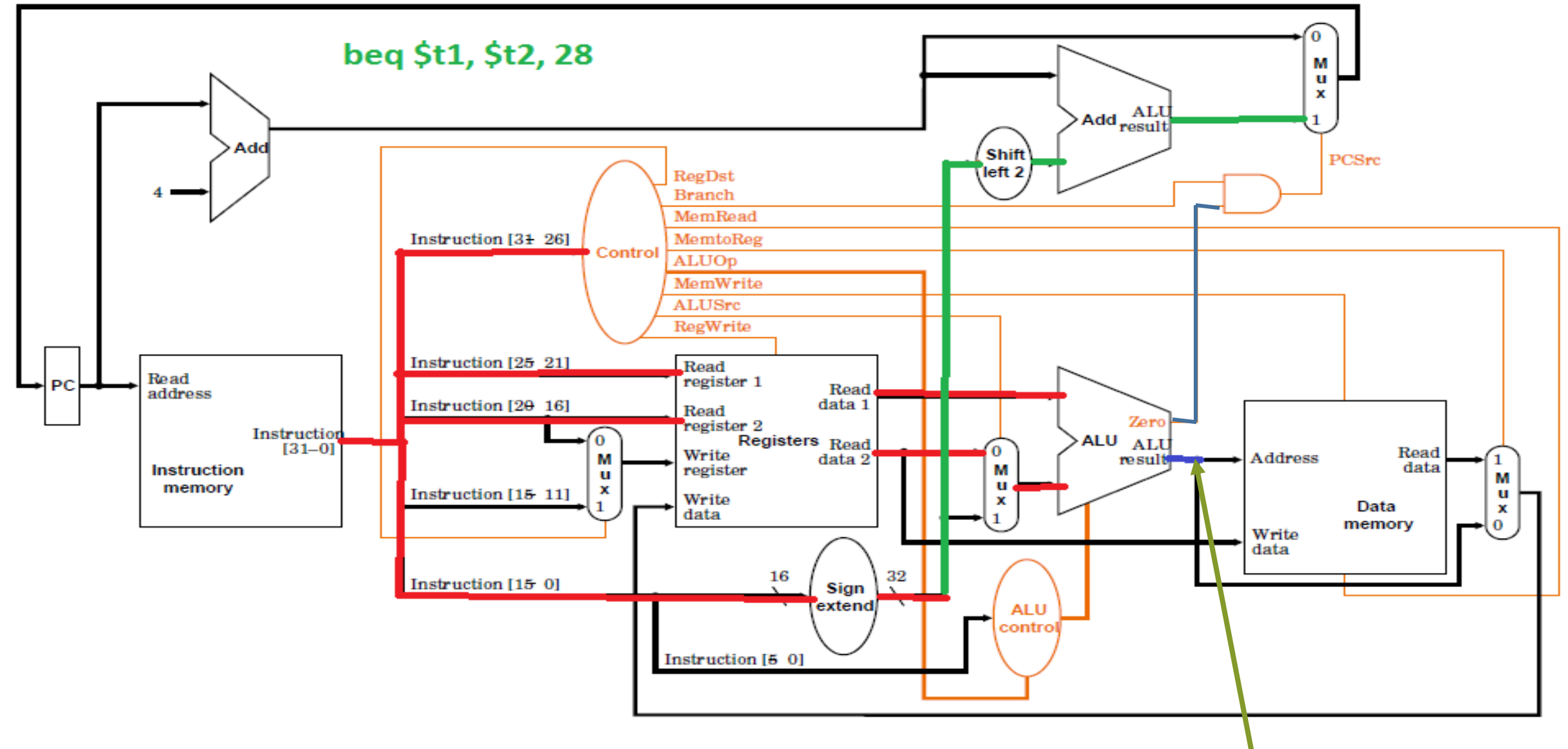

What is the value here?

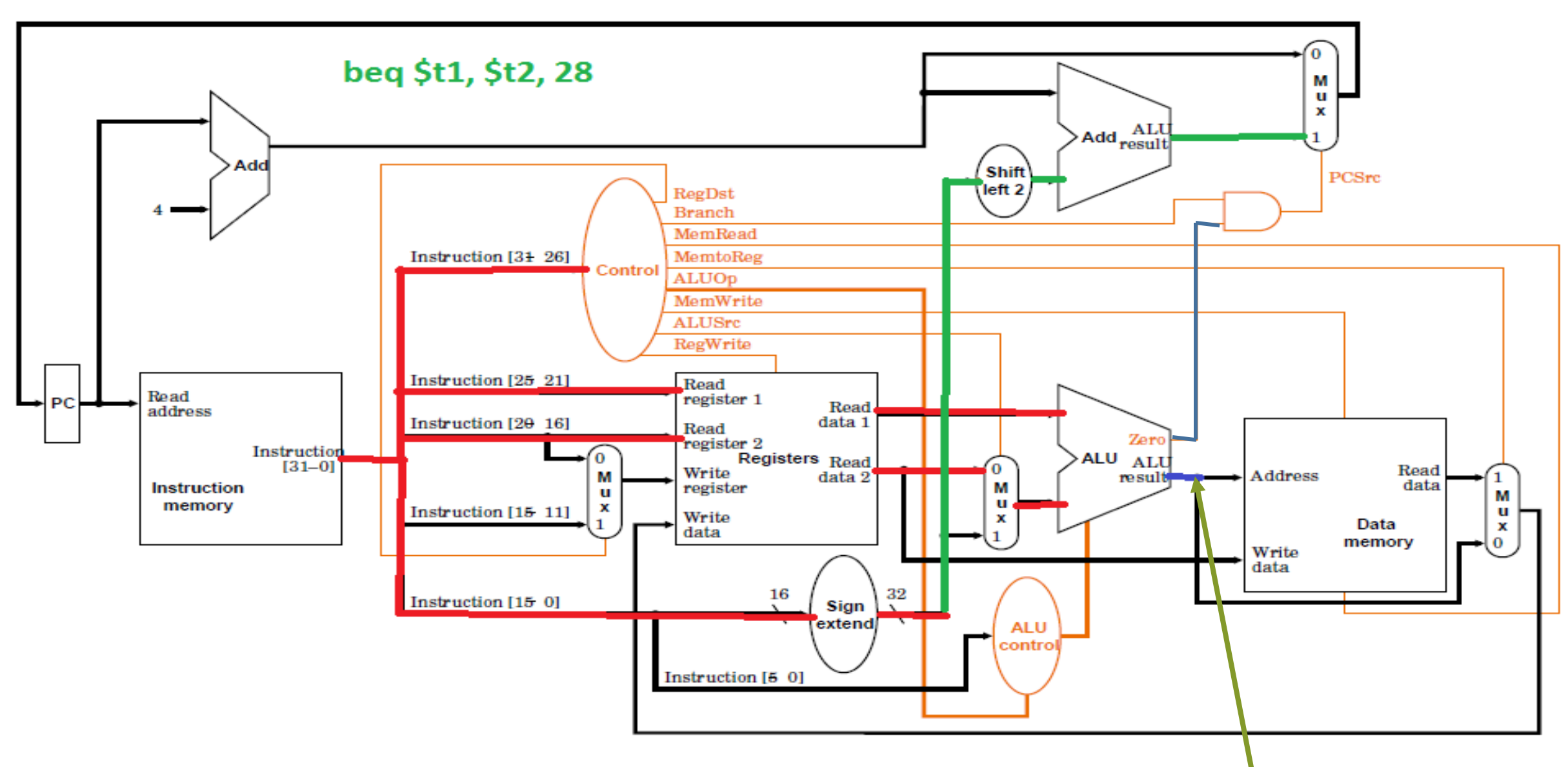


What is the value here?

If I know `$t1 == $t2`


Result is zero

beq \$t1, \$t2, 28

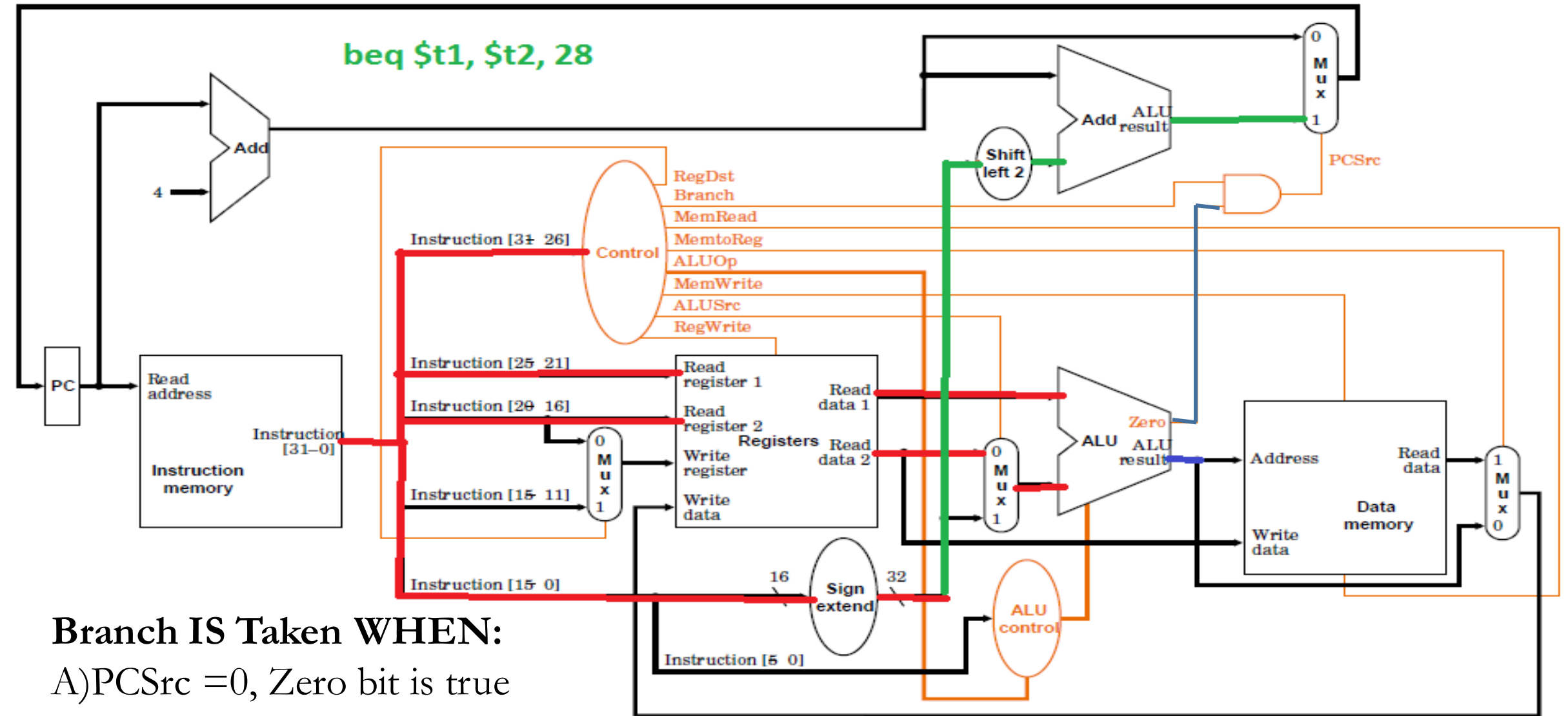

Branch IS Taken WHEN:

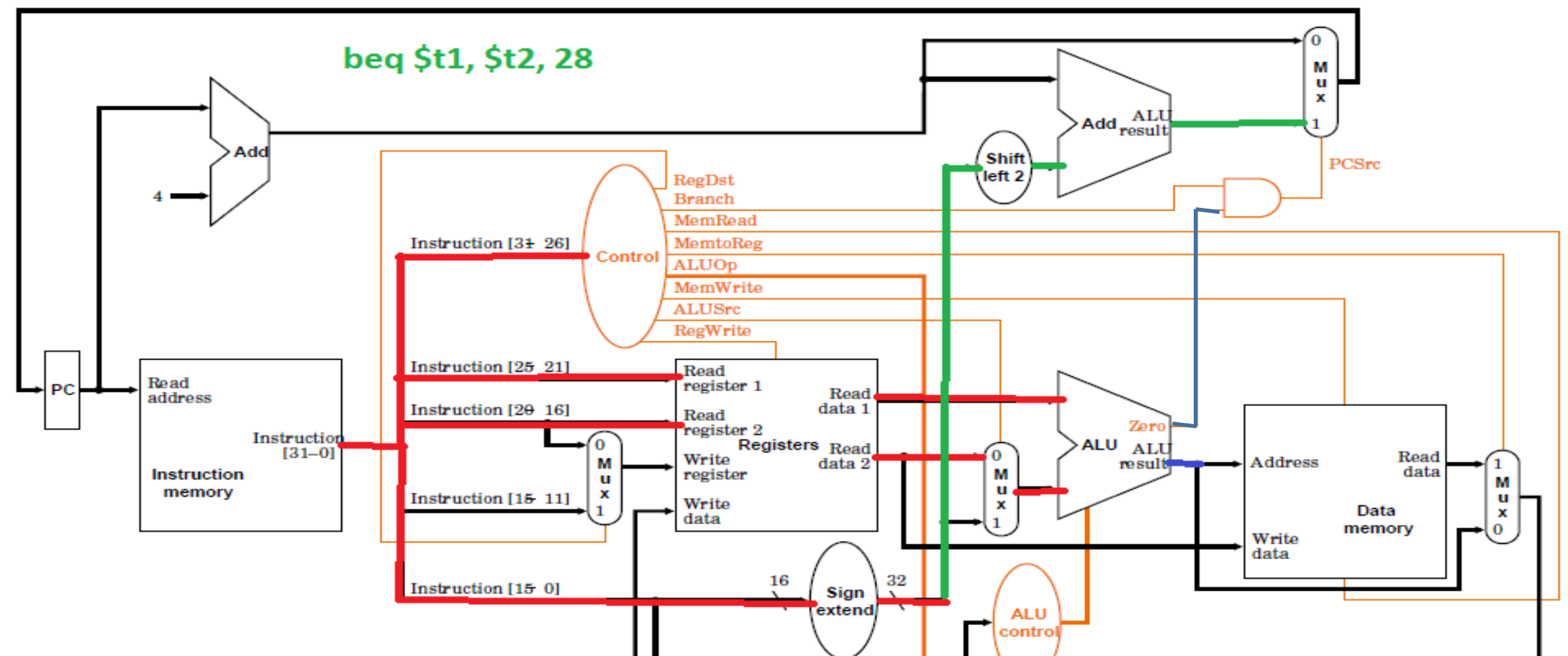
- A) PCSrc = 0, Zero bit is true
- B) Branch = 1, Zero = 1, PCSrc = 1
- C) Branch = 0, Zero = 1, PCSrc = 1
- D) Need more hardware to decide
- E) ALUSrc = 0, Branch = 1, Zero = 0



Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Tells you exactly what the control lines
Need to be for each instruction


Which instruction is this?

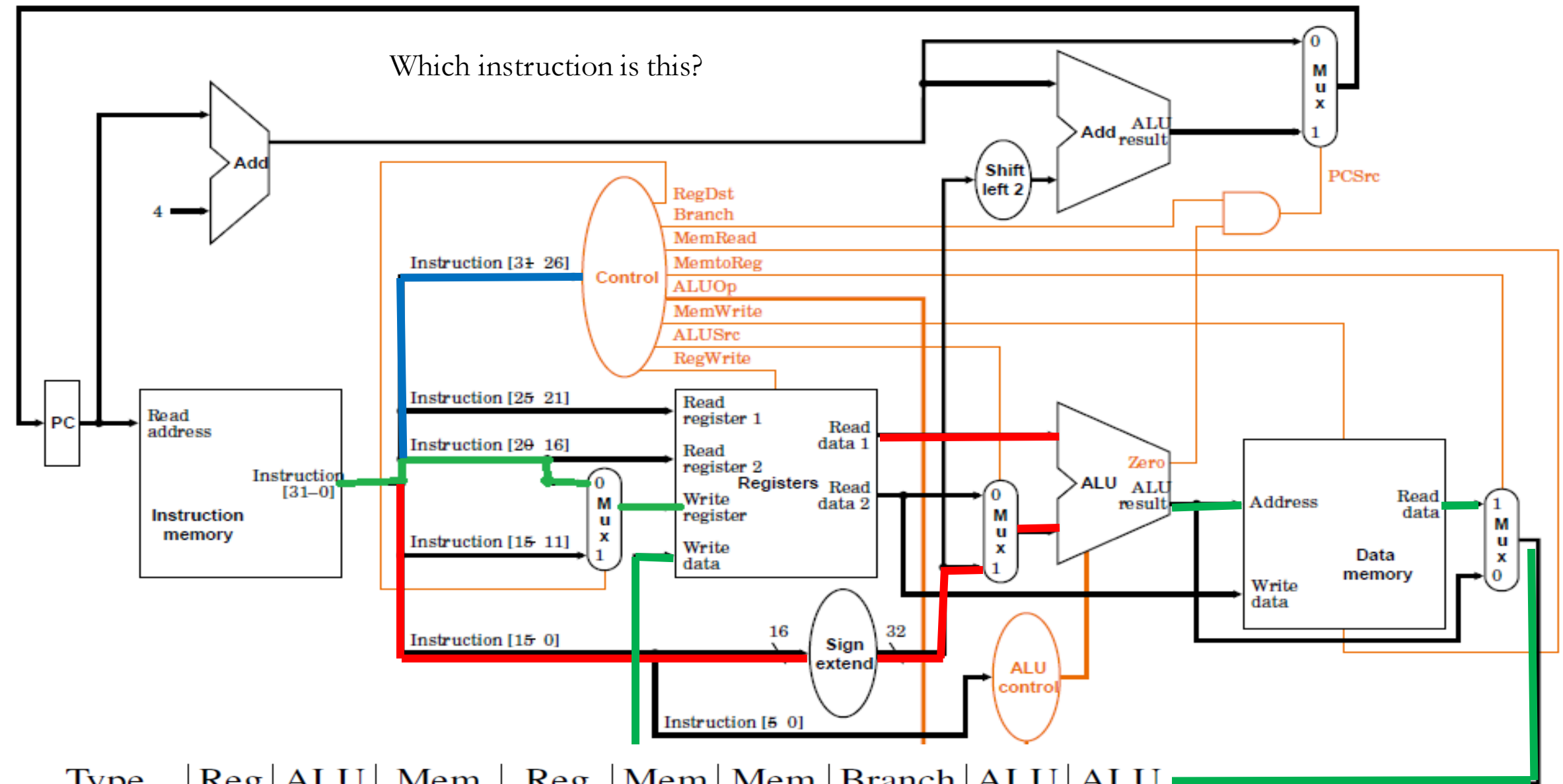

Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	0	1	0	0	1	1	0	0	0


Control Units : Course Notes


sw \$t1, 100(\$t2)

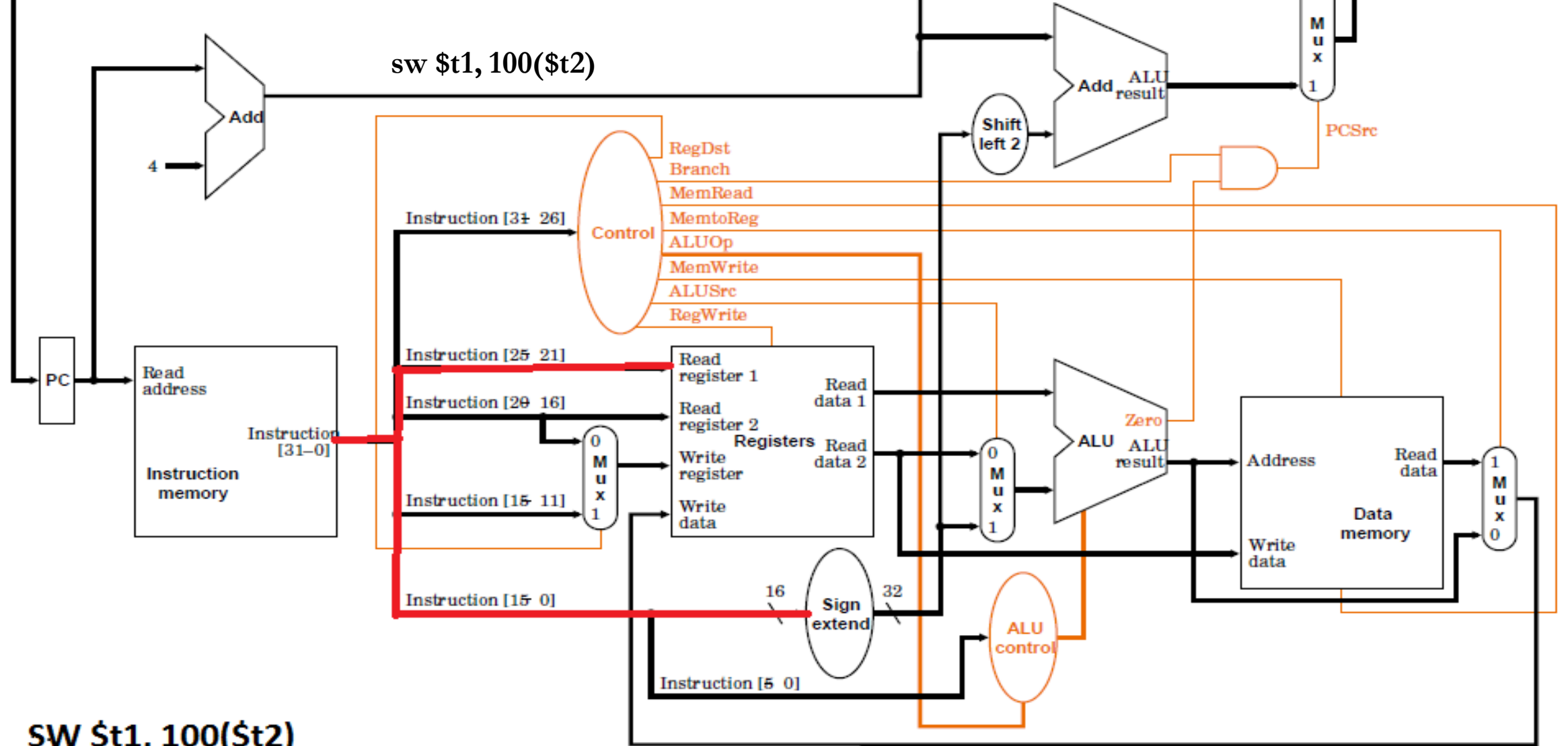

SW \$t1, 100(\$t2)

 
Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`




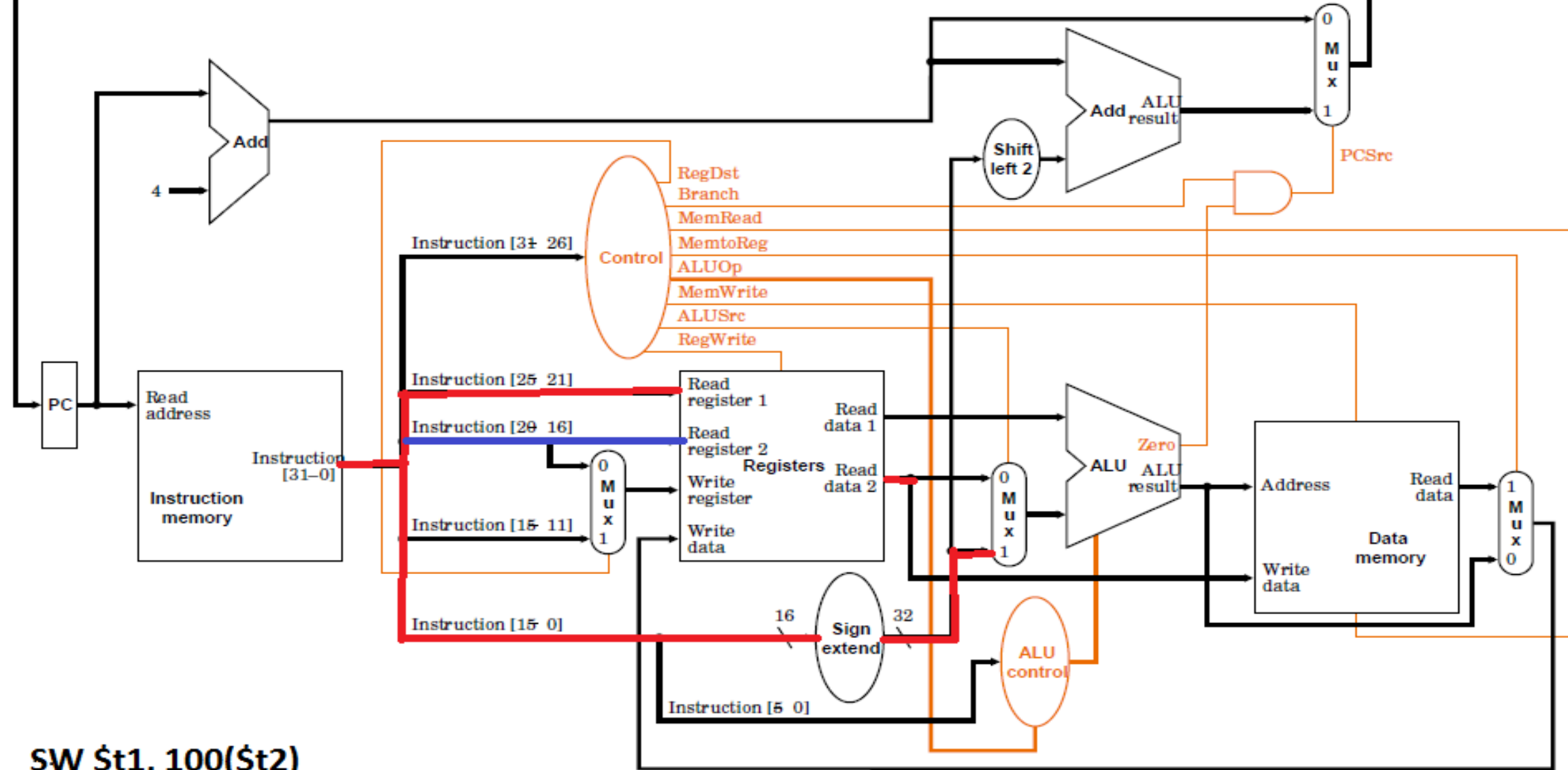


SW \$t1, 100(\$t2)

 
Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



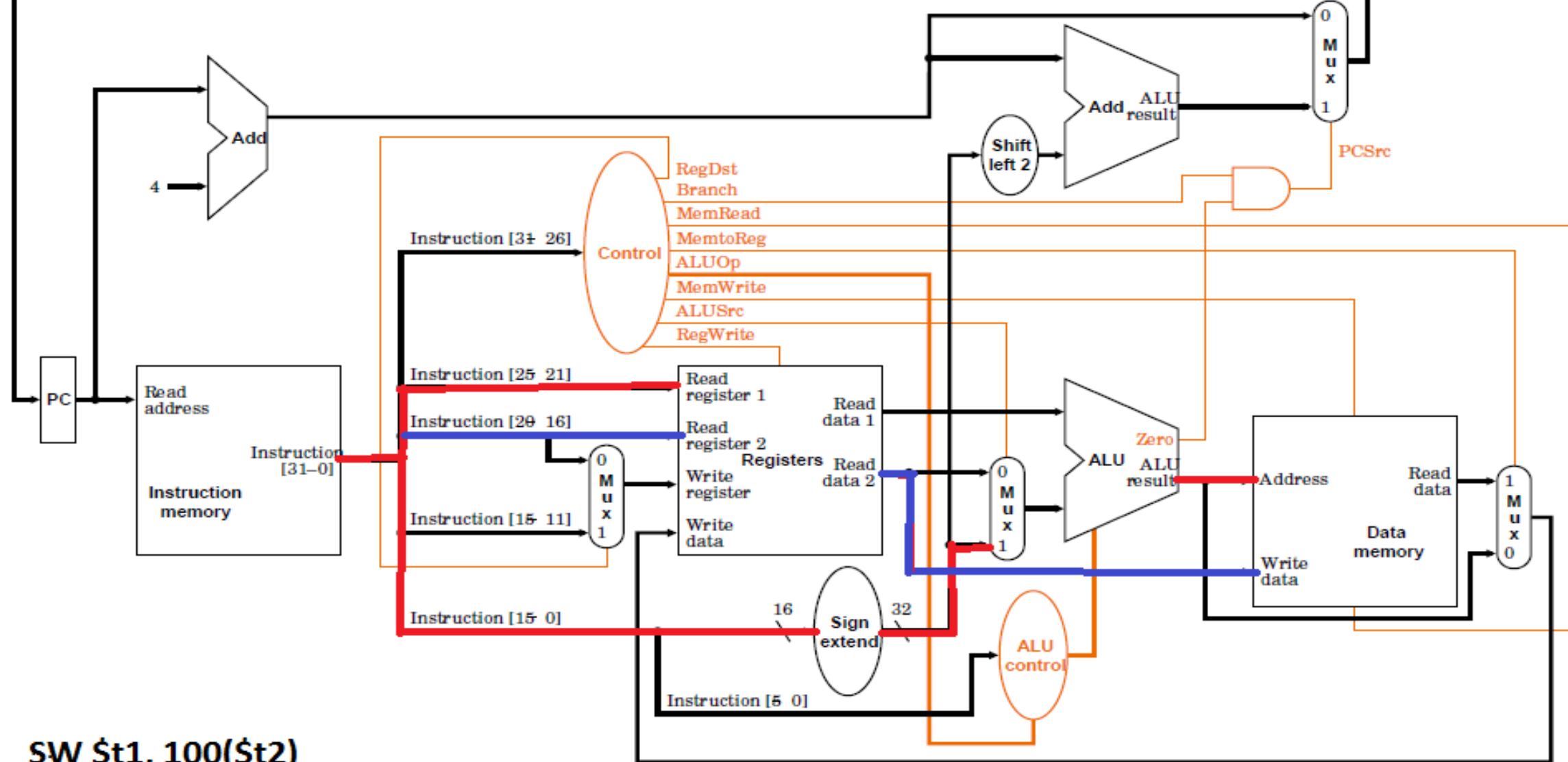

 
Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`



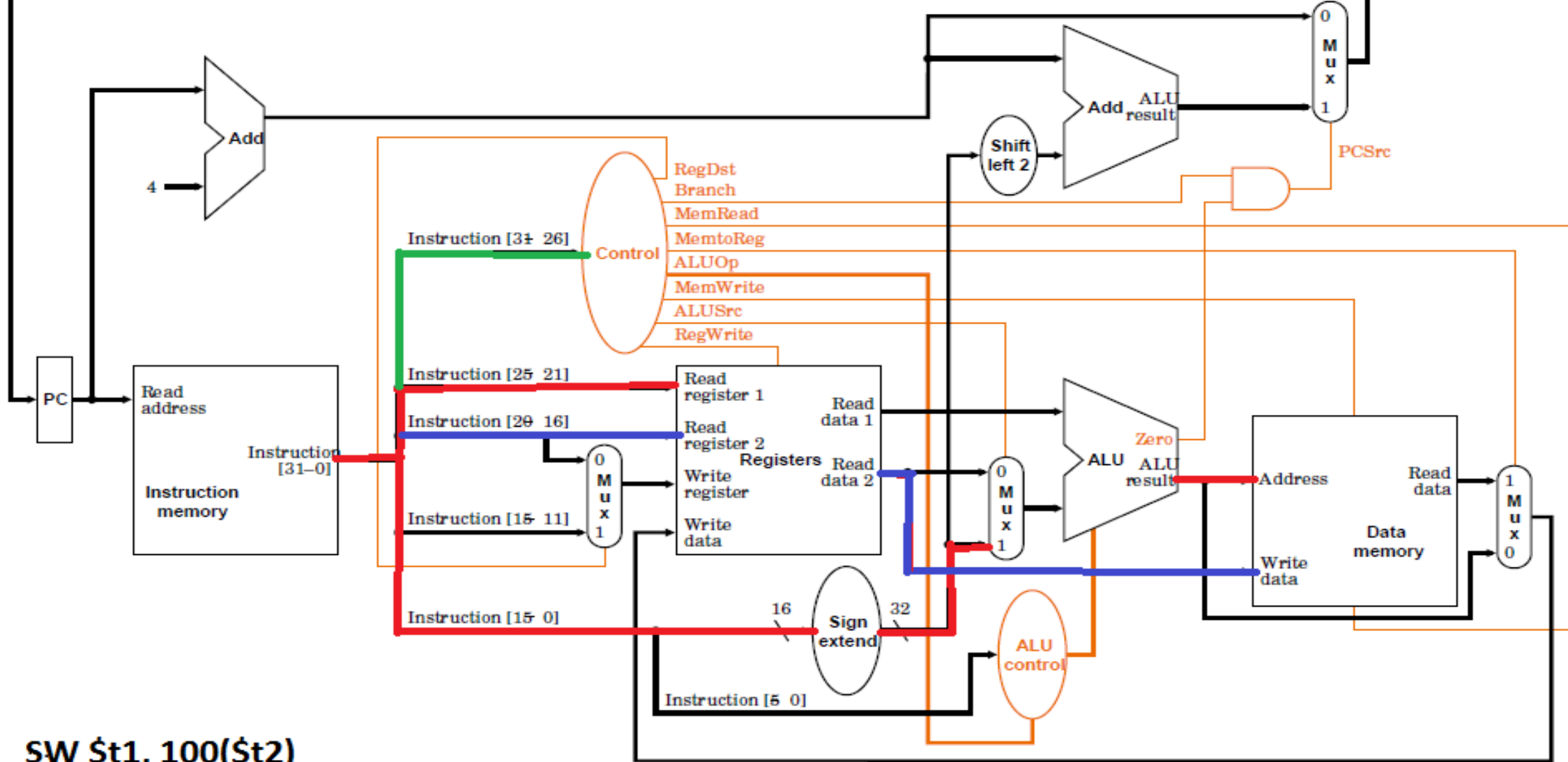


SW \$t1, 100(\$t2)

 
Load/store: `lw $t1, 100($t2) ⇒ lw rt, 100(rs)`




sw \$t1, 100(\$t2)

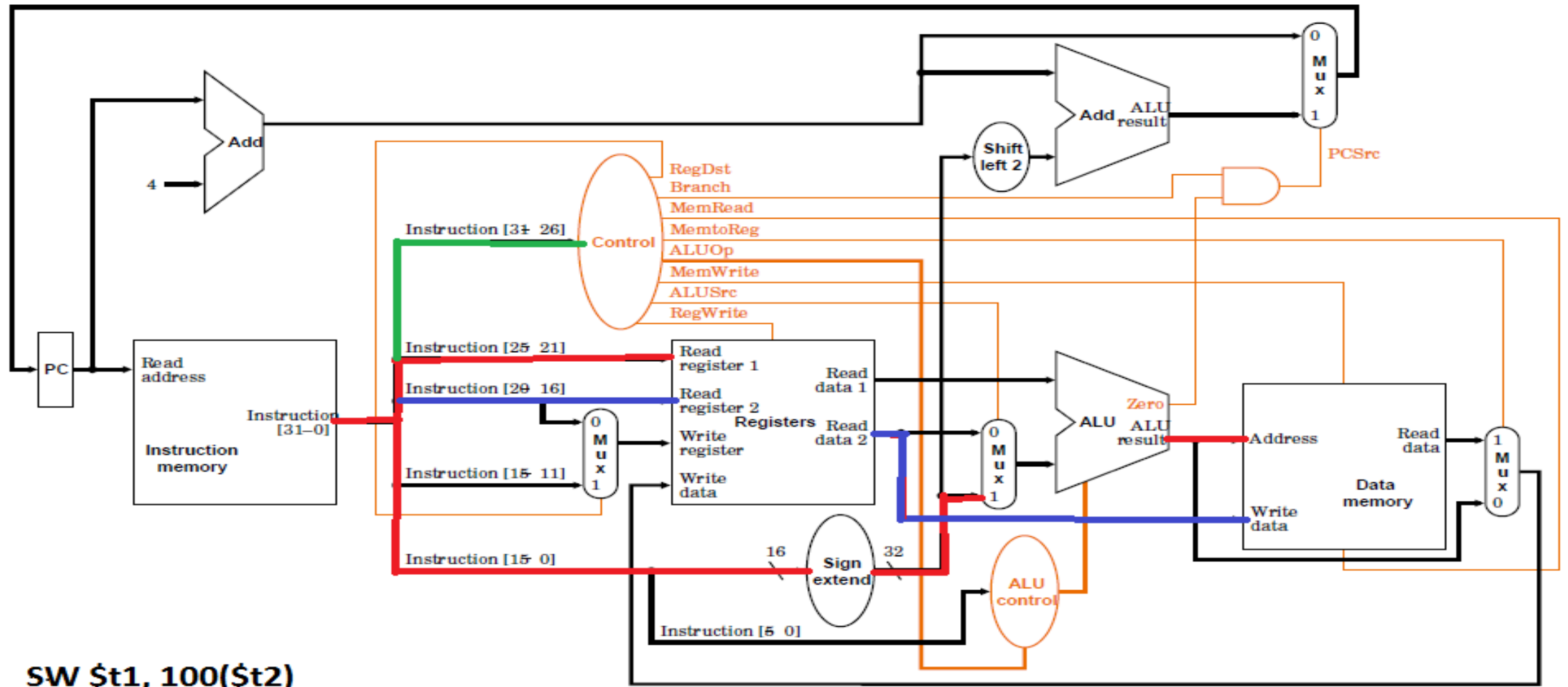

SW \$t1, 100(\$t2)

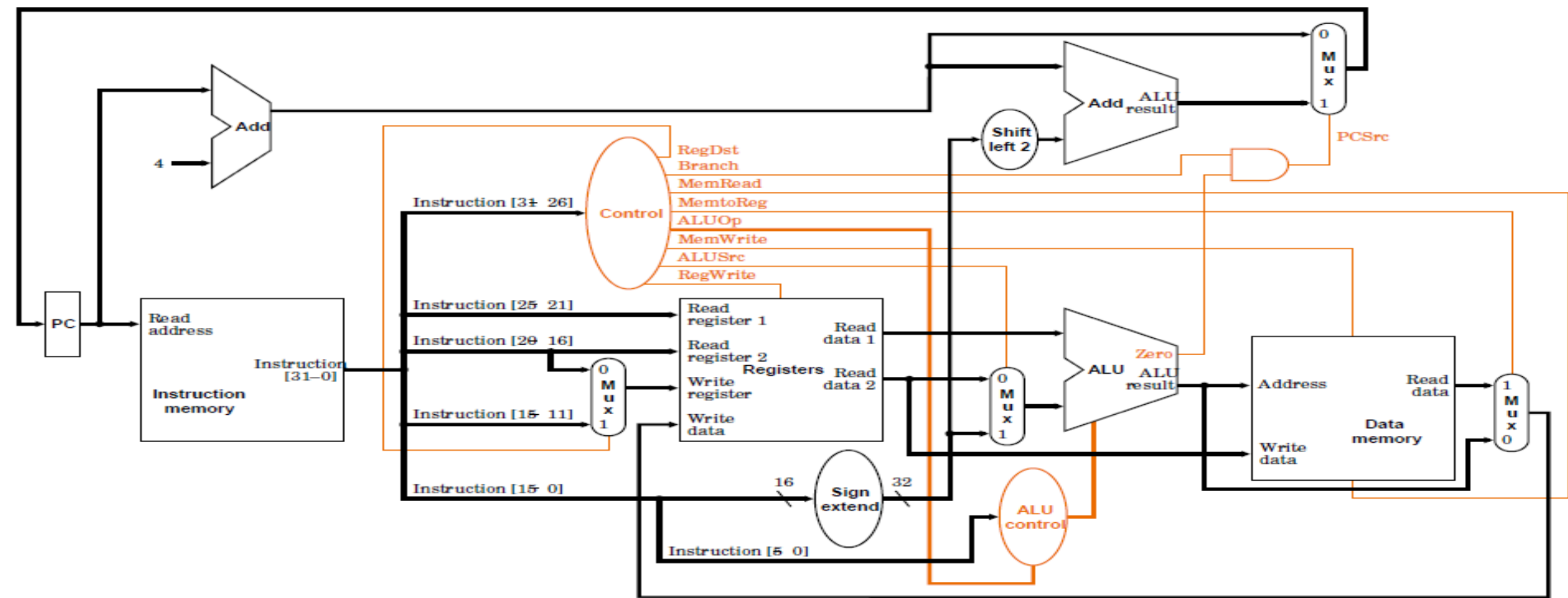

Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

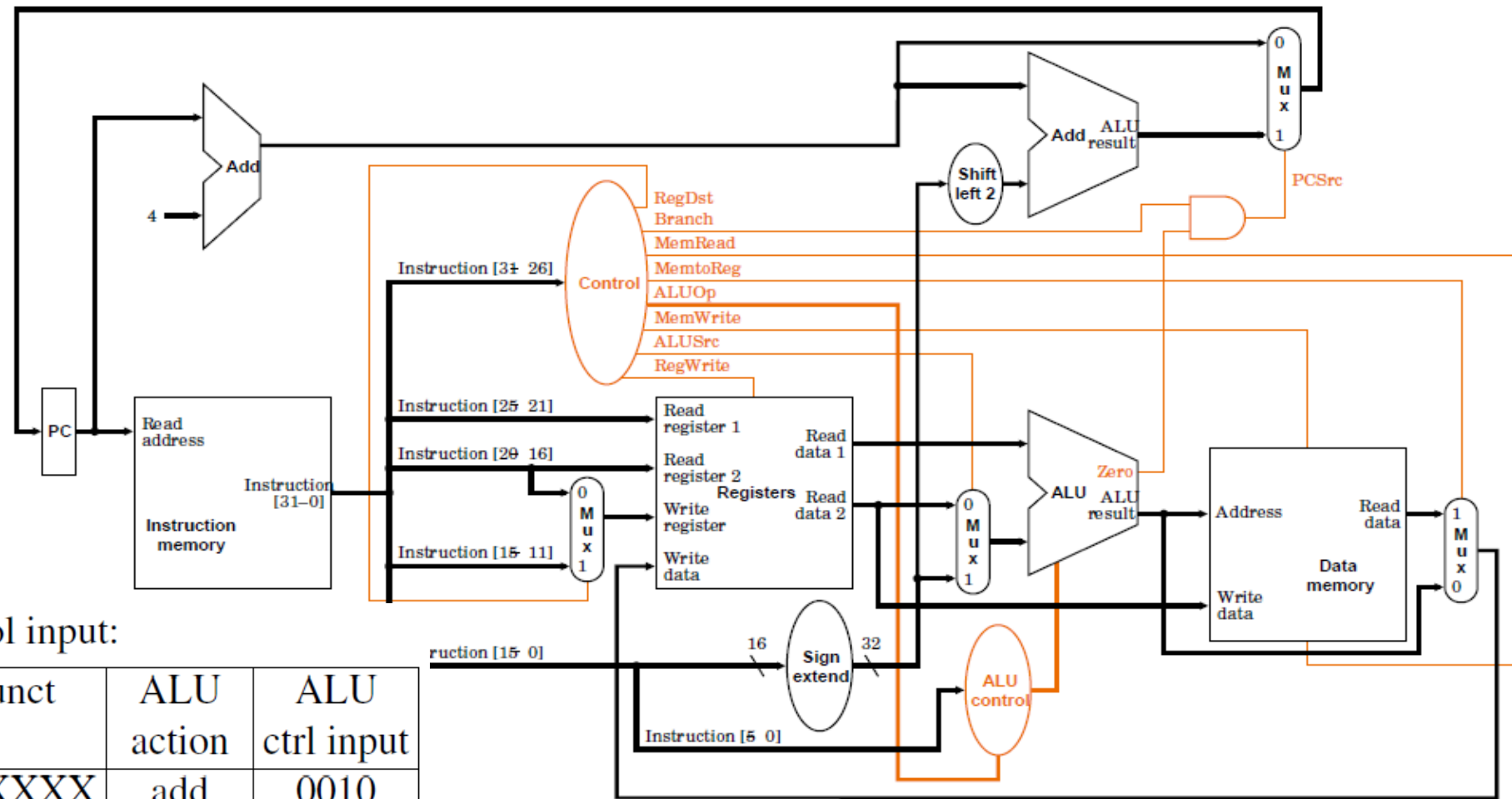

Mapping of operation to ALU control input:

Opcode	Operation	ALUOp	Funct	ALU action	ALU ctrl input
35	lw	00	XXXXXX	add	0010
43	sw	00	XXXXXX	add	0010
4	beq	01	XXXXXX	subtract	0110
0	add	10	100000	add	0010
0	sub	10	100010	subtract	0110
0	and	10	100100	AND	0000
0	or	10	100101	OR	0001
0	slt	10	101010	slt	0111

Mapping of operation to ALU control input:


Opcode	Operation	ALUop	Funct	ALU action	ALU ctrl input
35	lw	00	XXXXXX	add	0010
43	sw	00	XXXXXX	add	0010
4	beq	01	XXXXXX	subtract	0110
0	add	10	100000	add	0010
0	sub	10	100010	subtract	0110
0	and	10	100100	AND	0000
0	or	10	100101	OR	0001
0	slt	10	101010	slt	0111

ALUop		Funct field						Operation
ALUop1	ALUop0	F5	F4	F3	F2	F1	F0	3210
0	0	X	X	X	X	X	X	0010
X(0)	1	X	X	X	X	X	X	0110
1	X(0)	X	X	0	0	0	0	0010
1	X(0)	X	X	0	0	1	0	0110
1	X(0)	X	X	0	1	0	0	0000
1	X(0)	X	X	0	1	0	1	0001
1	X(0)	X	X	1	0	1	0	0111

Mapping of operation to ALU control input:

Opcode	Operation	ALUOp	Funct	ALU action	ALU ctrl input
35	lw	00	XXXXXX	add	0010
43	sw	00	XXXXXX	add	0010
4	beq	01	XXXXXX	subtract	0110
0	add	10	100000	add	0010
0	sub	10	100010	subtract	0110
0	and	10	100100	AND	0000
0	or	10	100101	OR	0001
0	slt	10	101010	slt	0111

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	3210
0	0	X	X	X	X	X	X	0010
X(0)	1	X	X	X	X	X	X	0110
1	X(0)	X	X	0	0	0	0	0010
1	X(0)	X	X	0	0	1	0	0110
1	X(0)	X	X	0	1	0	0	0000
1	X(0)	X	X	0	1	0	1	0001
1	X(0)	X	X	1	0	1	0	0111

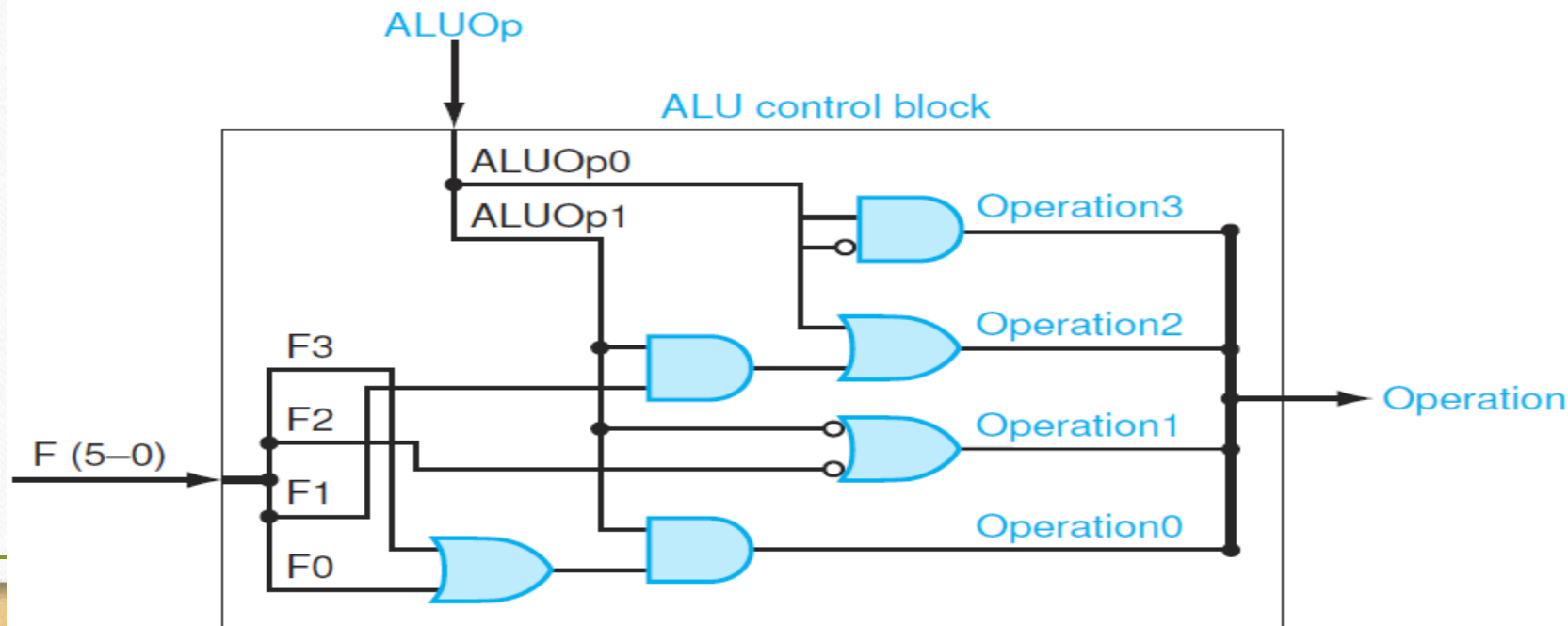

Type	Reg Dst	ALU Src	Mem ToReg	Reg Write	Mem Read	Mem Write	Branch	ALU op1	ALU op0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Type	Dec Opcode	Binary Opcode
R-format	0	000 000
lw	35	100 011
sw	43	101 011
beq	4	000 100

