


Digital Logic Design

Part 3

Binary digits

- Basic unit of information in digital communication: 0 or 1
- Represented internally as a high or low voltage
- Transistors : An on/off switch controlled by electricity

Transistors:

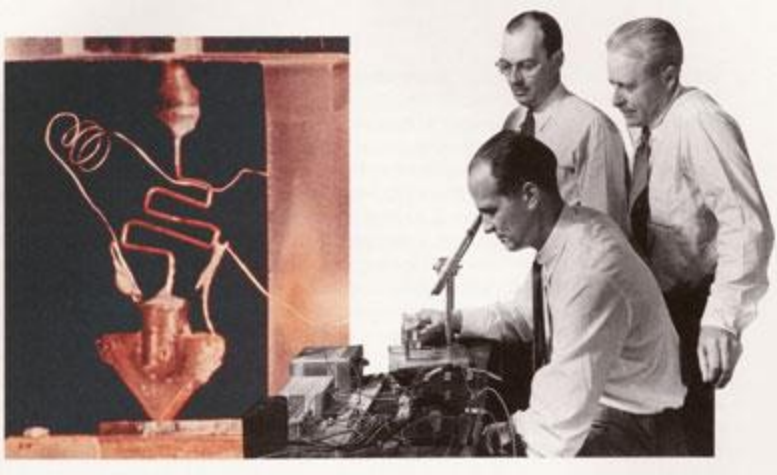

- **The first transistor was invented in 1947 by William Shockley John Bardeen and Walter Brattain at Bell Laboratories.**
- **Most important electronics event of the 20th century: leading to IC (integrated circuit) and microprocessor technology serving as the basis of electronics**

Background on Transistors

- First Early Computer: Charles Babbage and Early form of Computers
 - Used Relays or Vacuum Tubes to represent states of matter
- Transistors : Cheap, Reliable and Small

 - Voltage applied to a control terminal (On or Off is generated)
- 1959: Robert Noyce: (Cofounded Fairchild Semiconductor and Intel) patented a method of interconnecting many transistors on a single chip.
 - At that time transistors cost was ~\$10 😊

Background on Transistors

- First Early Computer: Charles Babbage and Early form of Computers
 - Used Relays or Vacuum Tubes to represent states of matter
- Transistors : Cheap, Reliable and Small

 - Voltage applied to a control terminal (On or Off is generated)
- 1959: Robert Noyce: (Cofounded Fairchild Semiconductor and Intel) patented a method of interconnecting many transistors on a single chip.
 - At that time transistors cost was ~\$10 ☺
 - Today we can pack ~1billion MOS or MOSFET transistors onto 1cm^2 silicon chip
 - Cost 10 microcents per transistor


MOSFETS : Metal-Oxide-semiconductor field effect transistors

Also Known As : MOS transistors

- Built from silicon (Si) : 4 valence electrons in outer shell
 - Silicon forms strong crystal lattice:
-
- All electrons tied up in adjacent bonds → Therefore poor conductor
 - However, (Si) becomes a better conductor when small amounts of impurities (called dopants) are added to this lattice structure
 - N-Type: Small amounts of Arsenic(5 valence electrons) atoms added – leaving extra floating electrons that are not involved in bonding. Negatively charge particles
 - P-Type: Small amounts of Boron(3 valence electrons) atoms added – leaving positively charged ions within the lattice: Results in Positively charged particles
 - Silicon becomes a Semiconductor with the addition of dopants

MOSFETS : Metal-Oxide-semiconductor field effect transistors


Also Known As : MOS transistors

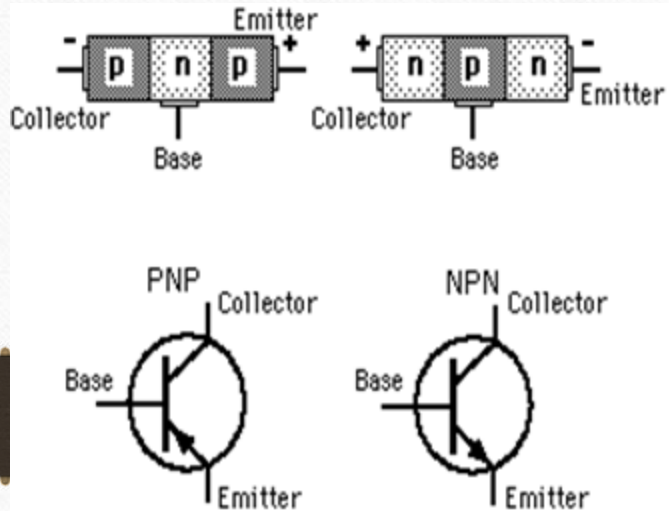

Physlinks.com

- MOS transistors :sandwich of layers of conducting and insulating materials
- nMOS (nnp) and pMOS (pnp)
- Base Collector and Emitter Model: **Gate-Source-Drain**
- **Two types of Transistors have opposite behaviours**
- **That compliment each other: CMOS uses both nMOS and pMOS**

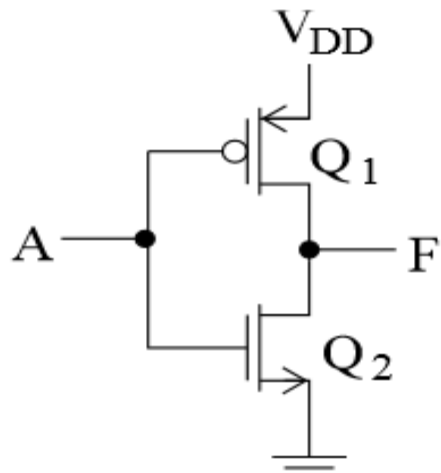- Further Reading
- <http://hyperphysics.phy-astr.gsu.edu/hbase/solids/dope.html#c4>
- <http://www.cs.mun.ca/~paul/transistors/node1.html>
- **Go To Course Notes: Section 2: Transistors/ Examples on Board**




A	Q_1	Q_2	F
0	Low	High	1
1	High	Low	0

PMOS and NMOS together form CMOS: Compliment MOS

WHY:

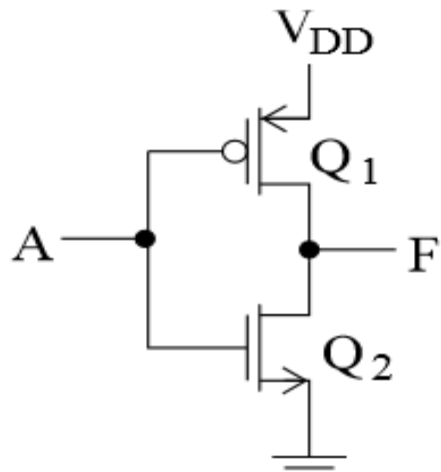***We want both 0, 1 signals to be Strong readings**
Use properties of NMOS and CMOS together



PMOS and NMOS together form CMOS:


A goes into the Gate at both Transistors

***Does a Signal pass or not pass**

***Are we connected to Ground**

A	Q_1	Q_2	F
0	Low	High	1
1	High	Low	0

→ That will determine F

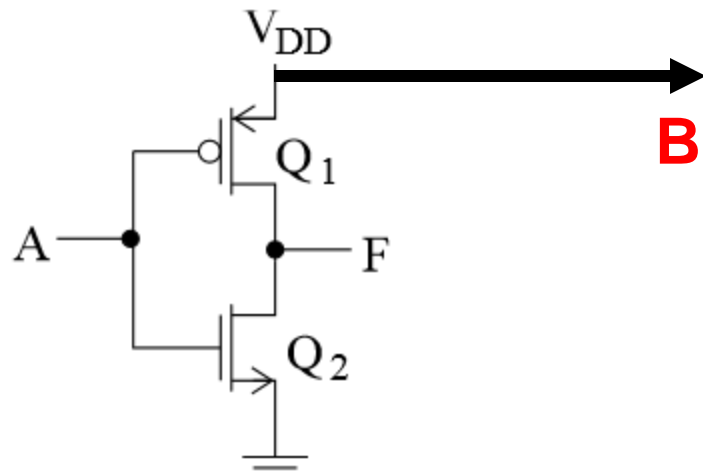


A	Q_1	Q_2	F
0	Low	High	1
1	High	Low	0

When $A = 0$

What is the Output at **B**:


- A) 1
- B) 0
- C) Neither
- D) V_{ss}
- E) Ground

CMOS NAND

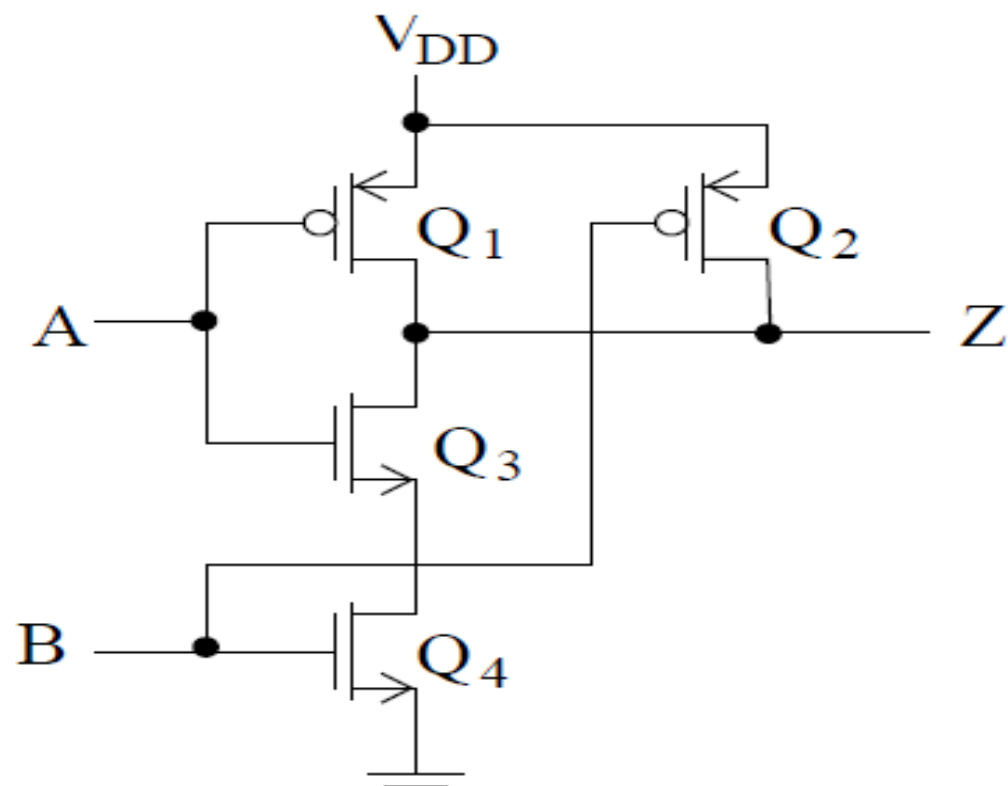

A	B	Q_1	Q_2	Q_3	Q_4	Z
0	0	Low	Low	High	High	1
0	1					
1	0					
1	1					

CMOS NAND

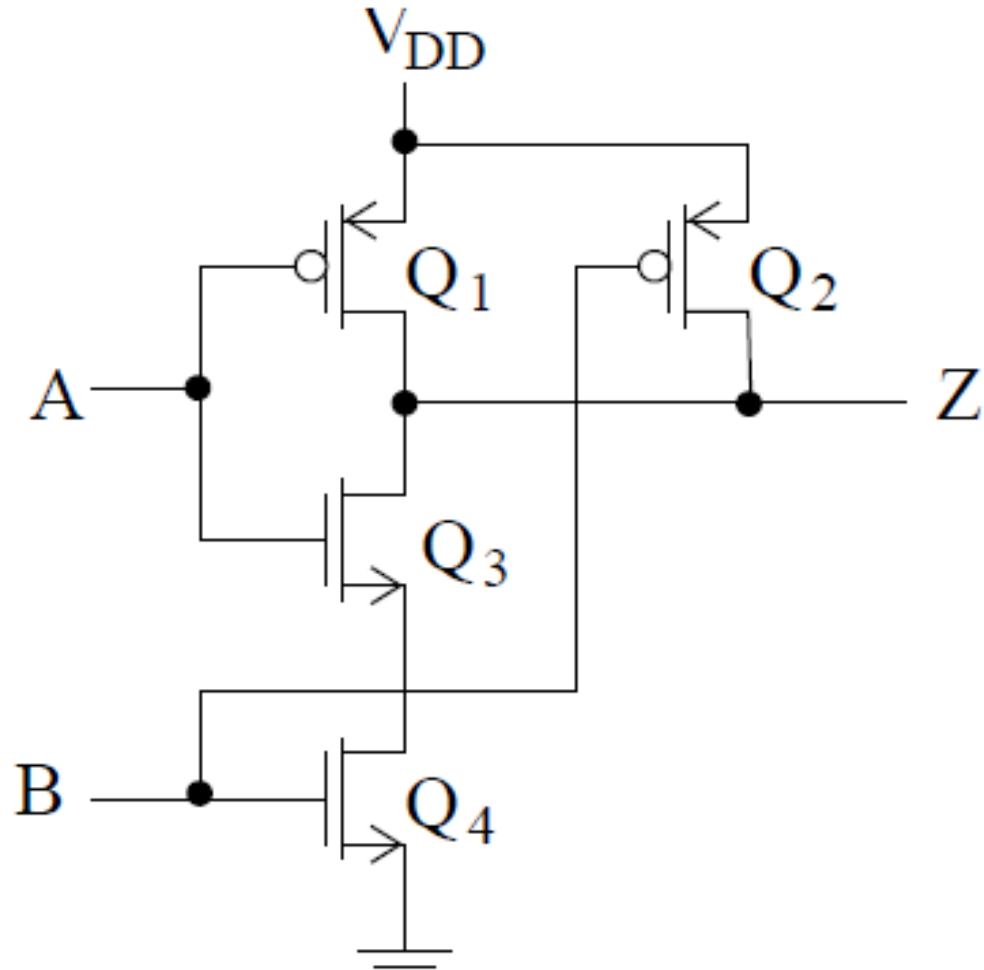


Scale up to 3 input NAND
GATE

Add one more NMOS and one
more PMOS per input

CMOS AND and OR

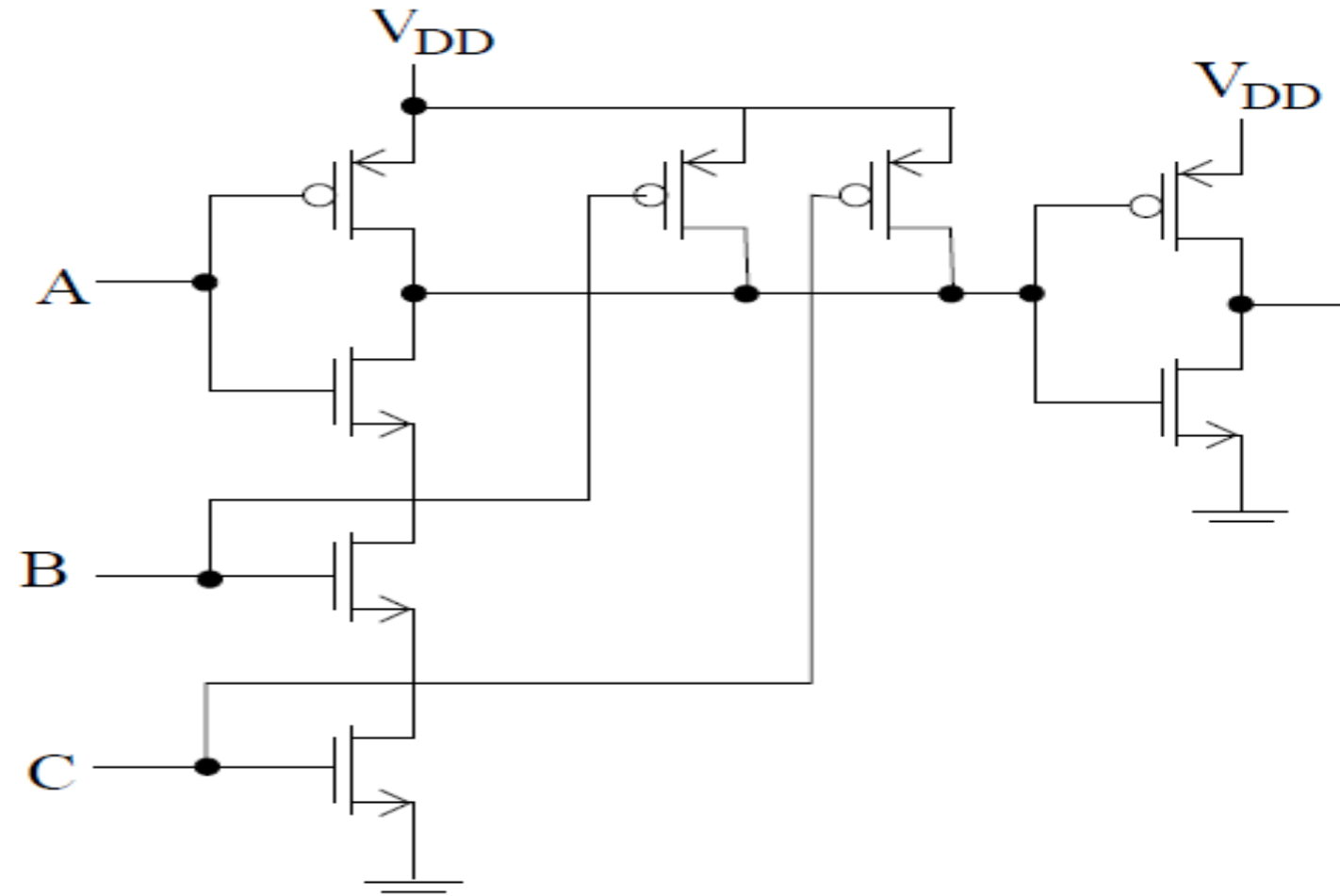- To get AND and OR, add inverter at end
- Example: 3 Input AND




- Thus, NAND is preferred to AND in actual circuits

CMOS AND and OR

- To get AND and OR, add inverter at end
- Example: 3 Input AND

Designing our circuits
Using NAND gates
Is easier from
Implementation
Perspective.

Less Transistors
In the hardware

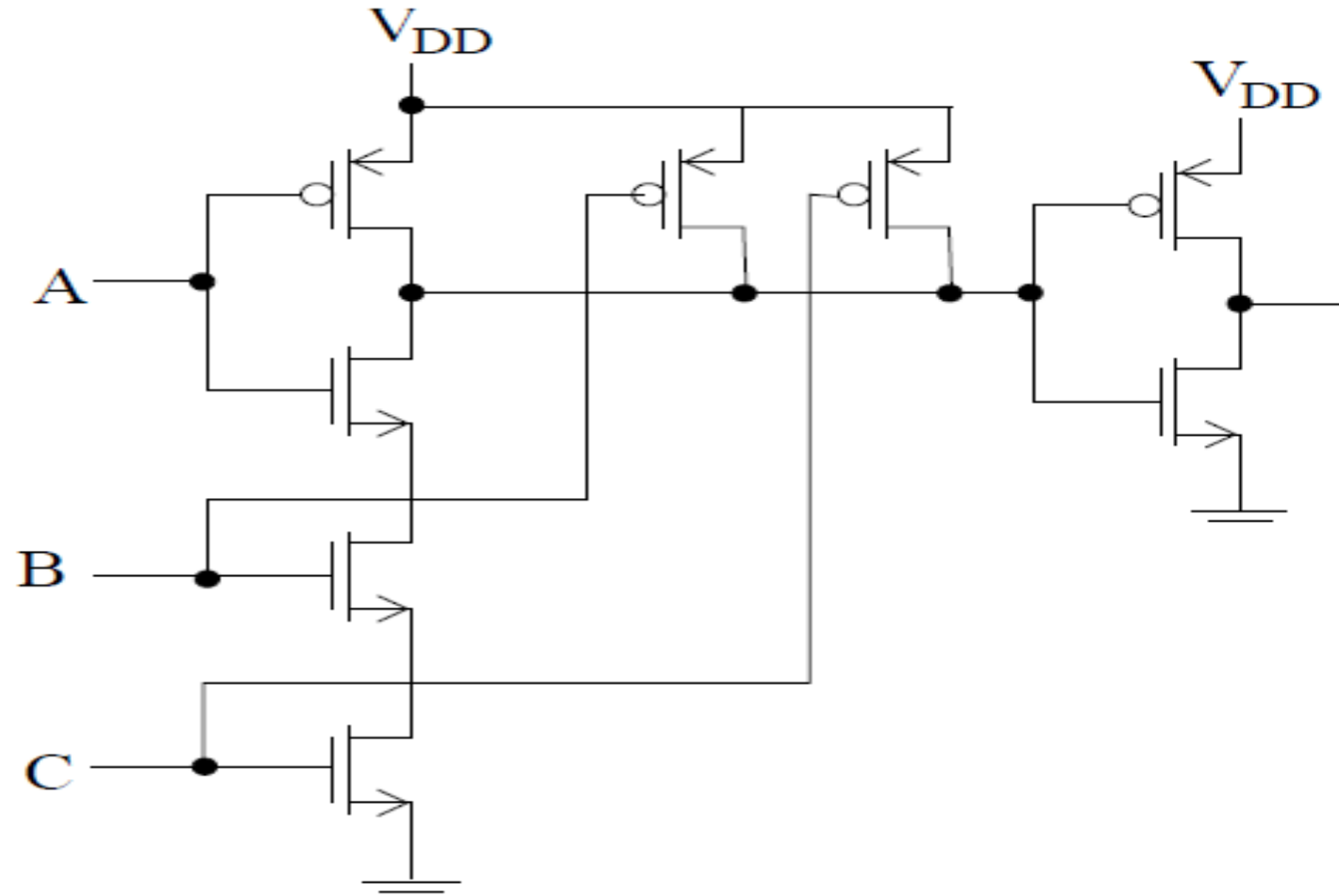

- Thus, NAND is preferred to AND in actual circuits